
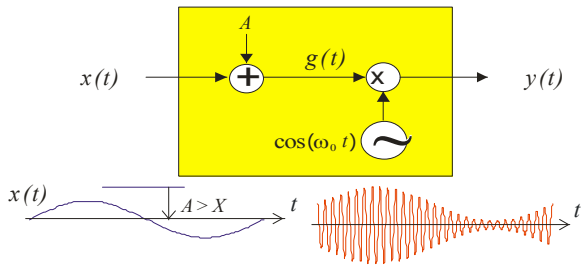



Amplitudni modulator AM-DSB-LC

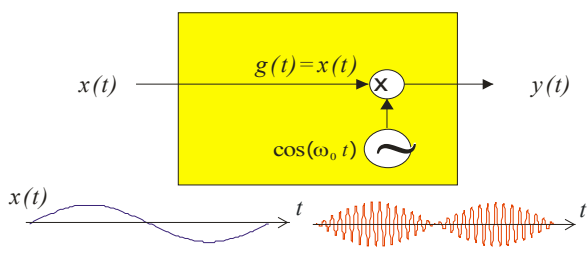


Amplitudni modulator AM-DSB-SC




demodulator AM-DSB-LC detektor ovojnice

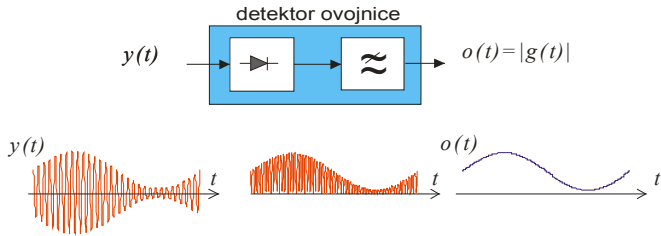


demodulator AM-DSB-SC sinhroni detektor:

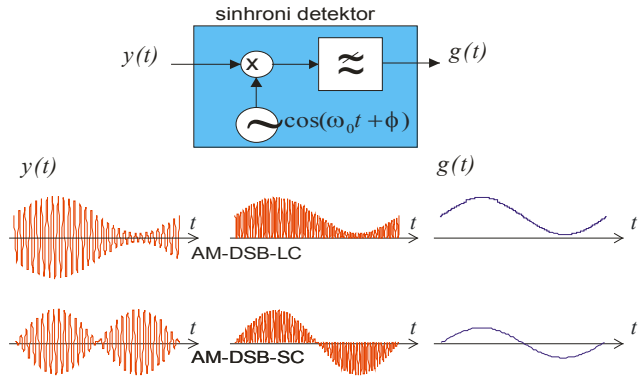


Frekvenčni modulator

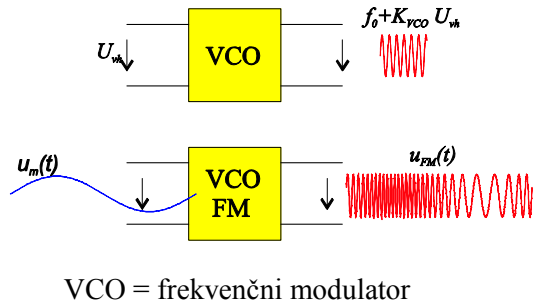


Fazno ujeta zanka PLL

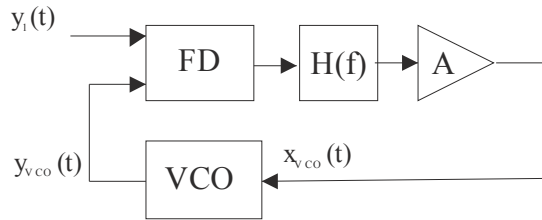


nelinearni fazni detektor

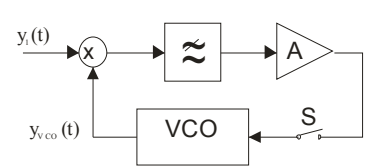


Binarni PAM-2

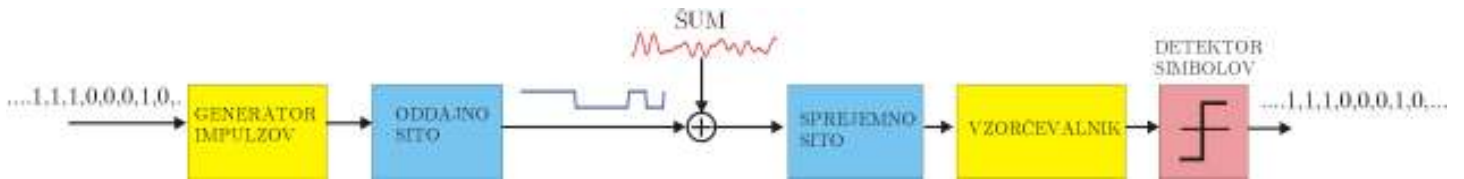


Binarni ASK modulator:

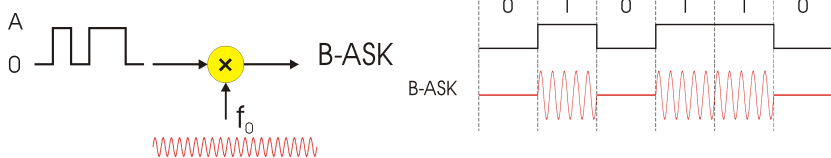


Binarni PSK modulator:

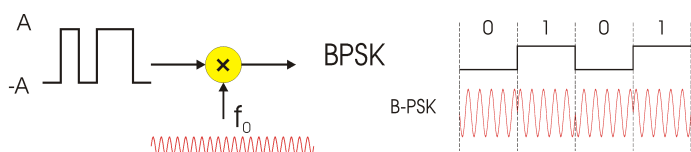

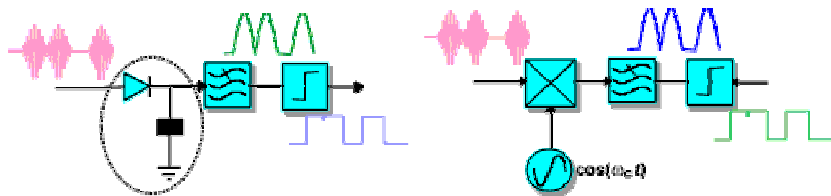
ASK demodulator: detektor ovojnice in koherentni detektor



PSK demodulator: koherentni detektor

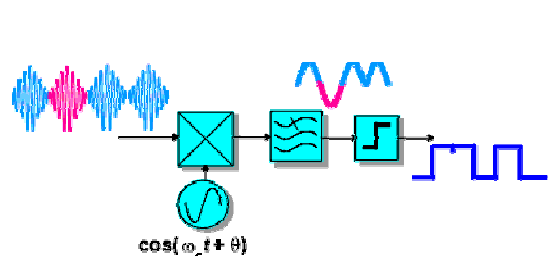

Binarni FSK modulator:

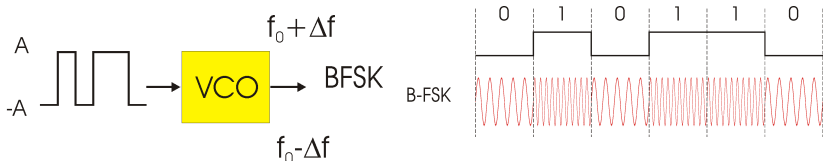

FSK demodulator:

- PLL demodulator (levo),
- nekoherentni detektor dveh ASK signalov (desno)

