

Digital Integrated Circuits


A Design Perspective

Jan M. Rabaey
Anantha Chandrakasan
Borivoje Nikolic

The Wire

July 30, 2002

The Wire

 


schematics




physical


Interconnect Impact on Chip

 

Wire Models

 


All-inclusive model

 


Capacitance-only

Impact of Interconnect Parasitics

 - Interconnect parasitics
 - reduce reliability
 - affect performance and power consumption
- Classes of parasitics
 - Capacitive
 - Resistive
 - Inductive



Nature of Interconnect

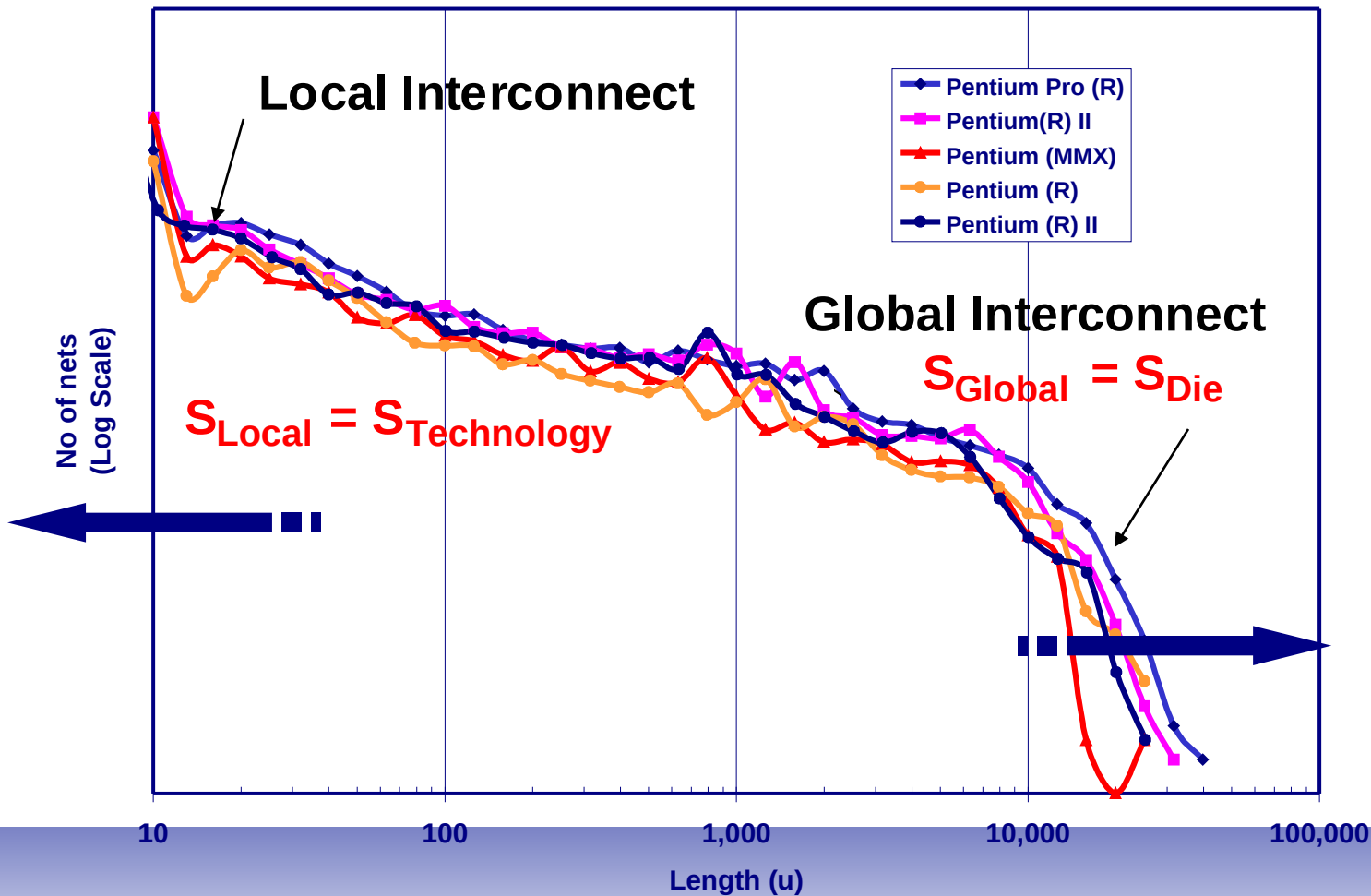


Source: Intel

INTERCONNECT

Capacitance




Capacitance of Wire Interconnect

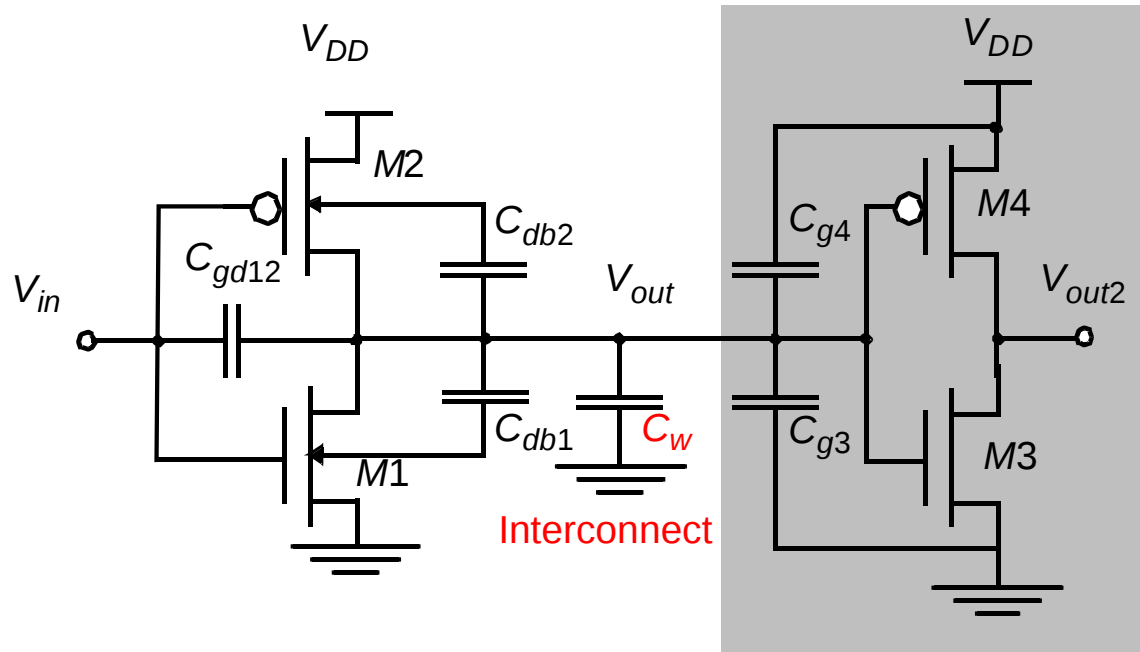


Interconnect

Fanout

Simplified Model

 

Capacitance: The Parallel Plate Model

 


$$C_{int} = \frac{\epsilon_{di}}{t_{di}} WL$$

$$S_{Cwire} = \frac{S}{S \cdot S_L} = \frac{1}{S_L}$$

Permittivity


Material	ϵ_r
Free space	1
Aerogels	~1.5
Polyimides (organic)	3-4
Silicon dioxide	3.9
Glass-epoxy (PC board)	5
Silicon Nitride (Si_3N_4)	7.5
Alumina (package)	9.5
Silicon	11.7

Fringing Capacitance

 


(a)
 
$$C_{wire} = C_{pp} + C_{fringe} = \frac{w\epsilon_{di}}{t_{di}} + \frac{2\pi\epsilon_{di}}{\log(t_{di}/H)}$$




(b)

Fringing versus Parallel Plate

 


(from [Bakoglu89])

Interwire Capacitance

 

Impact of Interwire Capacitance

 

(from [Bakoglu89])

Wiring Capacitances (0.25 μm CMOS)


	Field	Active	Poly	Al1	Al2	Al3	Al4
Poly	88						
	54						
Al1	30	41	57				
	40	47	54				
Al2	13	15	17	36			
	25	27	29	45			
Al3	8.9	9.4	10	15	41		
	18	19	20	27	49		
Al4	6.5	6.8	7	8.9	15	35	
	14	15	15	18	27	45	
Al5	5.2	5.4	5.4	6.6	9.1	14	38
	12	12	12	14	19	27	52

INTERCONNECT

Resistance




Wire Resistance

 

$$R = \frac{\rho L}{HW}$$

Sheet Resistance
 R_0

 


Interconnect Resistance

Material	ρ ($\Omega\text{-m}$)
Silver (Ag)	1.6×10^{-8}
Copper (Cu)	1.7×10^{-8}
Gold (Au)	2.2×10^{-8}
Aluminum (Al)	2.7×10^{-8}
Tungsten (W)	5.5×10^{-8}

Dealing with Resistance

- ❑ **Selective Technology Scaling**
- ❑ **Use Better Interconnect Materials**
 - reduce average wire-length
 - e.g. copper, silicides
- ❑ **More Interconnect Layers**
 - reduce average wire-length

Polycide Gate MOSFET

 


Silicides: WSi_2 , TiSi_2 , PtSi_2 and TaSi

Conductivity: 8-10 times better than Poly

Sheet Resistance

Material	Sheet Resistance (Ω/\square)
n- or p-well diffusion	1000 – 1500
n^+ , p^+ diffusion	50 – 150
n^+ , p^+ diffusion with silicide	3 – 5
n^+ , p^+ polysilicon	150 – 200
n^+ , p^+ polysilicon with silicide	4 – 5
Aluminum	0.05 – 0.1

Modern Interconnect

 

Example: Intel 0.25 micron Process


5 metal layers

Ti/Al - Cu/Ti/TiN

Polysilicon dielectric

<u>LAYER</u>	<u>PITCH</u>	<u>THICK</u>	<u>A.R.</u>
Isolation	0.67	0.40	-
Polysilicon	0.64	0.25	-
Metal 1	0.64	0.48	1.5
Metal 2	0.93	0.90	1.9
Metal 3	0.93	0.90	1.9
Metal 4	1.60	1.33	1.7
Metal 5	2.56	1.90	1.5
	μm	μm	

Layer pitch, thickness and aspect ratio

 

INTERCONNECT




Inductance






Interconnect Modeling

The Lumped Model

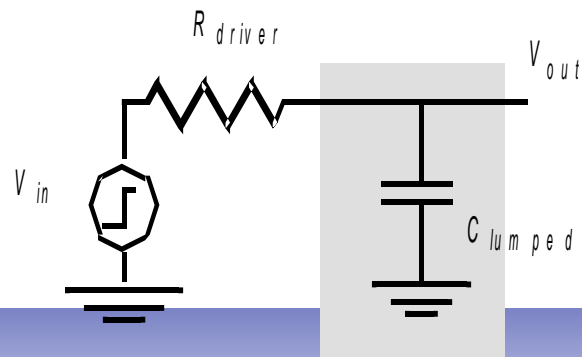 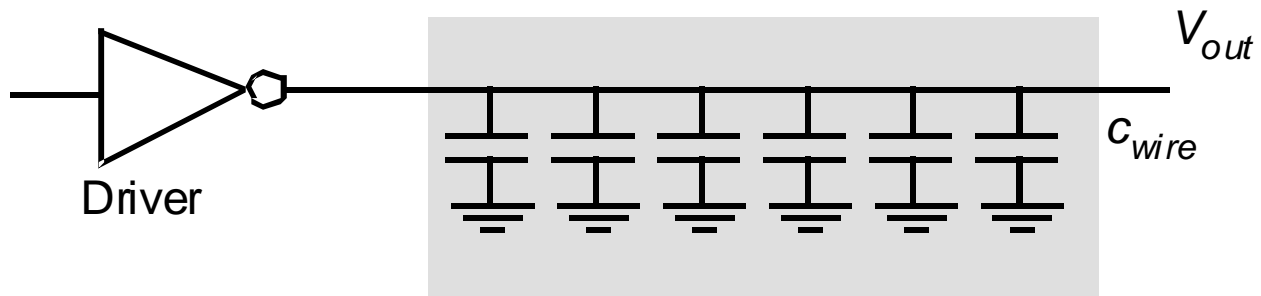

The Lumped RC-Model

The Elmore Delay

 


$$R_{ik} = \sum_{j \in N} R_j \Rightarrow (R_j \in [path(s \rightarrow i) \cap path(s \rightarrow k)])$$

$$\tau_{Di} = \sum_{k=1}^N C_k R_{ik}$$

The Ellmore Delay

RC Chain

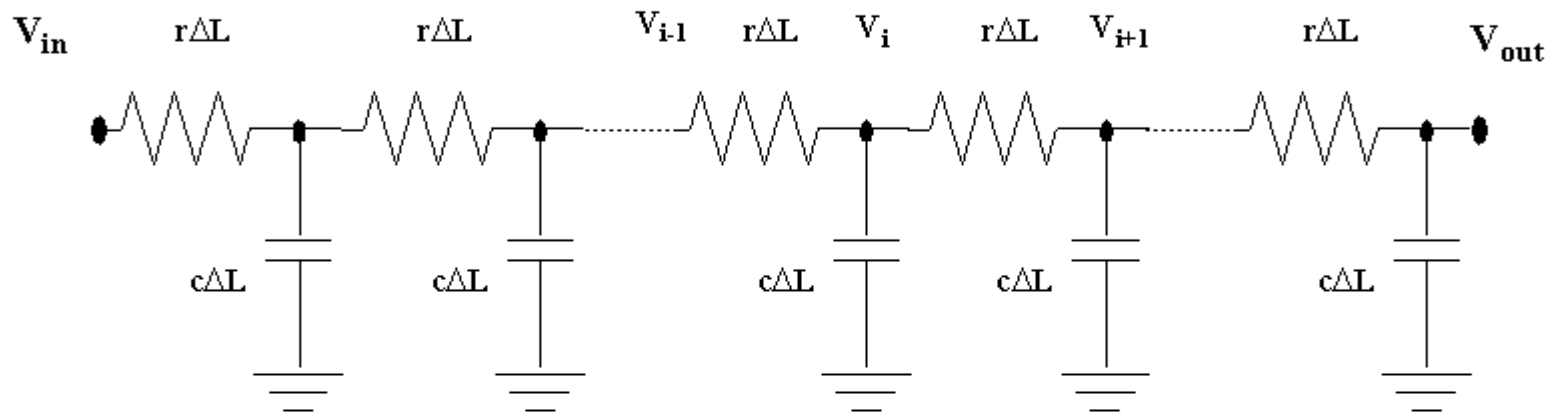

$$\tau_N = \sum_{i=1}^N R_i \sum_{j=i}^N C_j = \sum_{i=1}^N C_i \sum_{j=1}^i R_j$$

Wire Model




Assume: Wire modeled by N equal-length segments

$$\tau_{DN} = \left(\frac{L}{N}\right)^2 (rc + 2rc + \dots + Nrc) = (rcL^2) \frac{N(N+1)}{2N^2} = RC \frac{N+1}{2N}$$

For large values of N:

$$\tau_{DN} = \frac{RC}{2} = \frac{rcL^2}{2}$$

The Distributed RC-line

   


The diffusion equation

$$rc \frac{\partial V}{\partial t} = \frac{\partial^2 V}{\partial x^2}$$

$$\tau(V_{out}) = \frac{rc L^2}{2}$$

 
Step-response of RC wire as a function of time and space




RC-Models

Voltage Range	Lumped RC-network	Distributed RC-network
0→50% (t_p)	0.69 RC	0.38 RC
0→63% (τ)	RC	0.5 RC
10%→90% (t_T)	2.2 RC	0.9 RC

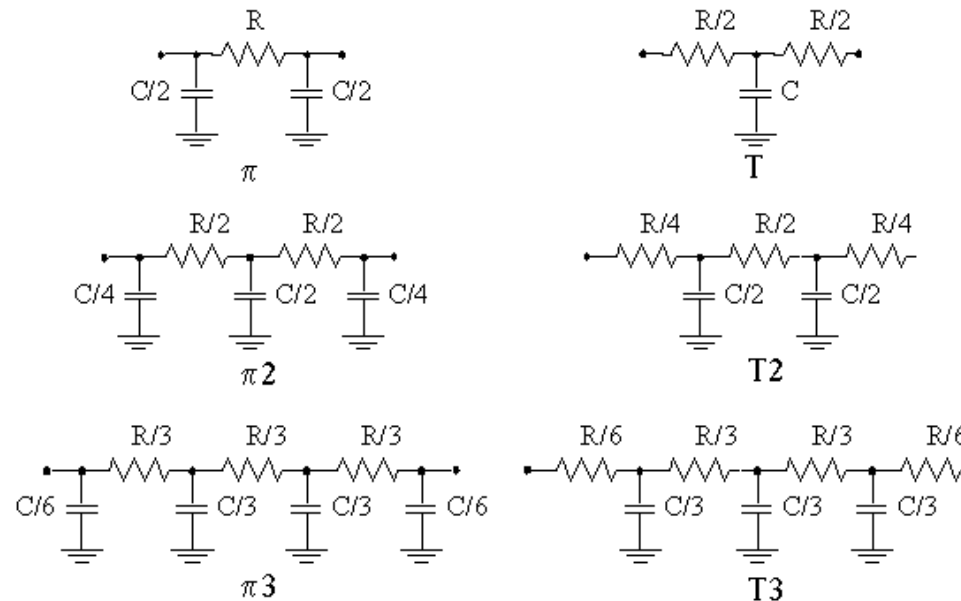Step Response of Lumped and Distributed RC Networks:
Points of Interest.



Driving an RC-line

 

$$\tau_D = R_s C_w + \frac{R_w C_w}{2} = R_s C_w + 0.5 r_w c_w L^2$$

$$t_p = 0.69 R_s C_w + 0.38 R_w C_w$$

Design Rules of Thumb

- rc delays should only be considered when $t_{pRC} \gg t_{pgate}$ of the driving gate

$$L_{crit} \gg \sqrt{t_{pgate} / 0.38rc}$$

- rc delays should only be considered when the rise (fall) time at the line input is smaller than RC, the rise (fall) time of the line

$$t_{rise} < RC$$

- when not met, the change in the signal is slower than the propagation delay of the wire