

KOMEL

P7

Digitalni svet

Gradniki digitalnih vezij: logična in sekvenčna vezja

Digitalna komunikacijska vezja

Vir: Floyd, poglavje 1 in 13.

15/11/2012

Koliko je že ura?



Računalniški številski sistem: binarni sistem

- Uporablja se binarni številski sistem: 0 in 1

8 bitov – byte

4 biti – nibble

- Enomestno binarno število je **bit – enota informacije**

Večina računalnikov uporablja 32, 64 in 128 bitne besede

1101 1100 0101 0001 1111 1010 0011 1101

- Računalniki izvajajo operacije nad zaporedjem bitov, ki jih imenujemo **besede**

Vgrajeni procesorji tudi še 8 in 16 bitne besede



= 1



= 0

Binarni zapis

$$\begin{aligned} 1011 &= 1*2^3 + 0*2^2 + 1*2^1 + \\ &\quad 1*2^0 \\ &= 8 + 0 + 2 + 1 = 11 \end{aligned}$$

- Desetiški sistem: osnova 10
 - 0, 1, 2, 3, 4, 5, 6, 7, 8, 9
- Binarni sistem: osnova 2
 - 0, 1

1	0	1	1
2^3	2^2	2^1	2^0

Primer 4 bitnega zapisa

10	2
0	0 0 0 0
1	0 0 0 1
2	0 0 1 0
3	0 0 1 1
4	0 1 0 0
5	0 1 0 1
6	0 1 1 0
7	0 1 1 1
8	1 0 0 0
9	1 0 0 1
10	1 0 1 0
11	1 0 1 1
12	1 1 0 0
13	1 1 0 1
14	1 1 1 0
15	1 1 1 1

Šestnajstiški sistem

- Uporablja se zaradi preproste pretvorbe iz dvojiškega sistema

$$16 = 2^4$$

- 4 biti binarnega sistema predstavljajo eno mesto v šestnajstiškem sistemu

2:	1001	0001	1010	1111
16:	9	1	A	F

Nabor 16 cifer:

0, 1, 2, 3, 4, 5, 6, 7, 8, 9, A, B, C, E, F

10	2	16
0	0 0 0 0	0
1	0 0 0 1	1
2	0 0 1 0	2
3	0 0 1 1	3
4	0 1 0 0	4
5	0 1 0 1	5
6	0 1 1 0	6
7	0 1 1 1	7
8	1 0 0 0	8
9	1 0 0 1	9
10	1 0 1 0	A
11	1 0 1 1	B
12	1 1 0 0	C
13	1 1 0 1	D
14	1 1 1 0	E
15	1 1 1 1	F

Pretvorba 2 → 16

- Vzemimo primer procesorja z dolžino besede 32 bitov:

01111000101001011010111110111110₂

– uredimo v skupine po 4 bite:

0111 1000 1010 0101 1010 1111 1011 1110₂

7 8 A 5 A F B E₁₆

- Šestnajstiški zapis ima ponavadi predpono 0x:

01111000101001011010111110111110₂ = 0x78A5AFBE

Logične operacije

Boolova algebra

Logične operacije

- Negacija (eniški komplement)
 - Negiramo vse bite v besedi

a	NE a
0	1
1	0



1011 1101 1111 0000


→

0100 0010 0000 1111


Logične operacije

- Logični ALI (OR)
 - Izhod je 1, če je 1 prvi ali drugi ali oba

$$0001 \mid 0010 = 0011$$

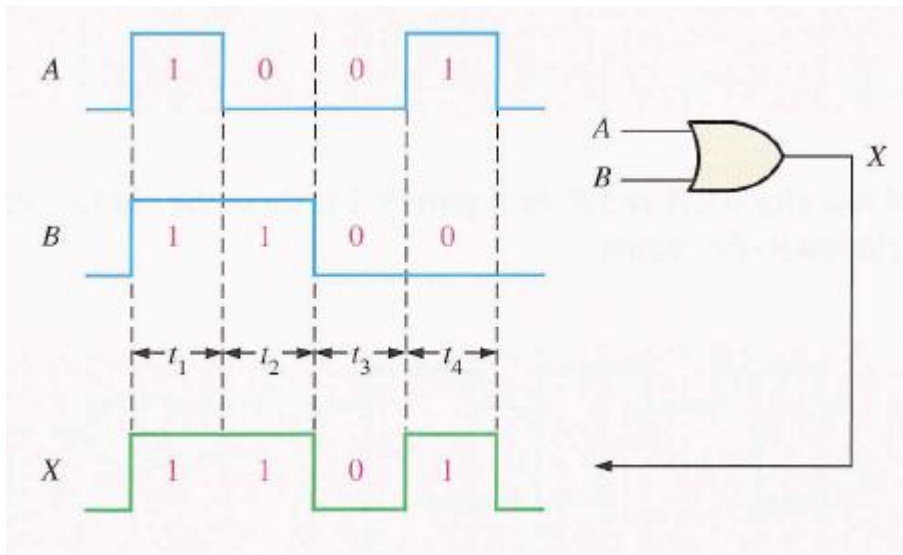

a	b	a ALI b
0	0	0
0	1	1
1	0	1
1	1	1

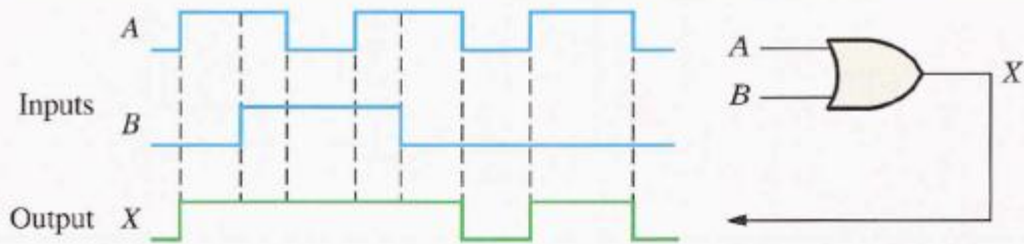


► **FIGURE 3-24**

A simplified intrusion detection system using an OR gate.

Open door/window sensors

HIGH = Open
LOW = Closed

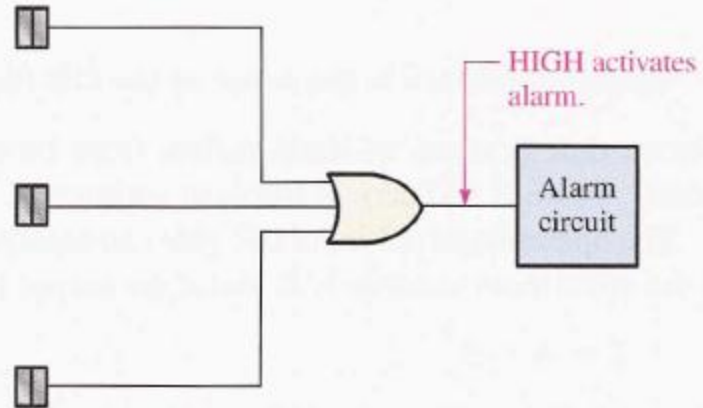



Logične operacije


- Logični IN (AND)
 - Izhod je 1, če je 1 prvi in drugi

a	b	a IN b
0	0	0
0	1	0
1	0	0
1	1	1

$$0011 \& 0001 = 0001$$

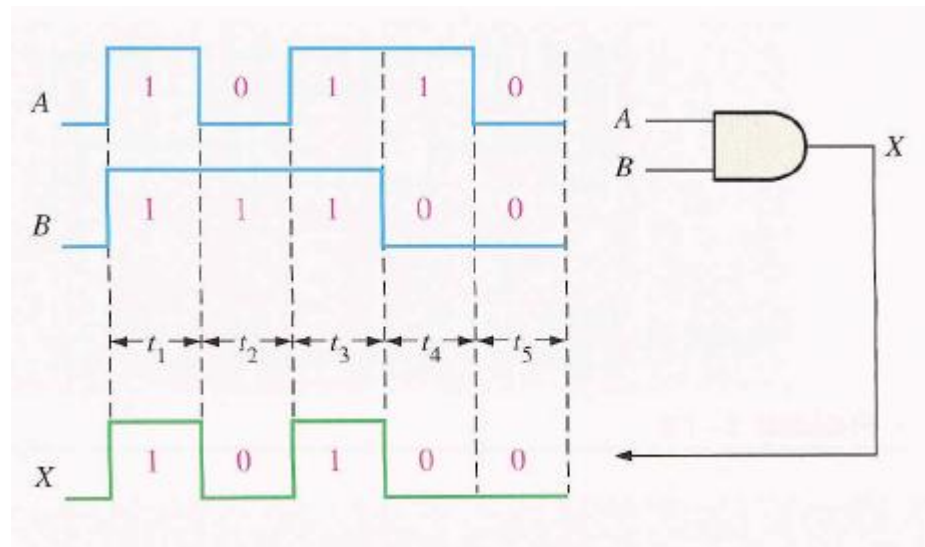

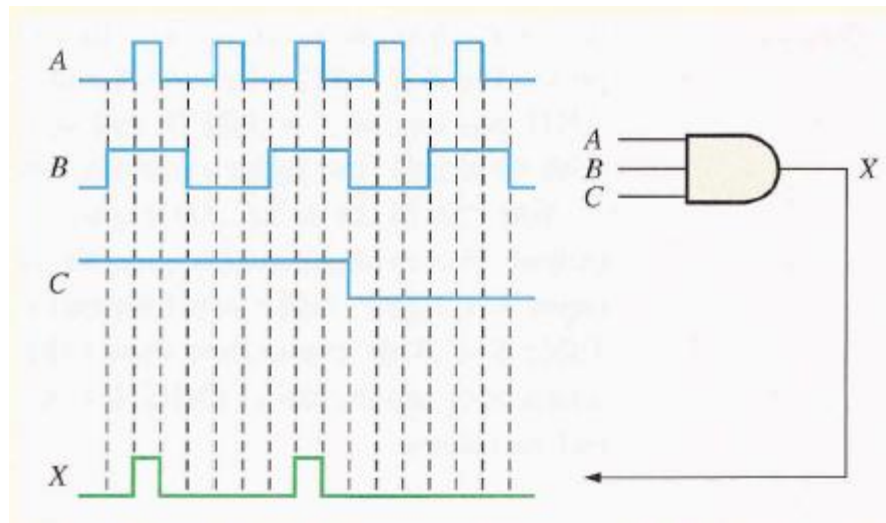

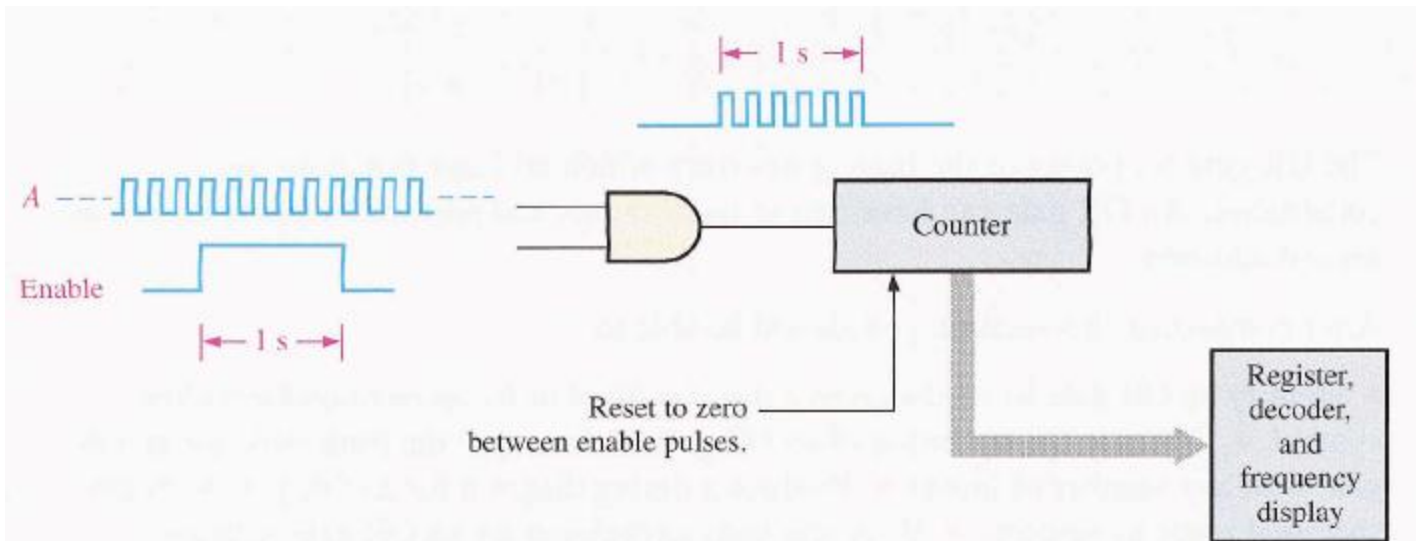

▲ **FIGURE 3-15**


An AND gate performing an enable/inhibit function for a frequency counter.

HIGH = On
LOW = Off

HIGH = Unbuckled
LOW = Buckled


Ignition switch
A

Seat belt
B

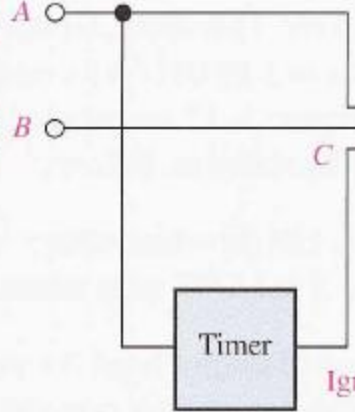



▲ **FIGURE 3-16**

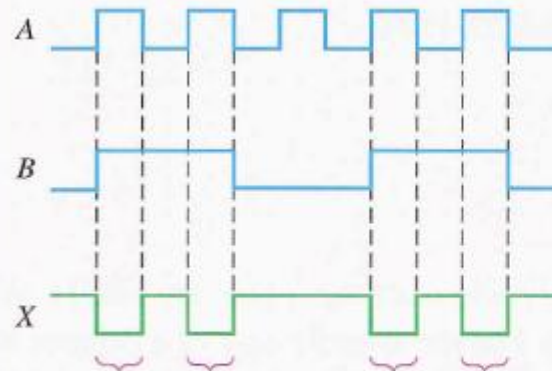
A simple seat belt alarm circuit using an AND gate.




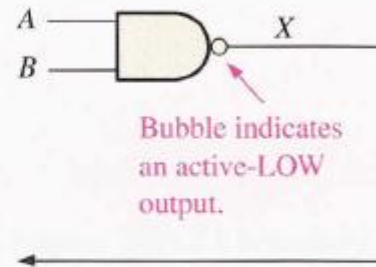
A and B are both HIGH during these four time intervals. Therefore X is LOW.




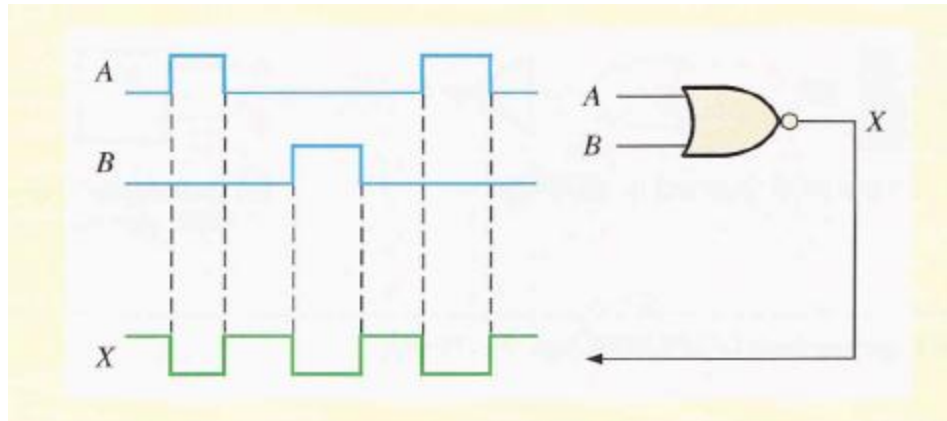

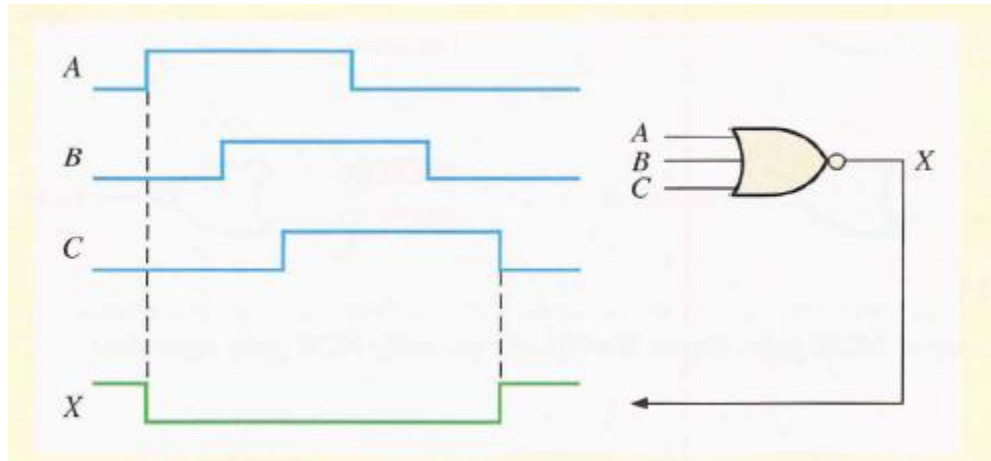

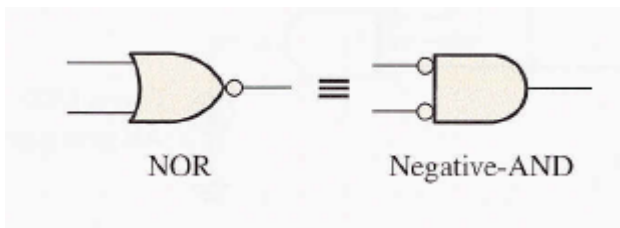

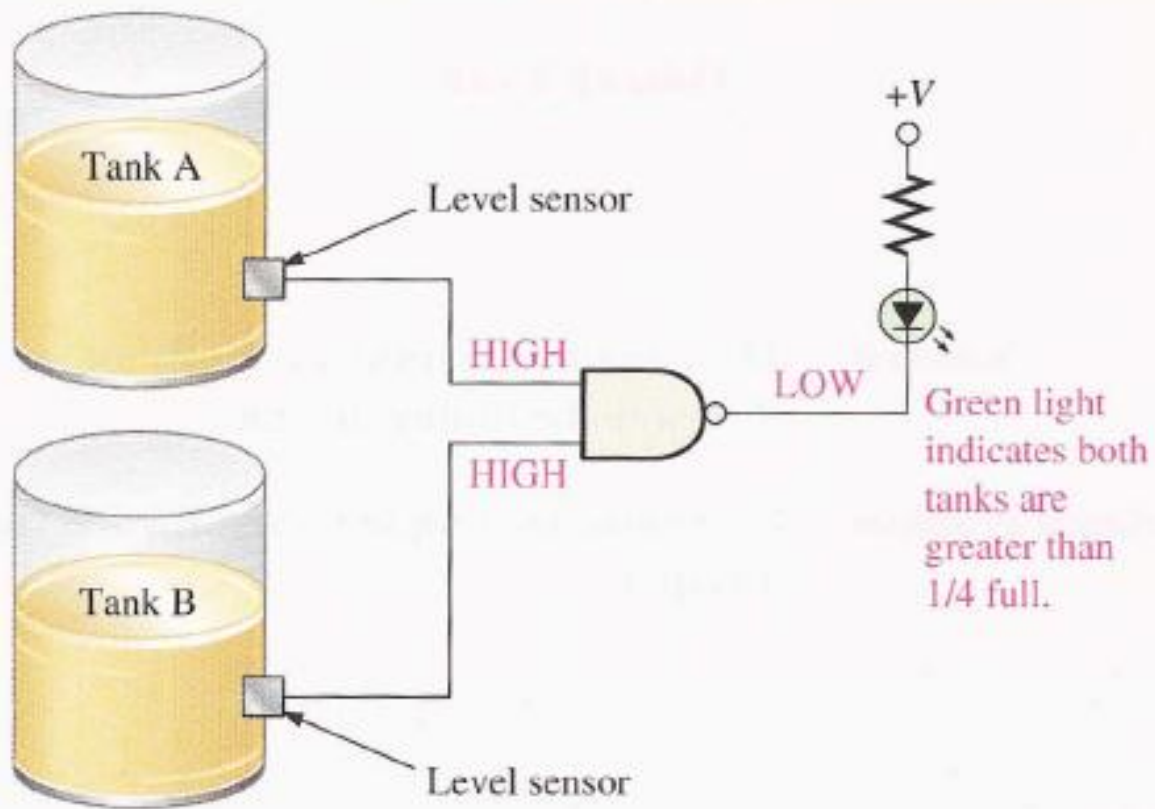

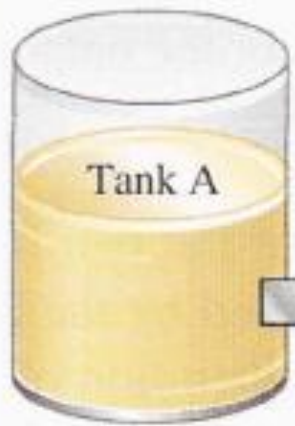


HIGH


LOW

HIGH





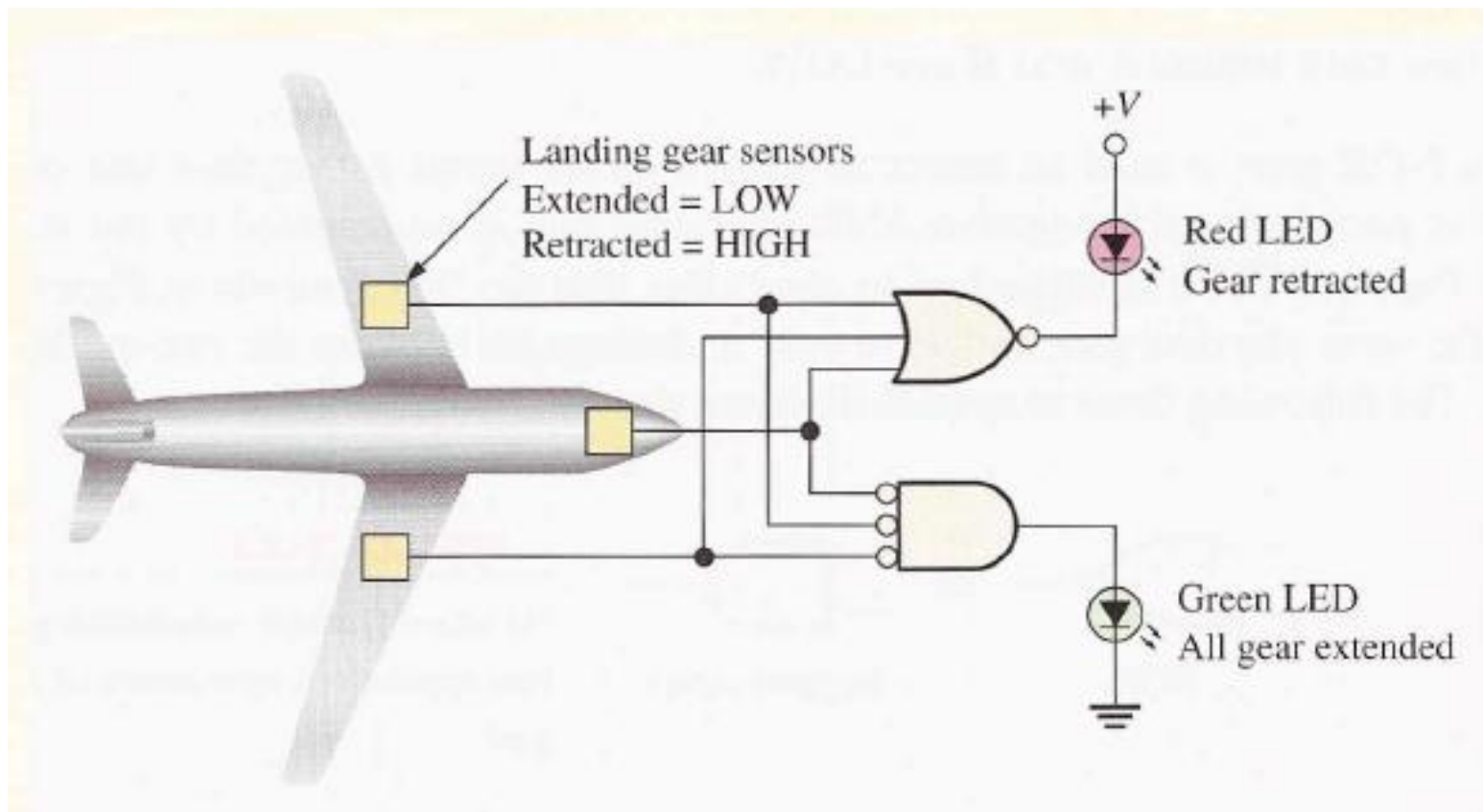Red light indicates one or both tanks are less than 1/4 full.



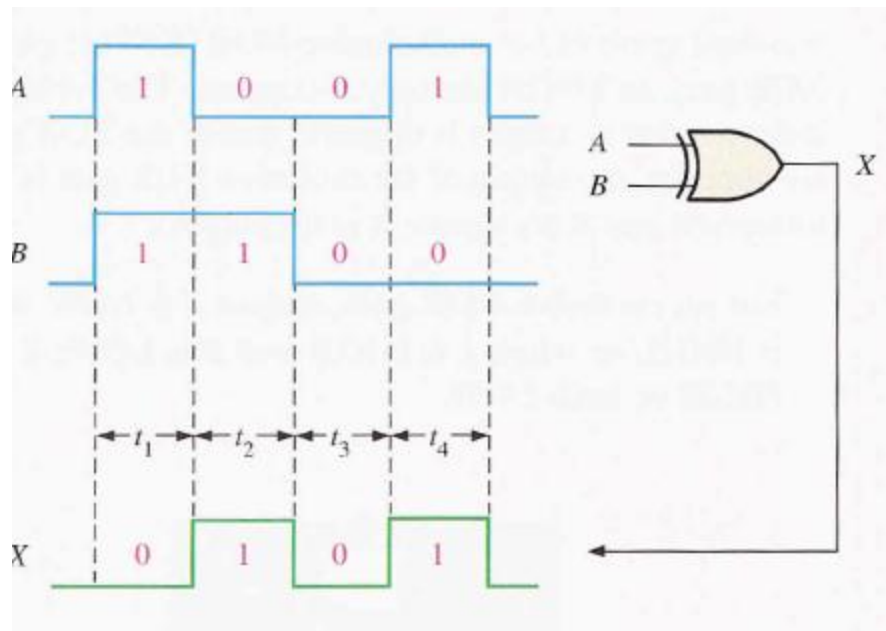



Input bits		Output (sum)
A	B	Σ
0	0	0
0	1	1
1	0	1
1	1	0 (without 1 carry)

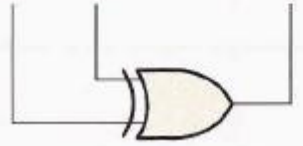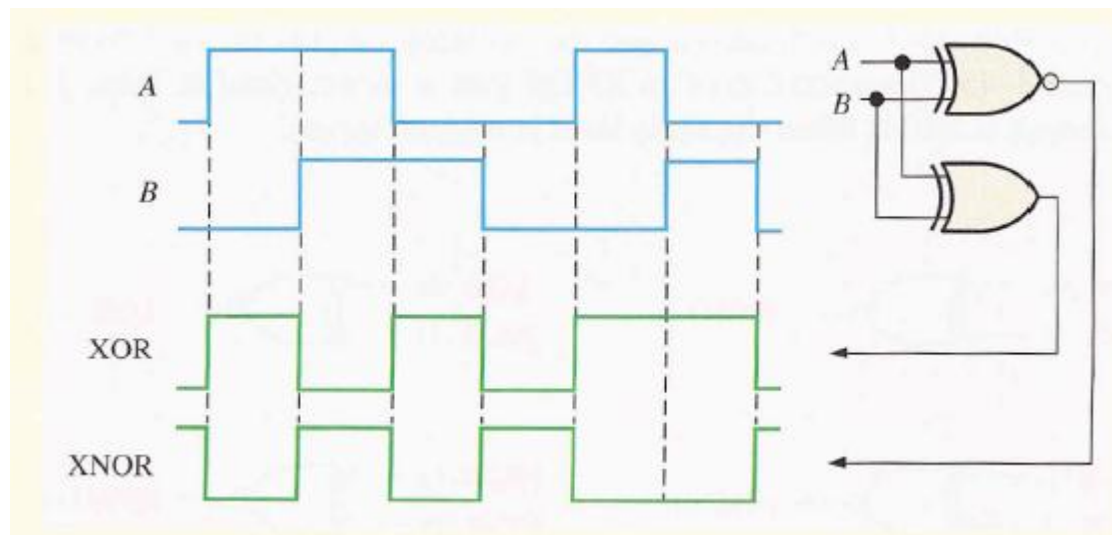



Gradniki digitalnih vezij


- Logična vezja
- Pomnilna vezja

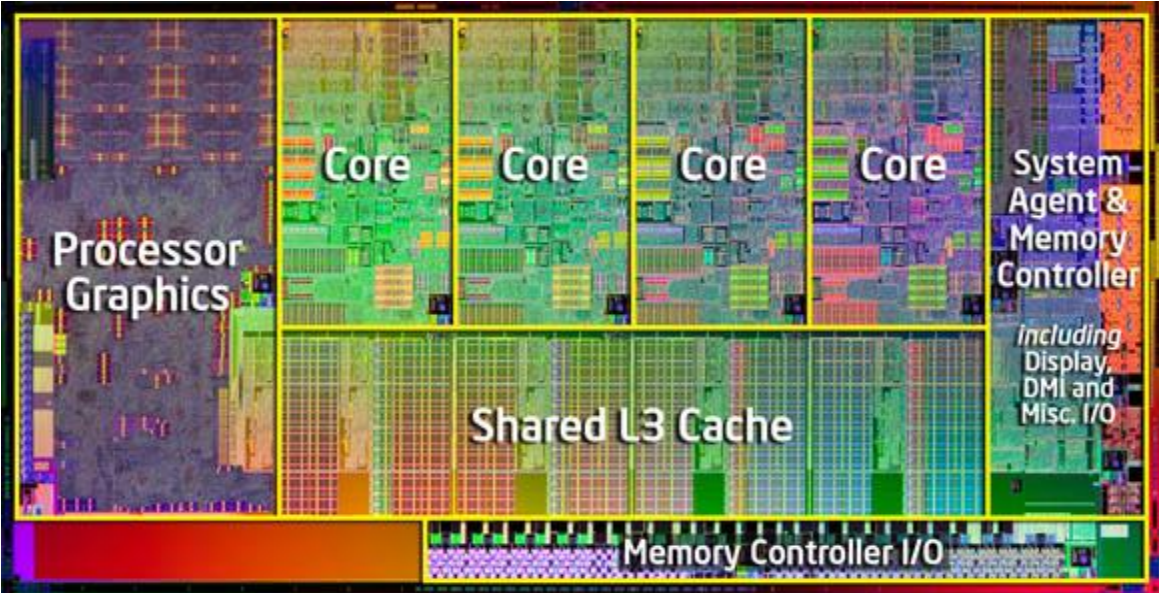

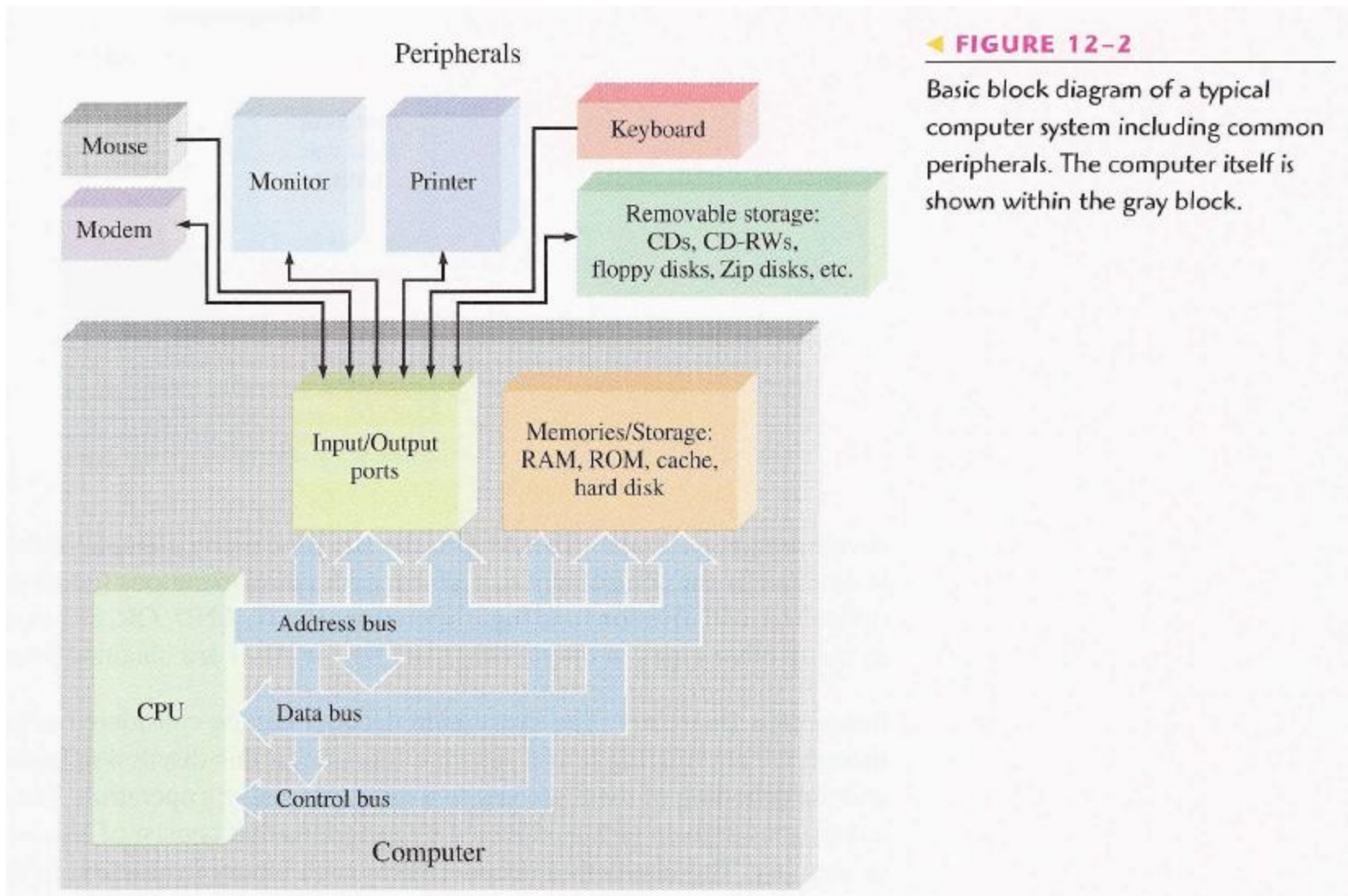


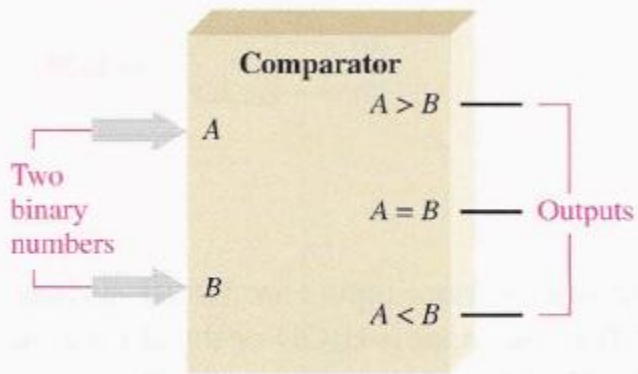


(a) Basic magnitude comparator

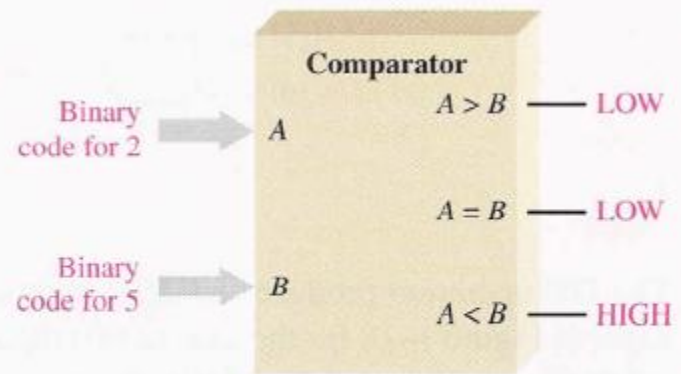


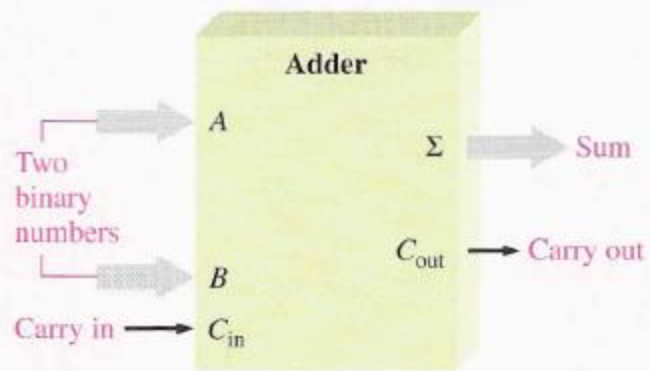
(b) Example: A is less than B ($2 < 5$) as indicated by the HIGH output ($A < B$)






(a) Basic adder






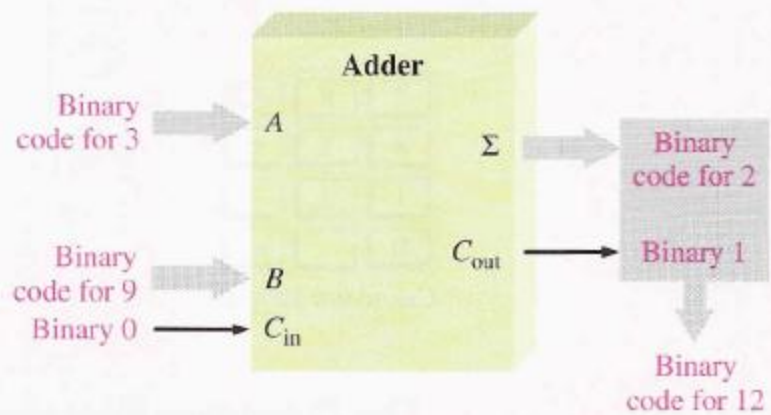



(b) Example: A plus B ($3 + 9 = 12$)

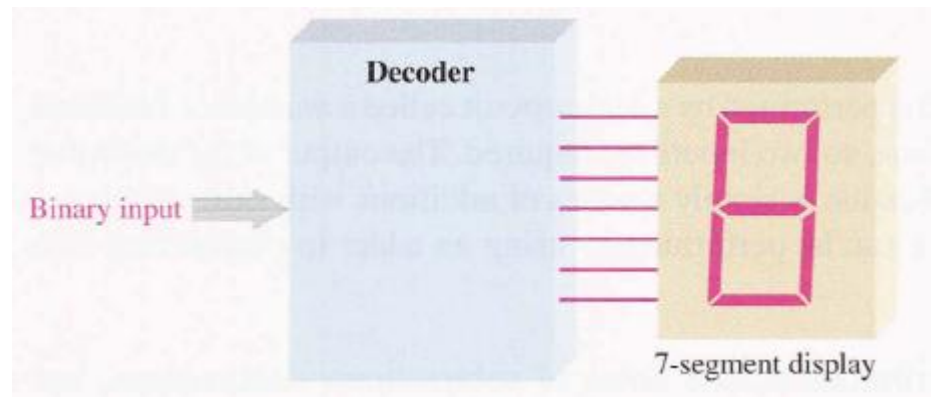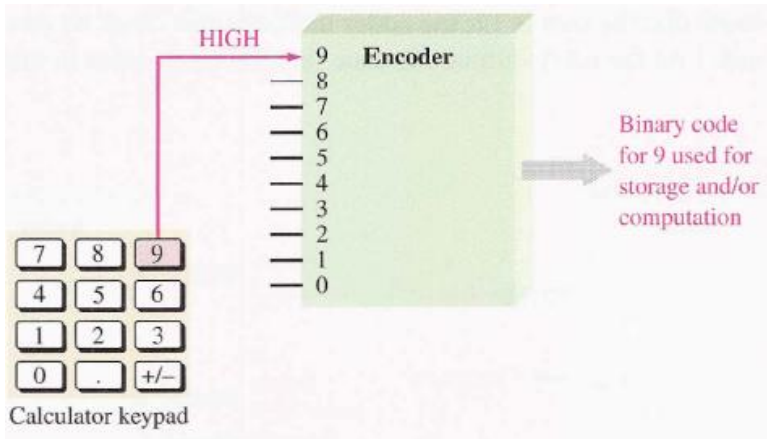

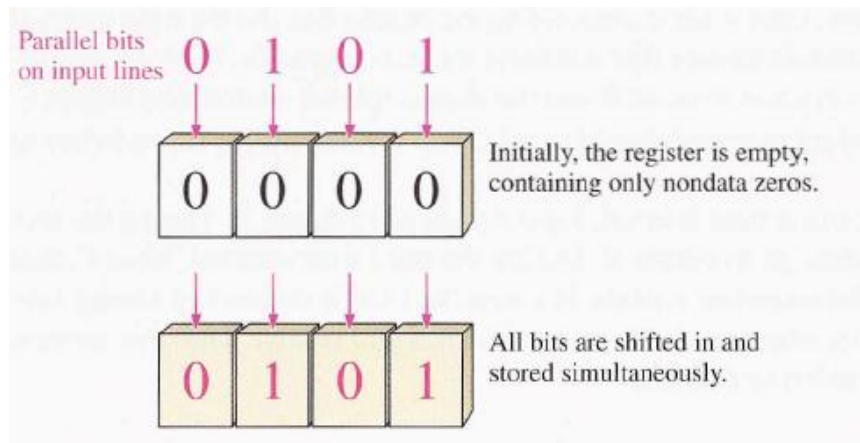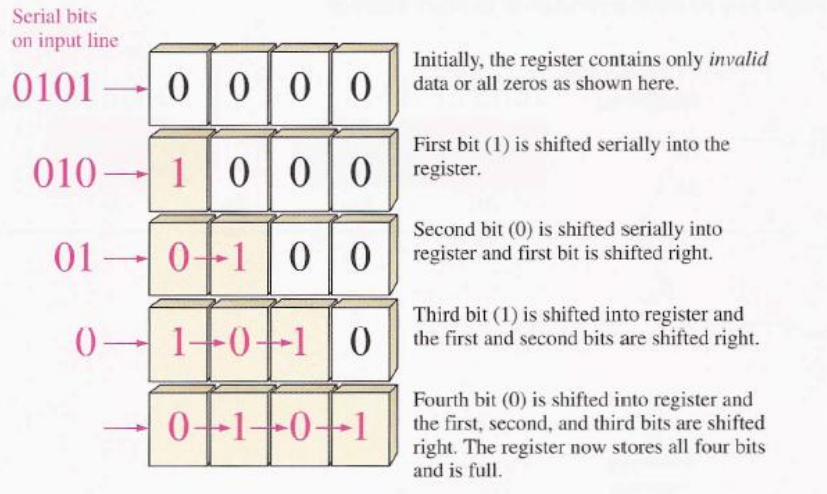

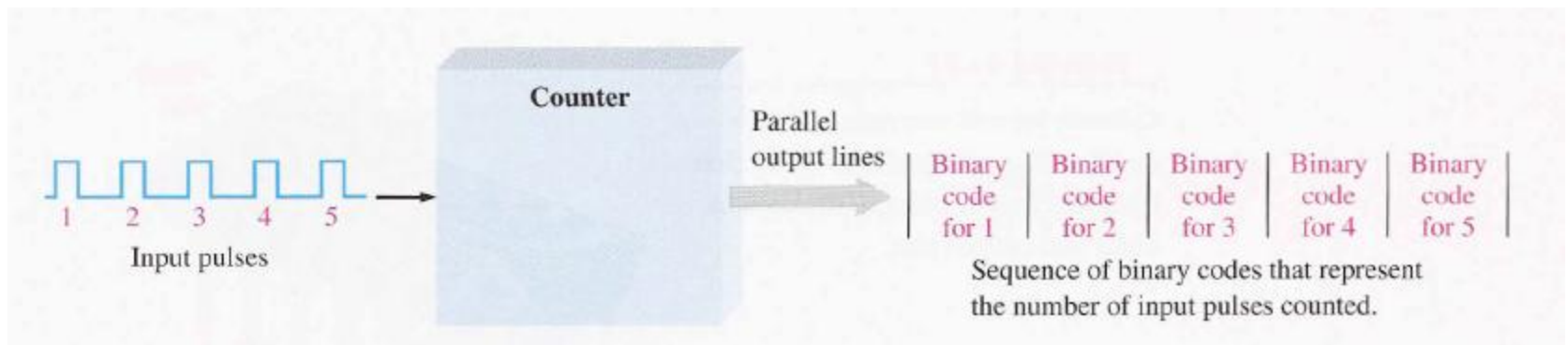

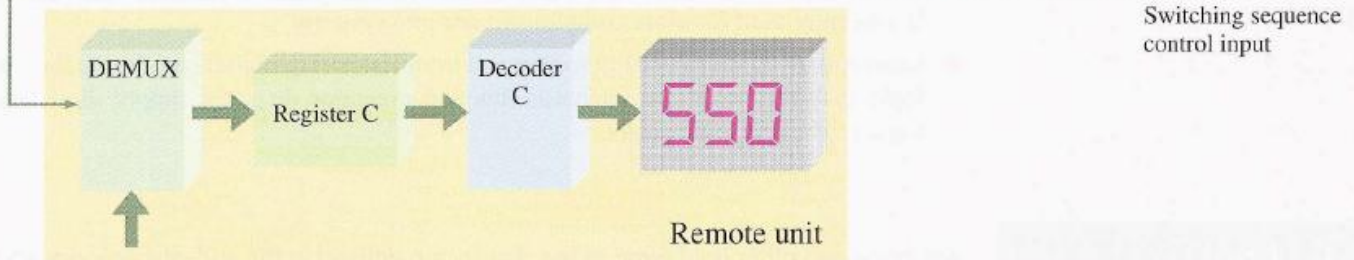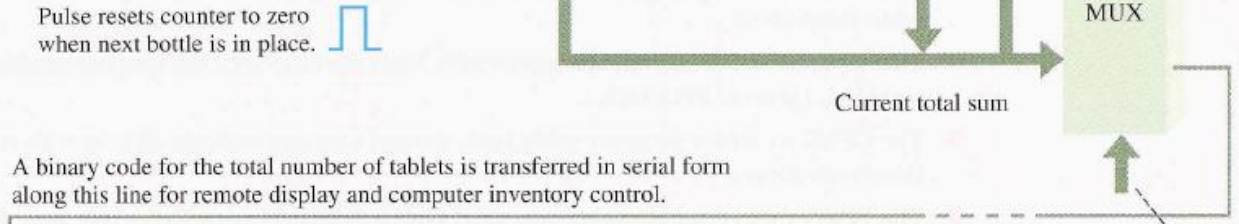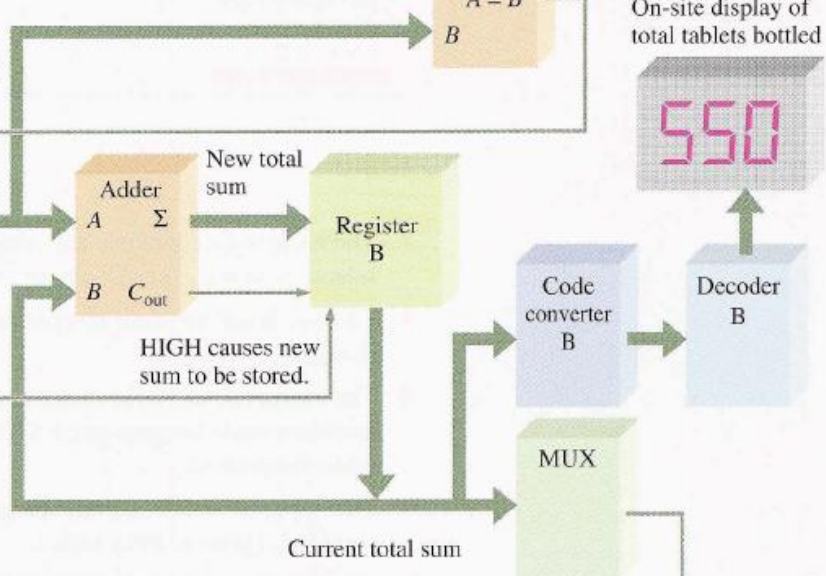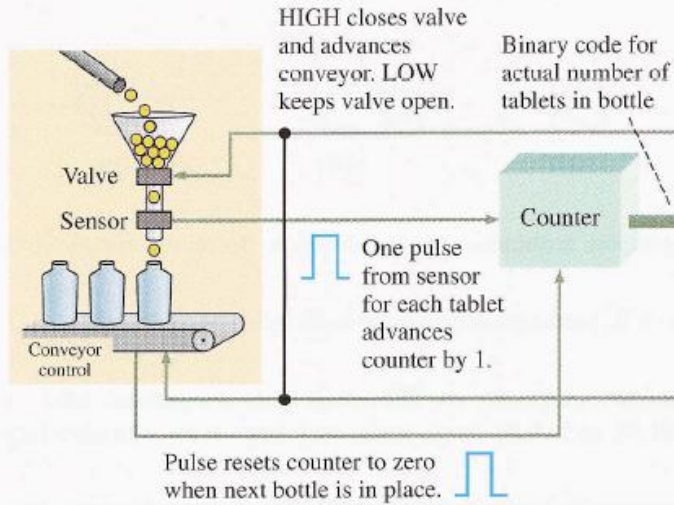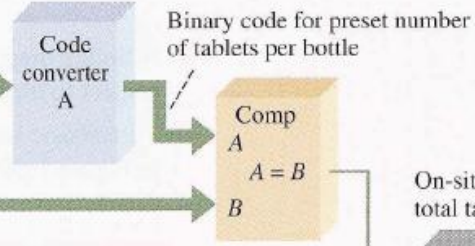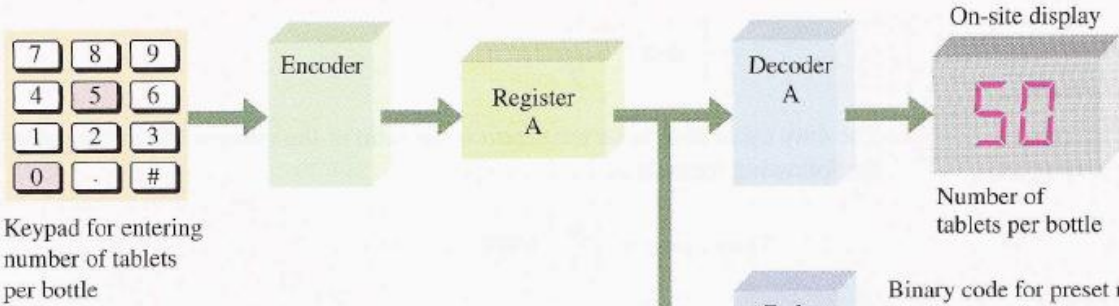


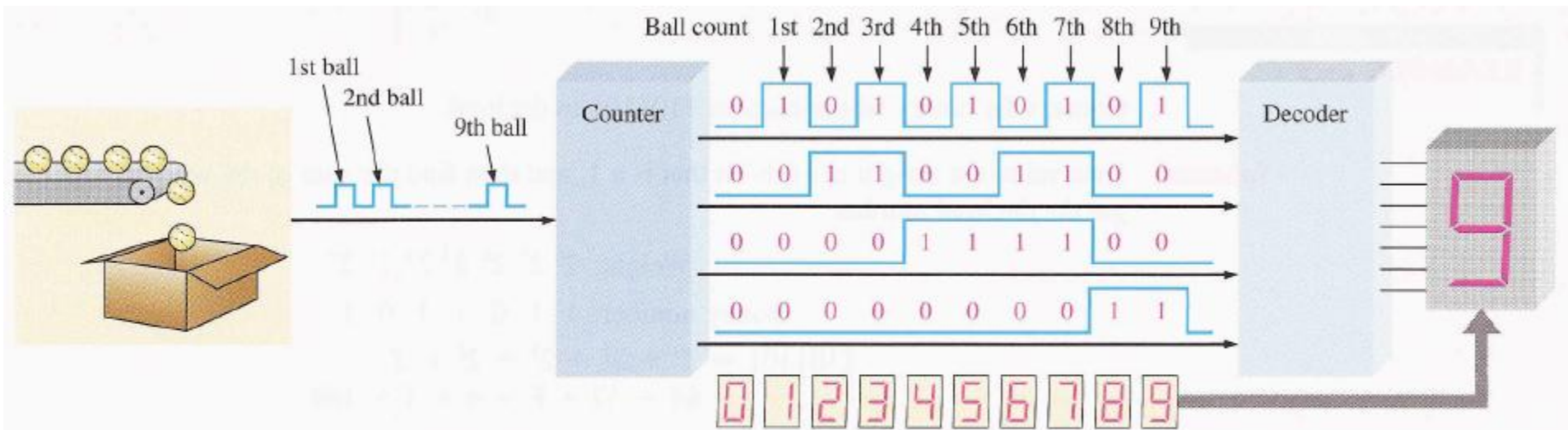


▲ FIGURE 2-1

Illustration of a simple binary counting application.


Demnilnik

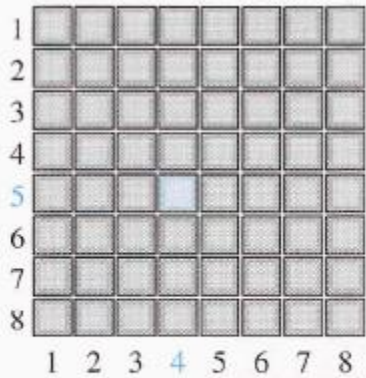


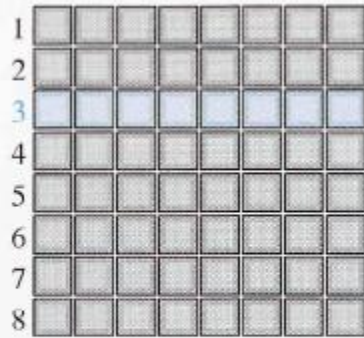
(a) The address of the blue bit is row 5, column 4.




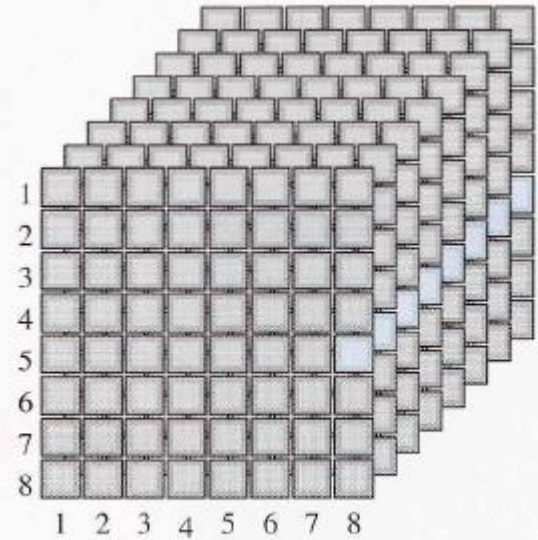(b) The address of the blue byte is row 3.




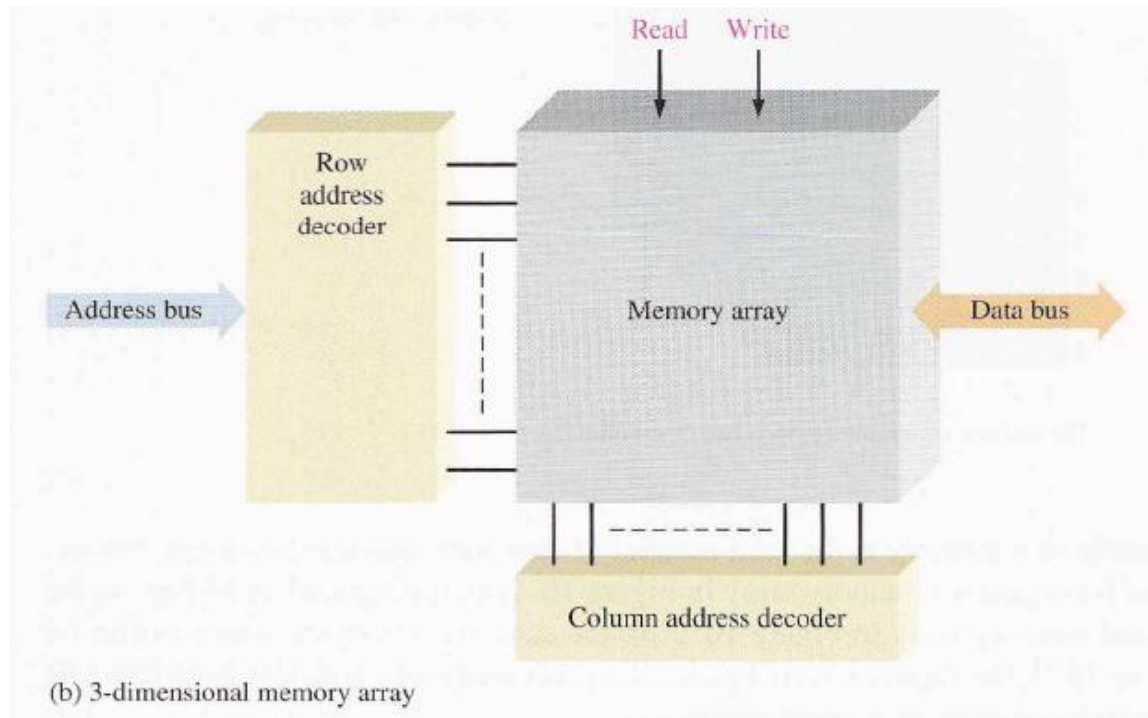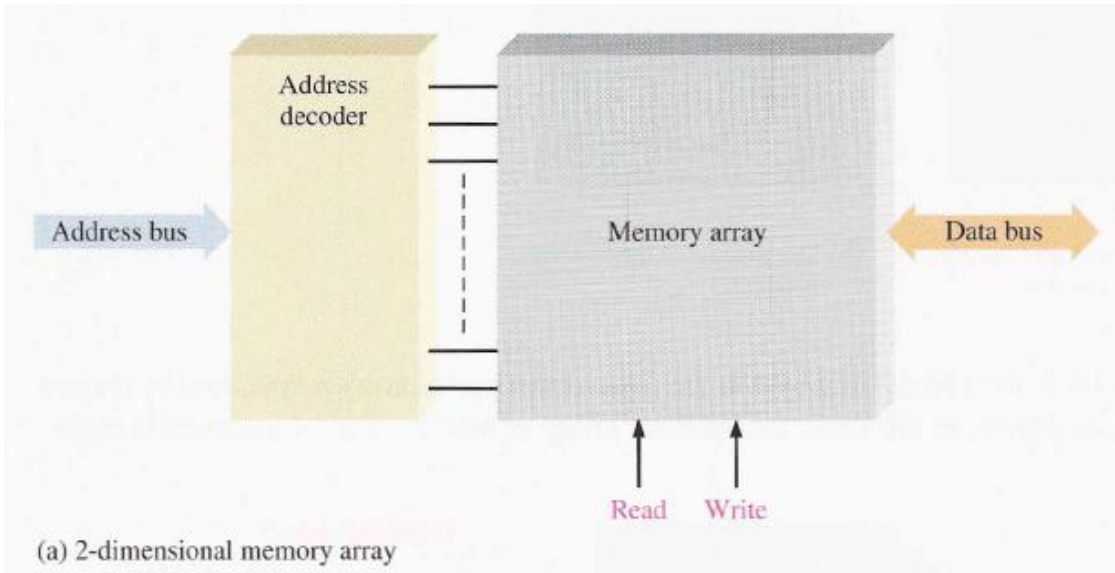The address of the blue byte is row 5, column 8.



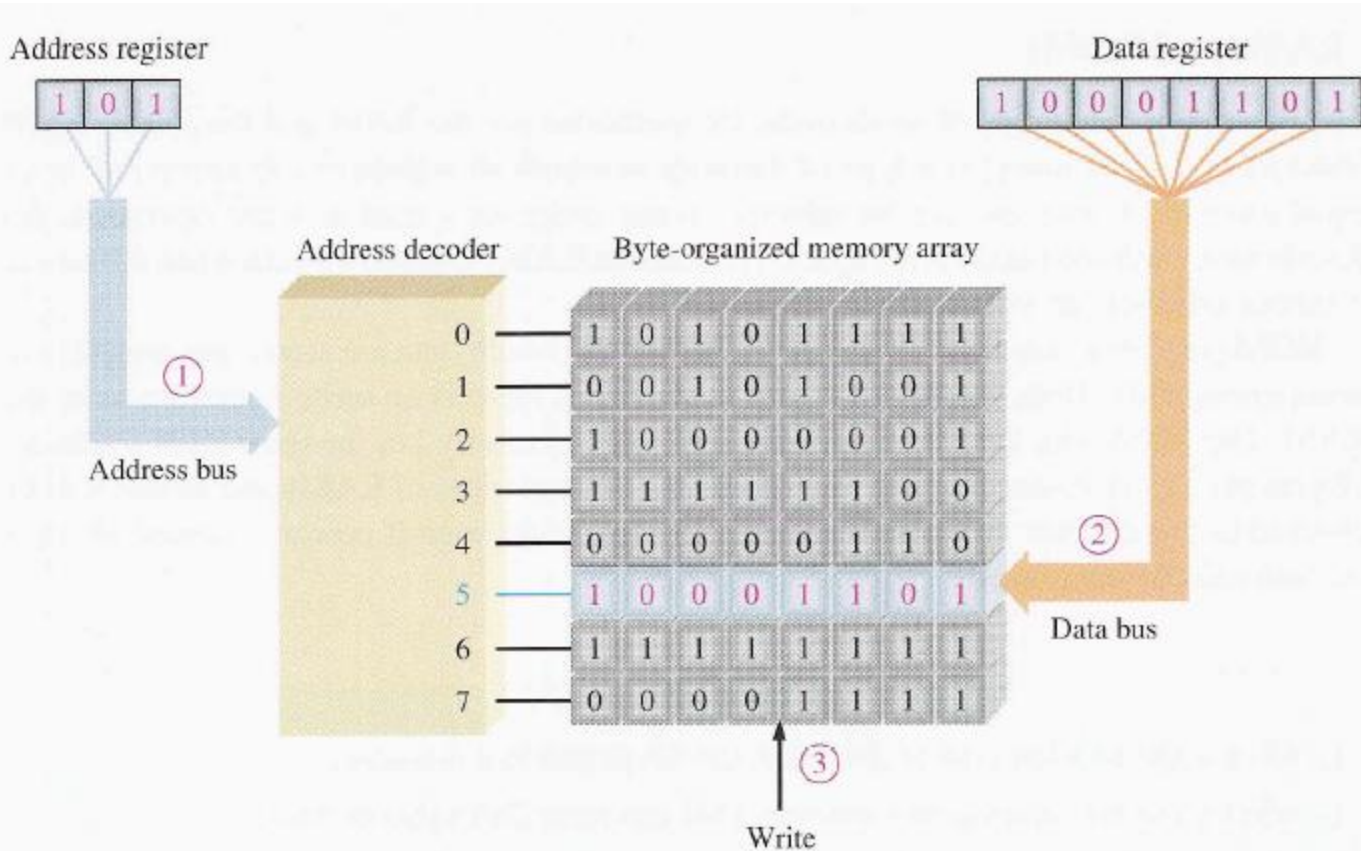


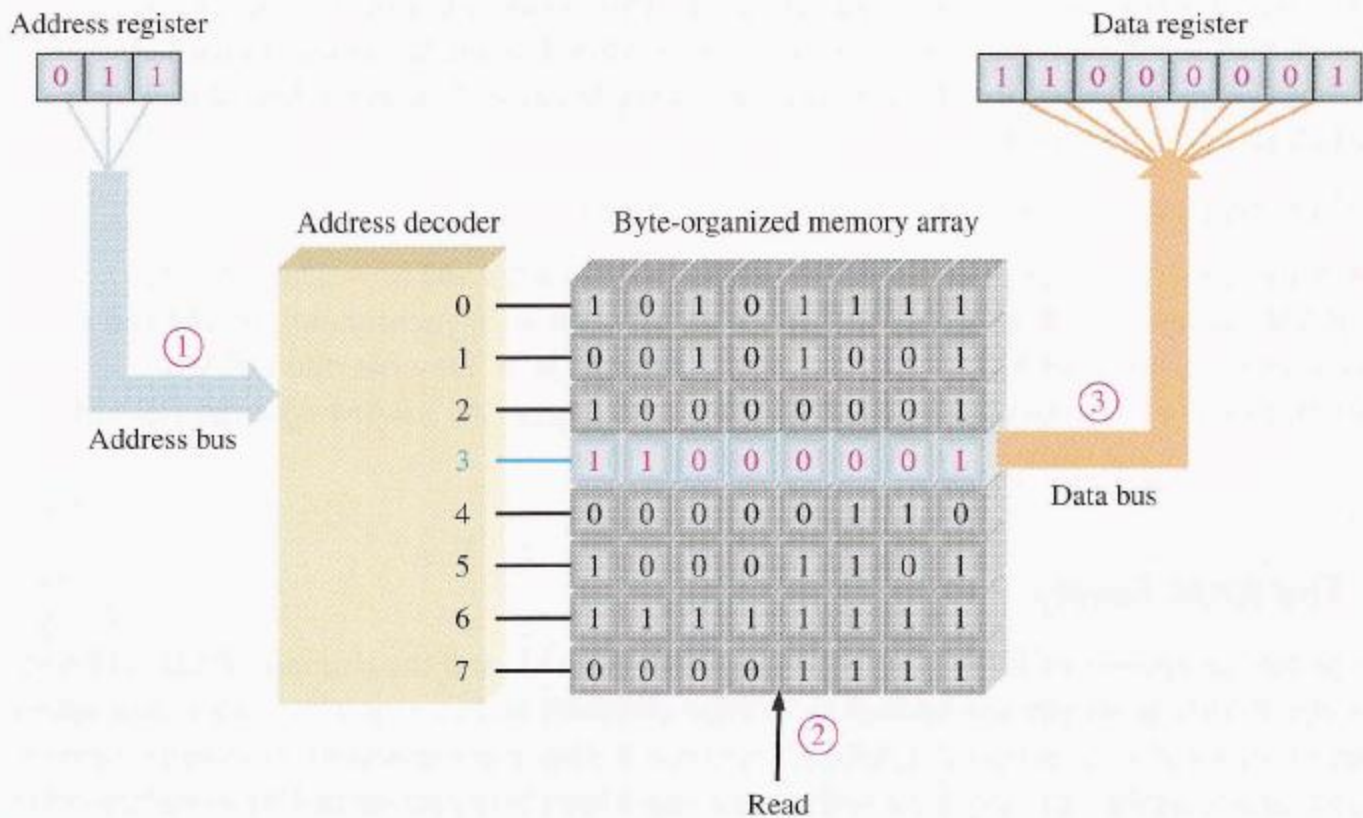
- ① Address code 101 is placed on the address bus and address 5 is selected.
- ② Data byte is placed on the data bus.
- ③ Write command causes the data byte to be stored in address 5, replacing previous data.




- ① Address code 011 is placed on the address bus and address 3 is selected.
- ② Read command is applied.
- ③ The contents of address 3 is placed on the data bus and shifted into data register.
The contents of address 3 is not erased by the read operation.

◀ **FIGURE 10-8**

A typical SRAM latch memory cell.

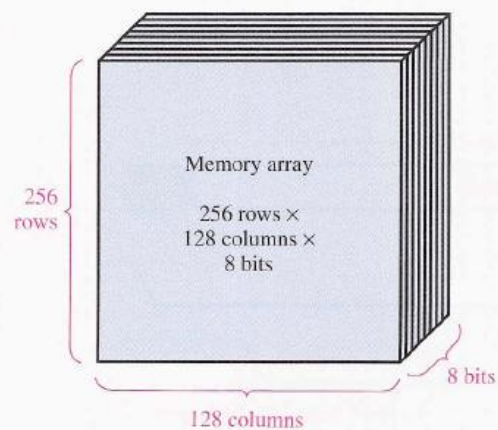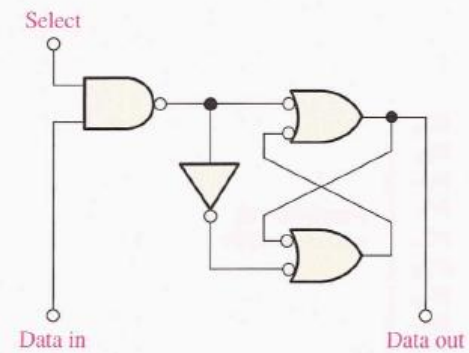

(a) Memory array configuration

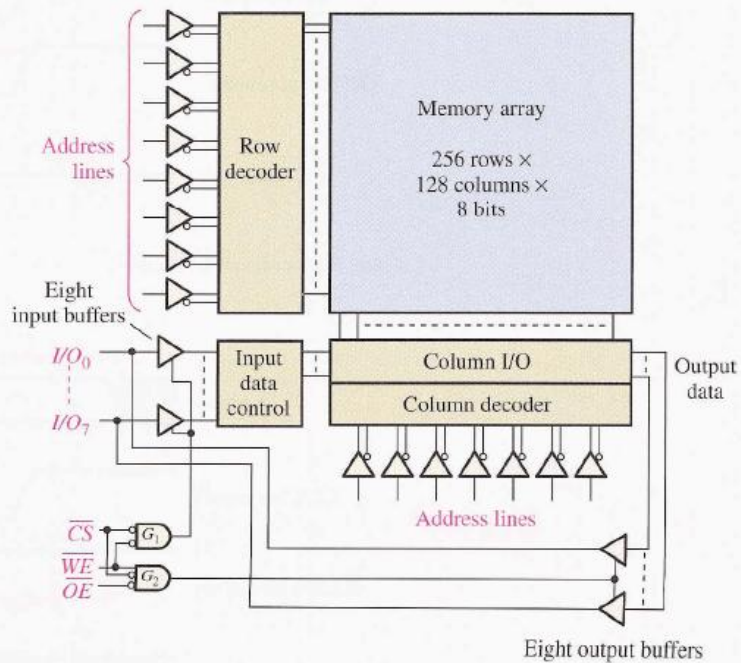


(b) Memory block diagram

▲ **FIGURE 10-11**


Basic organization of an asynchronous 32k x 8 SRAM.

► **FIGURE 10-12**

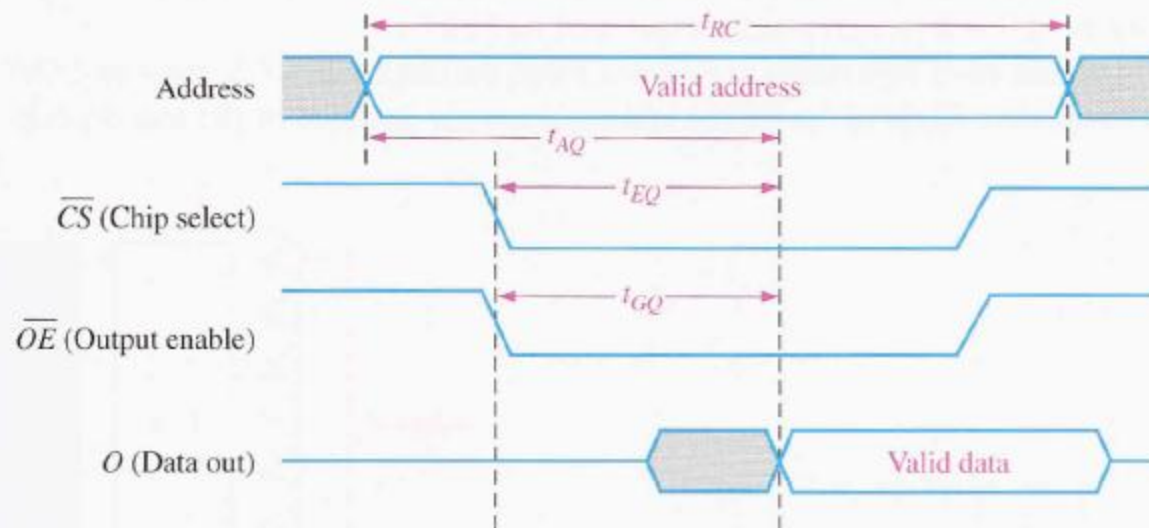Basic read and write cycle timing for the SRAM in Figure 10-11.





(a) Read cycle (\overline{WE} HIGH)

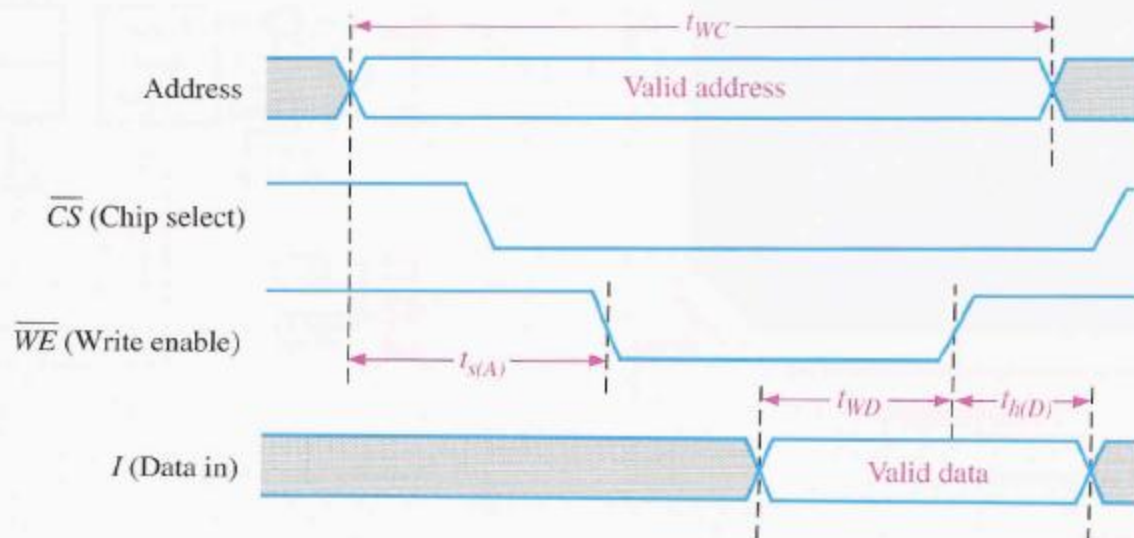

(b) Write cycle (\overline{WE} LOW)

▶ **FIGURE 10-16**

A MOS DRAM cell.

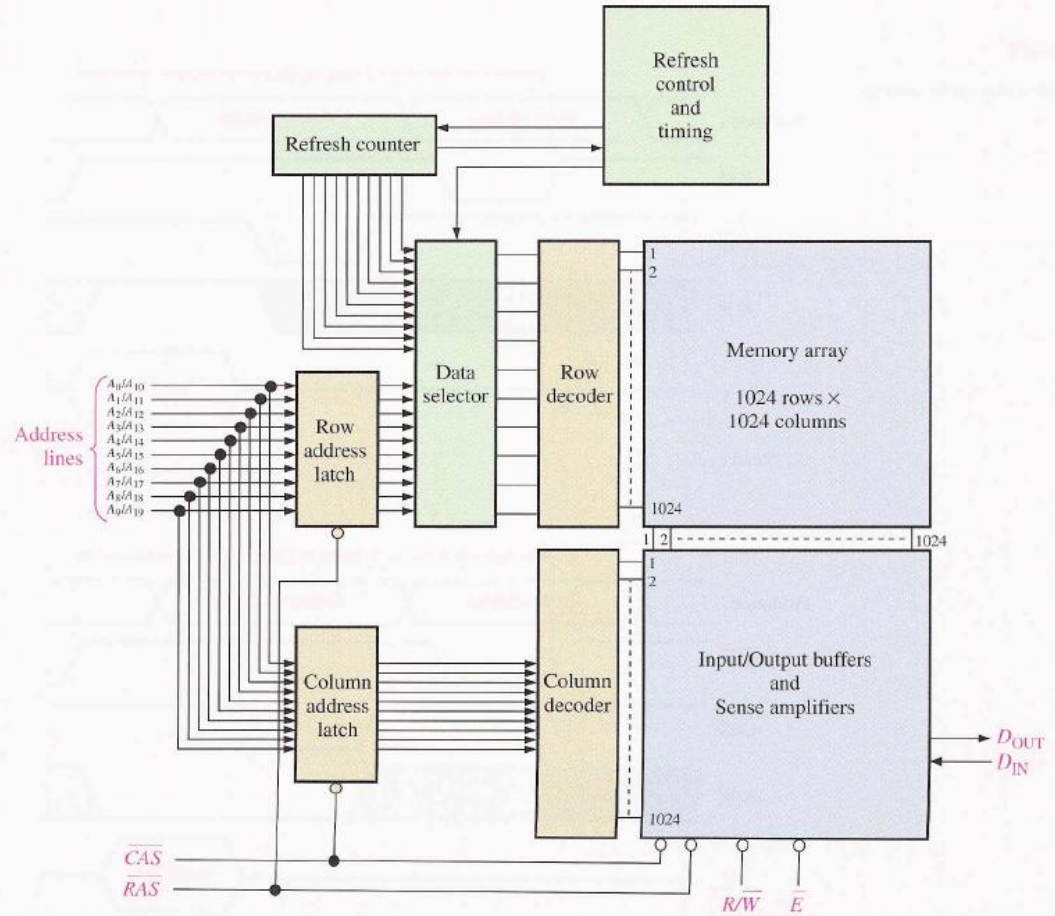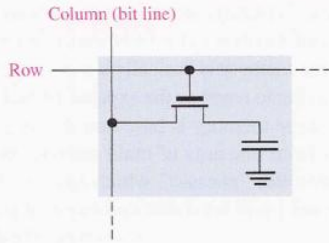


▲ **FIGURE 10-18**


Simplified block diagram of a 1M x 1 DRAM.

► **FIGURE 10-20**

Normal read and write cycle timing.

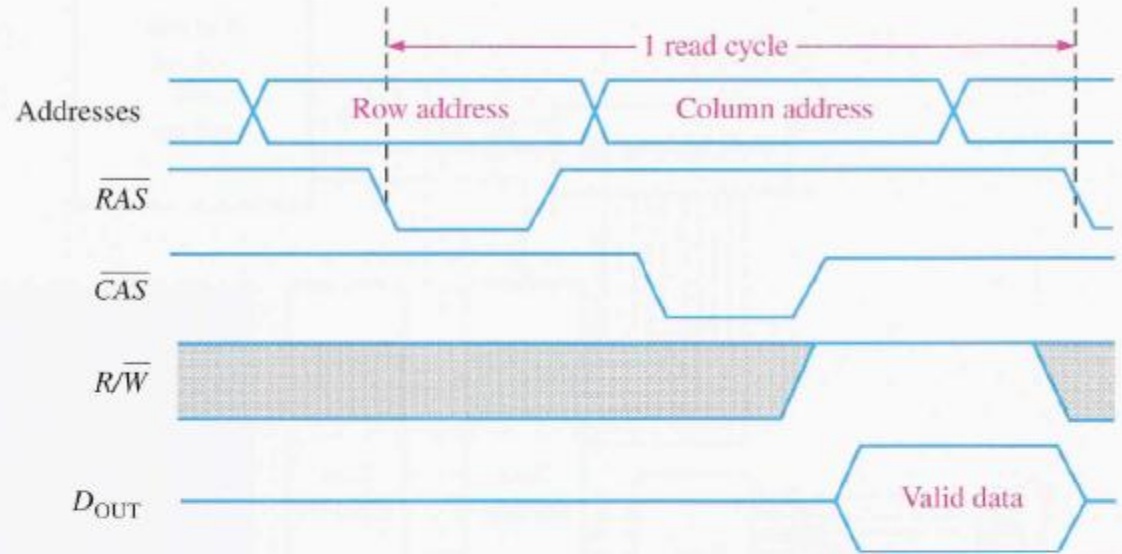

(a) Read cycle

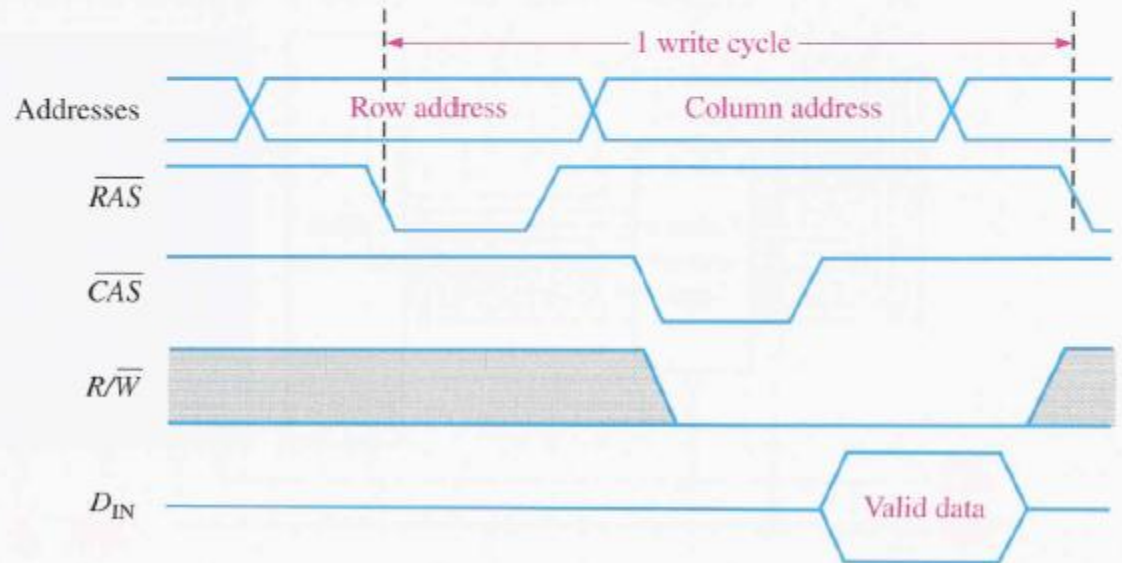


(b) Write cycle

CPE: centralna procesna enota

Podatki in informacije

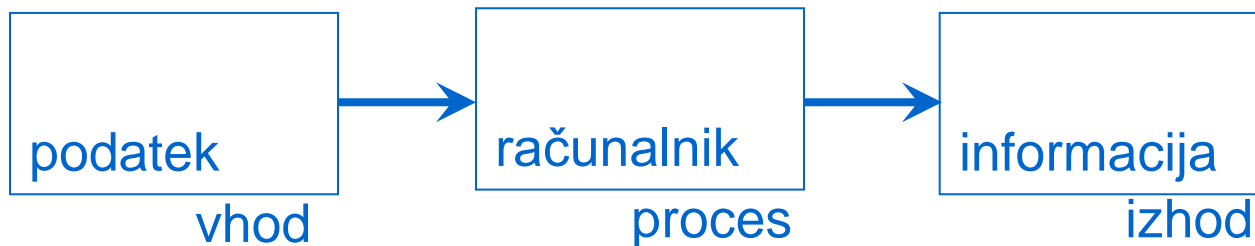- informacija, kot obdelan podatek
- računalnik:
 - komunikacija z zunanjim svetom
 - obdelava podatkov




- Primer: podatek - informacija

Računalnik

- osnovne komponente
 - CPE: centralno procesna enota
 - aritmetično-logična enota
 - nadzorna enota
 - pomnilnik
 - vhodno/izhodne enote
- von Neumannova arhitektura


Arhitektura računalniškega sistema

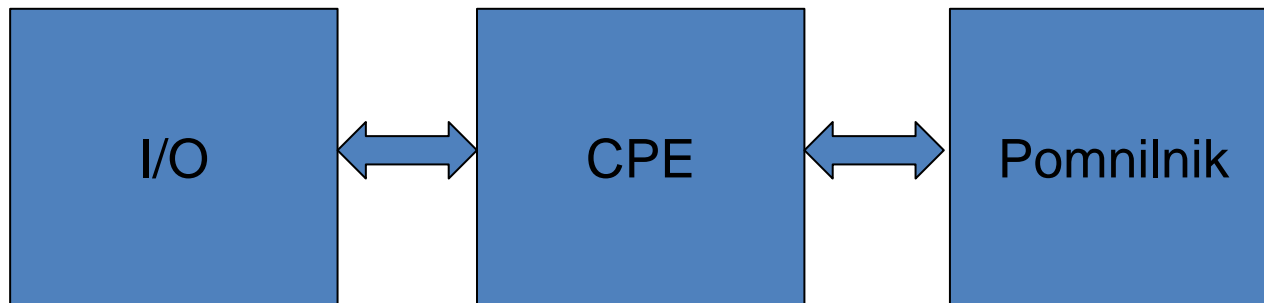- CPE: centralno procesna enota (CPU) - procesor
- Pomnilnik (memory): RAM, ROM, disk, ...
- Vhodno/izhodne enote (I/O): tipkovnica, zaslon, ...



CPE in Pomnilnik

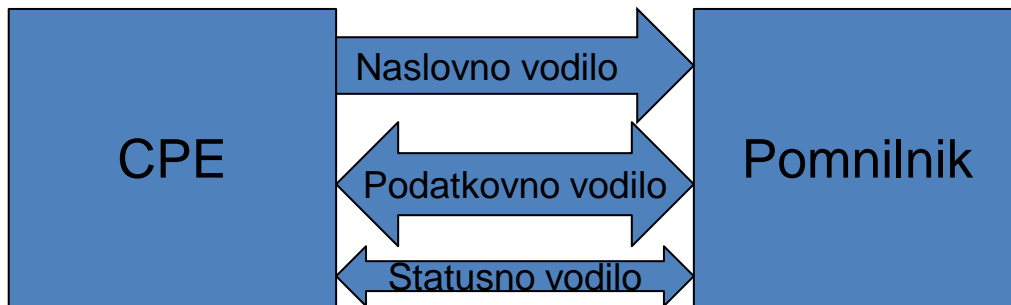- Enota: byte (8 bitov)
- Vsaka lokacija ima svoj naslov
- Daljše besede: uporabimo več zaporednih bajtov (byte)
 - 32 bitna beseda: 4 zaporedni bajti



1 bit


8 bits = 1 byte

1kbyte = 2^{10} = 1024 bytes

1Mbyte = 2^{20} = 1048576 bytes

CPE

Fetch
Decode
Execute
Store

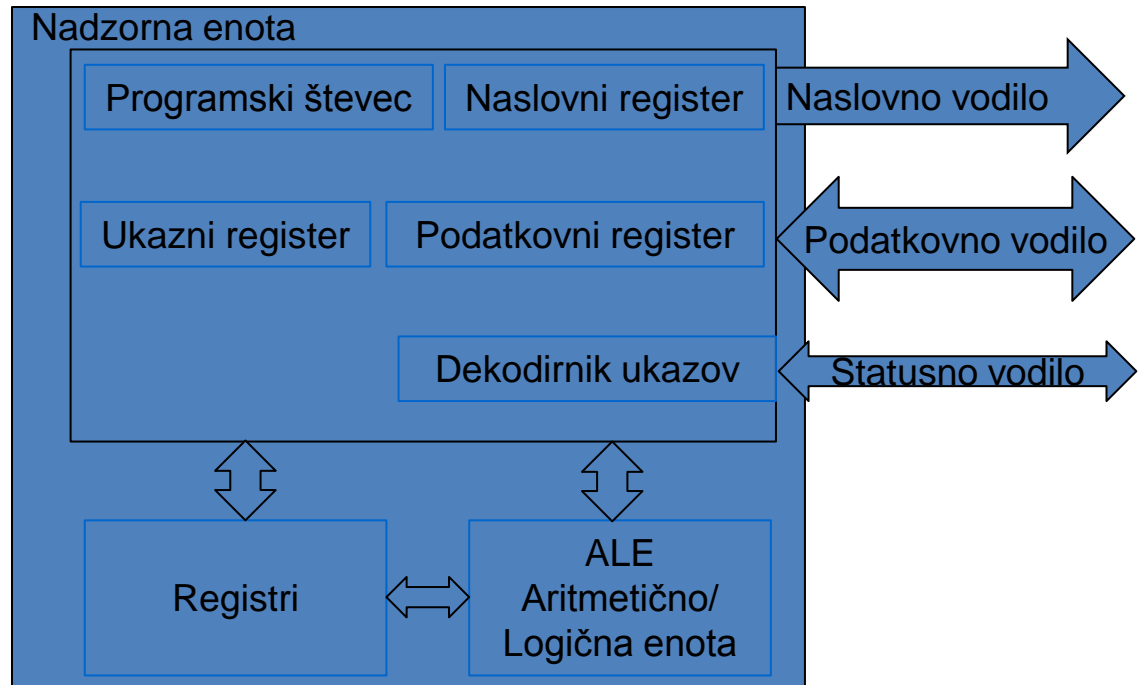


Primer: tekoči trak

Delovanje CPE

- osnovni cikel izvedbe ukaza (von Neumannov model)
 - beri (read)
 - dekodiraj (decode)
 - izvedi (execute)
 - shrani (store)
- strojna koda: ukazi in podatki, ki jih CPE neposredno izvaja
- zbirni jezik: simbolični zapis strojne kode

Mikroprocesor

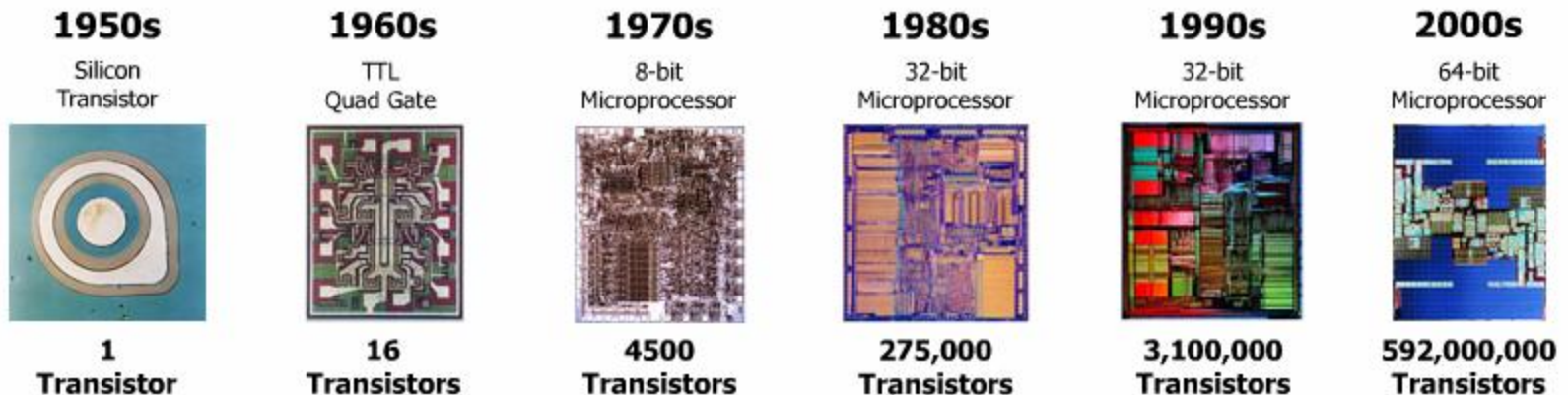- je srce osebnega računalnika
- in mnogih drugih elektronskih naprav: vgrajeni sistemi (embedded systems)
- polprevodniške tehnologije (CMOS)
- tranzistor kot osnovni gradnik (stikalo)
- Primeri rabe mikroprocesorjev: mobilni telefon
<http://www.computerhistory.org/>





Programiranje 1


- Strojni jezik
- Zbirni jezik (assembler) – simbolični strojni jezik
- Primer


<u>zbirnik</u>	<u>strojna koda (binarni zapis)</u>
mov a, #1	01110100 00000001
mov r1, #1	01111000 00000001
add a, r1	00101000

Intel 4004 in Pentium 4

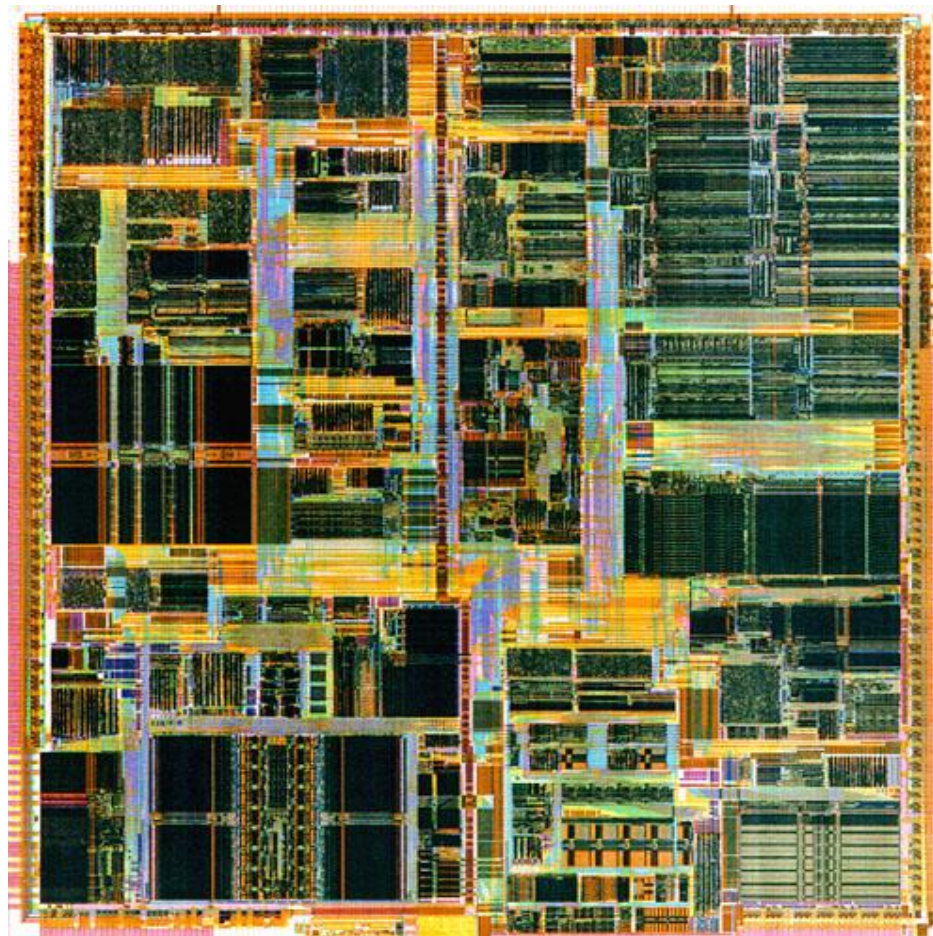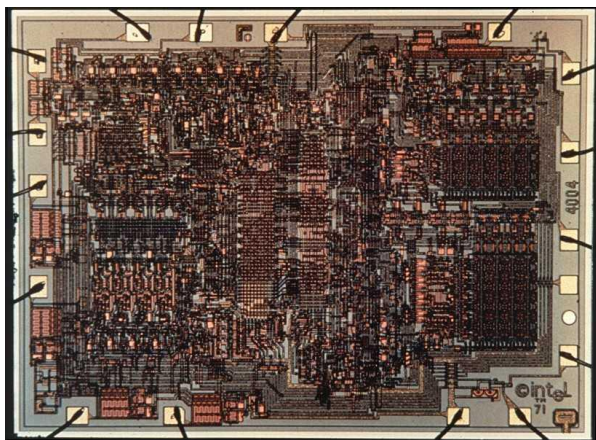


Digitalni sistemi v telekomunikacijah


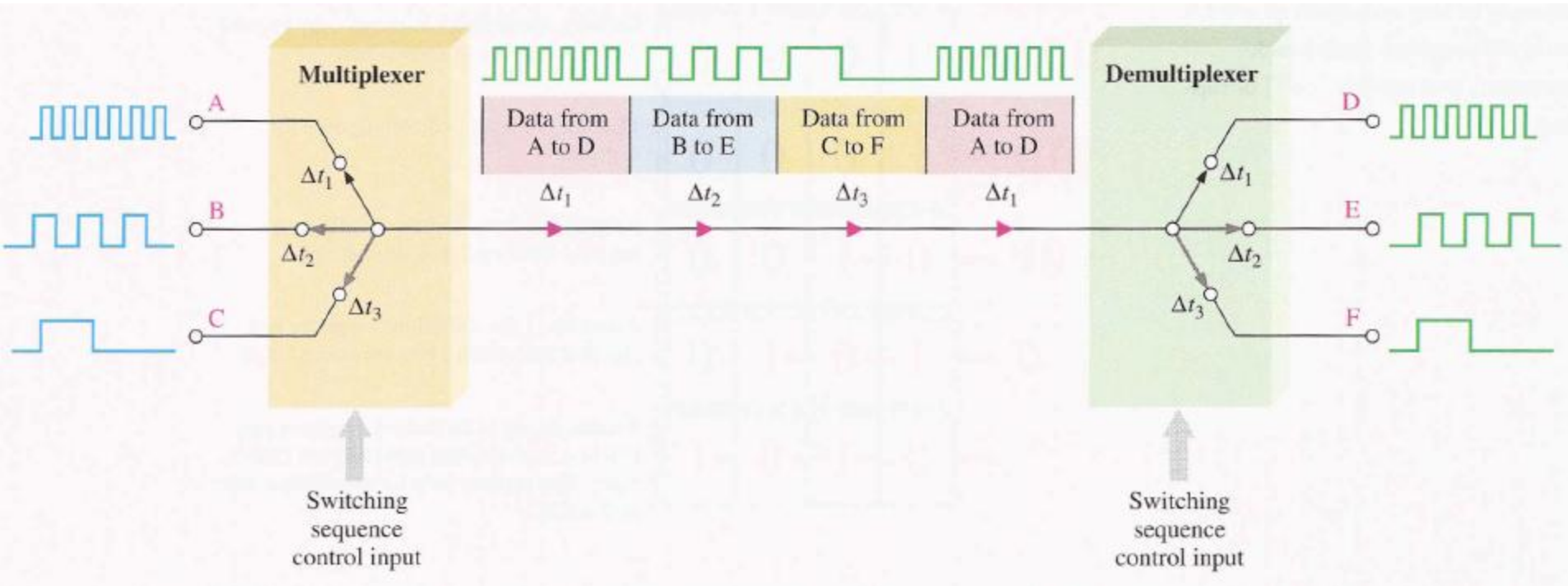


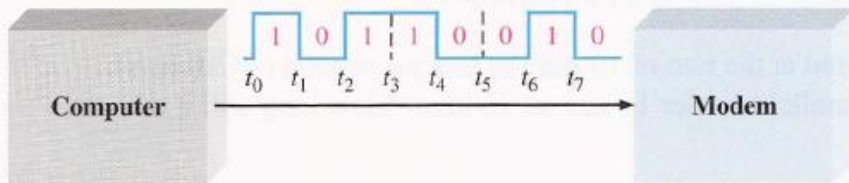


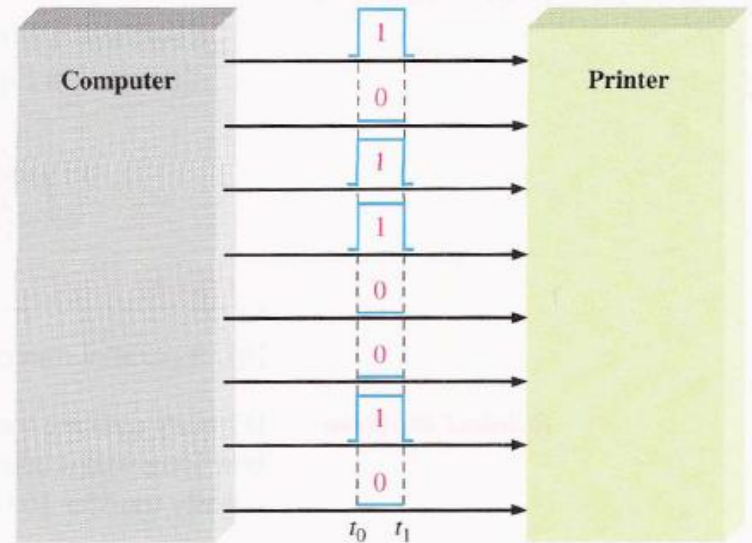(a) Serial transfer of 8 bits of binary data from computer to modem. Interval t_0 to t_1 is first.



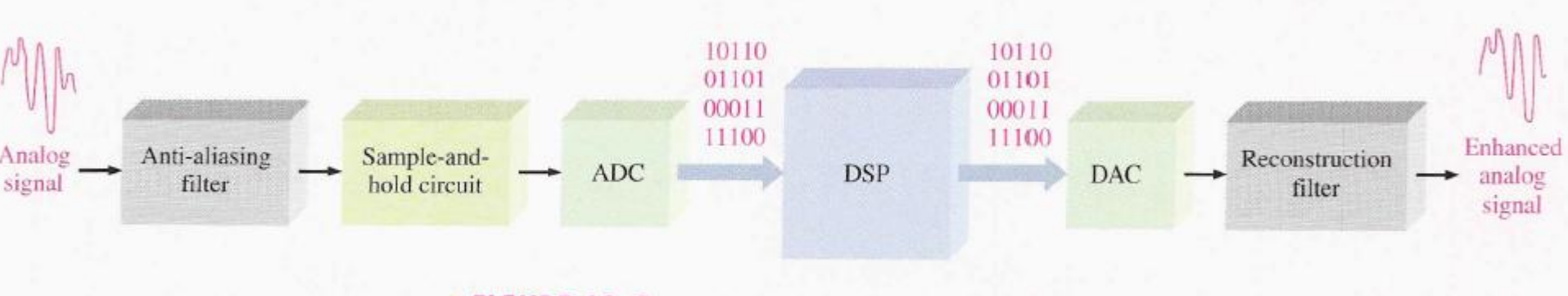
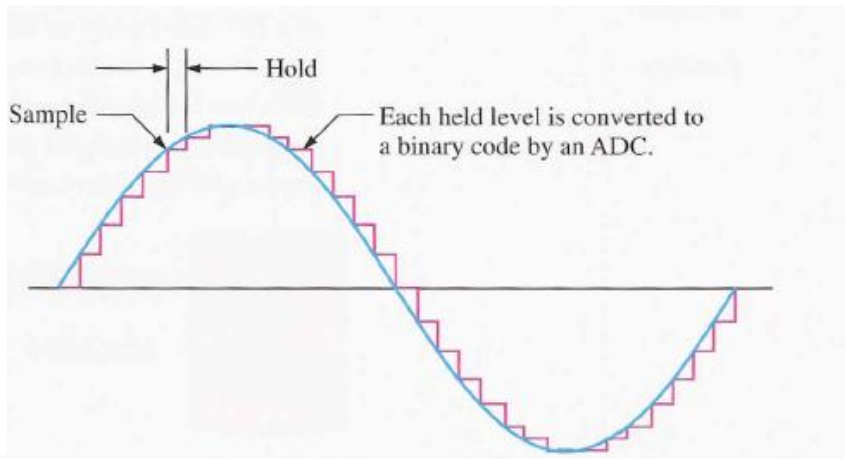
(b) Parallel transfer of 8 bits of binary data from computer to printer. The beginning time is t_0 .



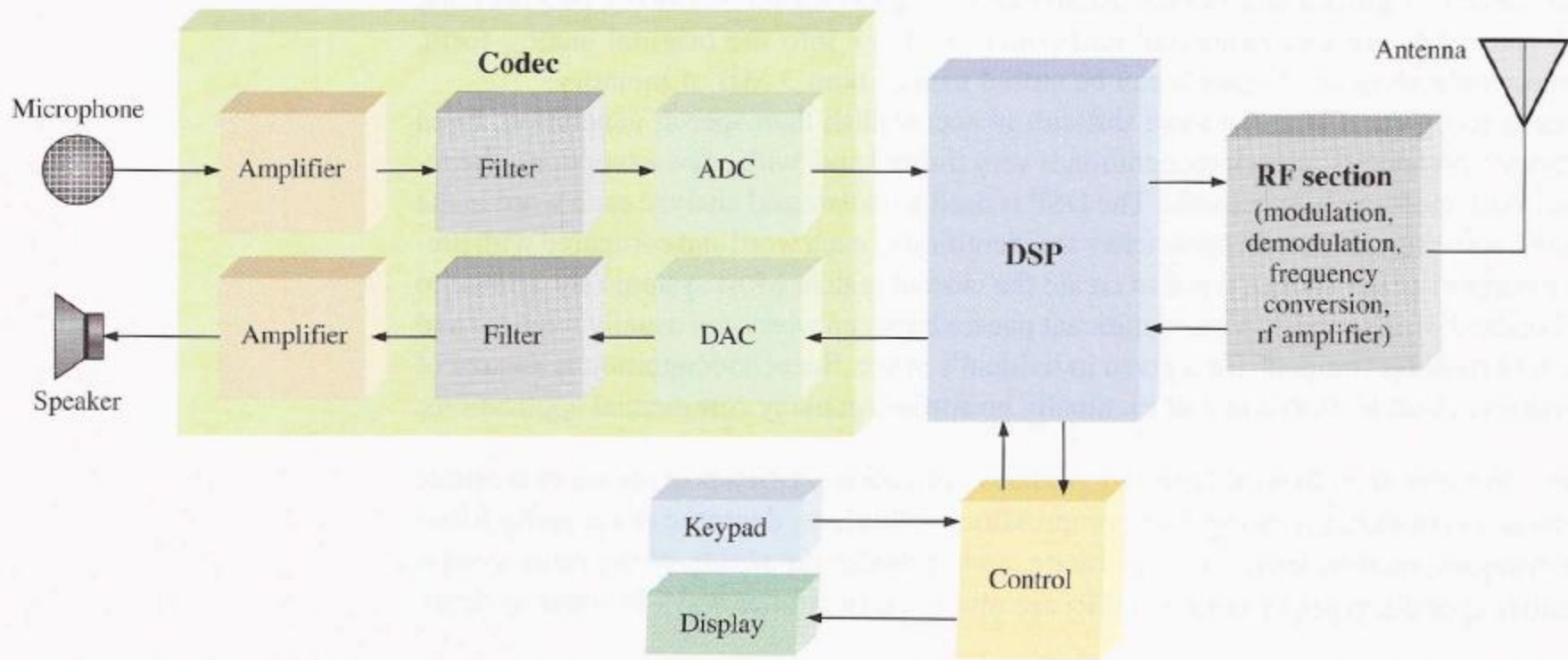

▲ **FIGURE 13-29**

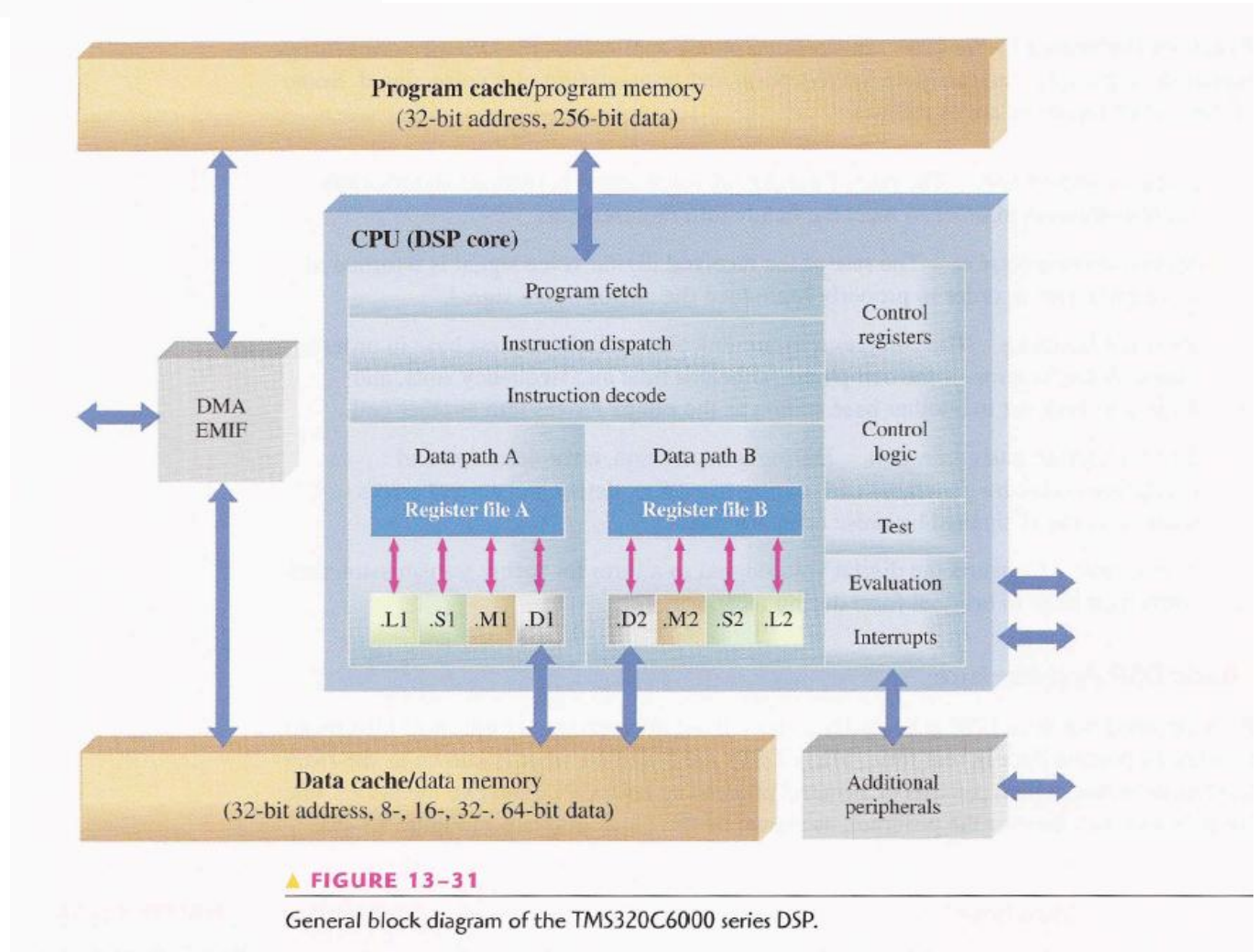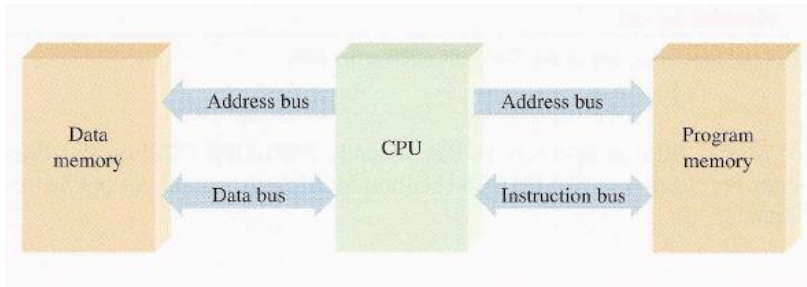Simplified block diagram of a digital cellular phone.



▲ **FIGURE 13-31**

General block diagram of the TMS320C6000 series DSP.