

$$R_T = \frac{(6.8 \text{ k}\Omega)(15 \text{ k}\Omega)}{(6.8 \text{ k}\Omega + 15 \text{ k}\Omega)} = 4.68 \text{ k}\Omega$$

and

$$I_C = \frac{10 \text{ V} - 0.7 \text{ V} - 6.88 \text{ V}}{680 + (4.68 \text{ k}\Omega/150)} = 3.4 \text{ mA} \quad \text{using equation 5.16}$$


The collector-emitter voltage is obtained by applying KVL to the collector-emitter branch of the circuit. Then:

$$V_{CE} = 10 \text{ V} - (3.4 \text{ mA})(680 \text{ }\Omega + 1.8 \text{ k}\Omega) = 1.56 \text{ V}$$

► PROBLEMS


5.1 For the base-bias circuit shown assume that $\beta = 150$ and $V_{BE} = 0.7 \text{ V}$ and determine I_C and V_{CE} .

[3.6 mA, 5.5 V]

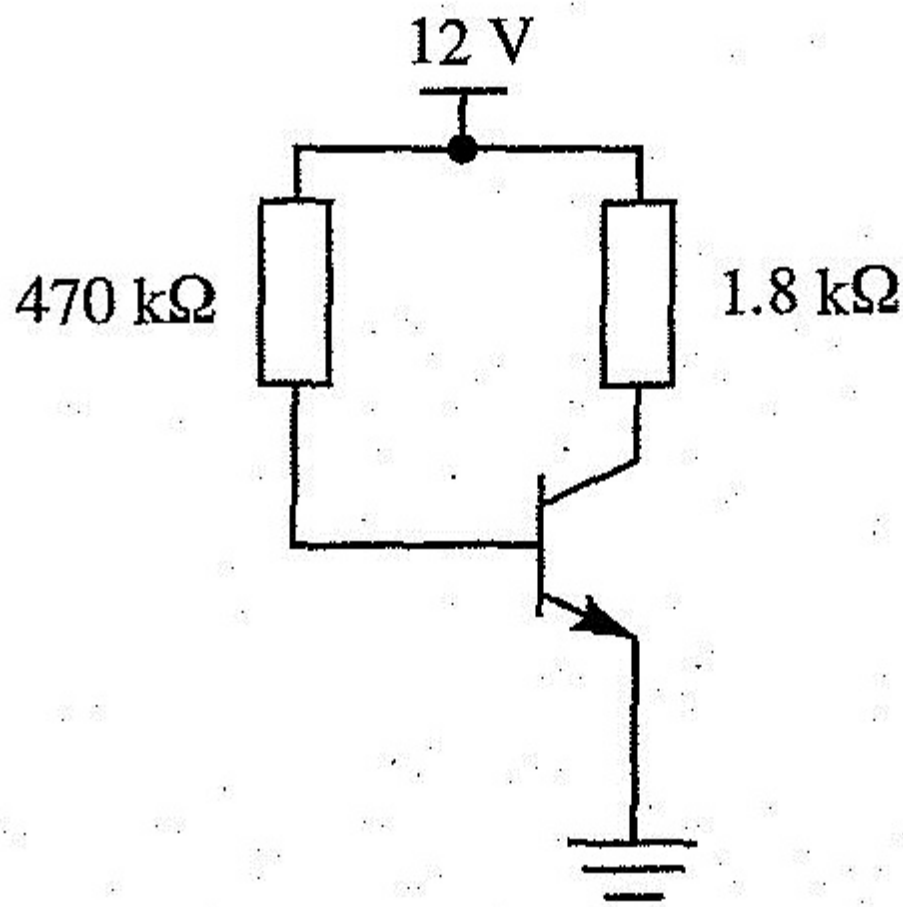

5.4 Determine a suitable value for R_B to provide a V_{CE} of 5 V for the circuit shown if $\beta = 180$ and $V_{BE} = 0.7 \text{ V}$.


[560 kΩ]

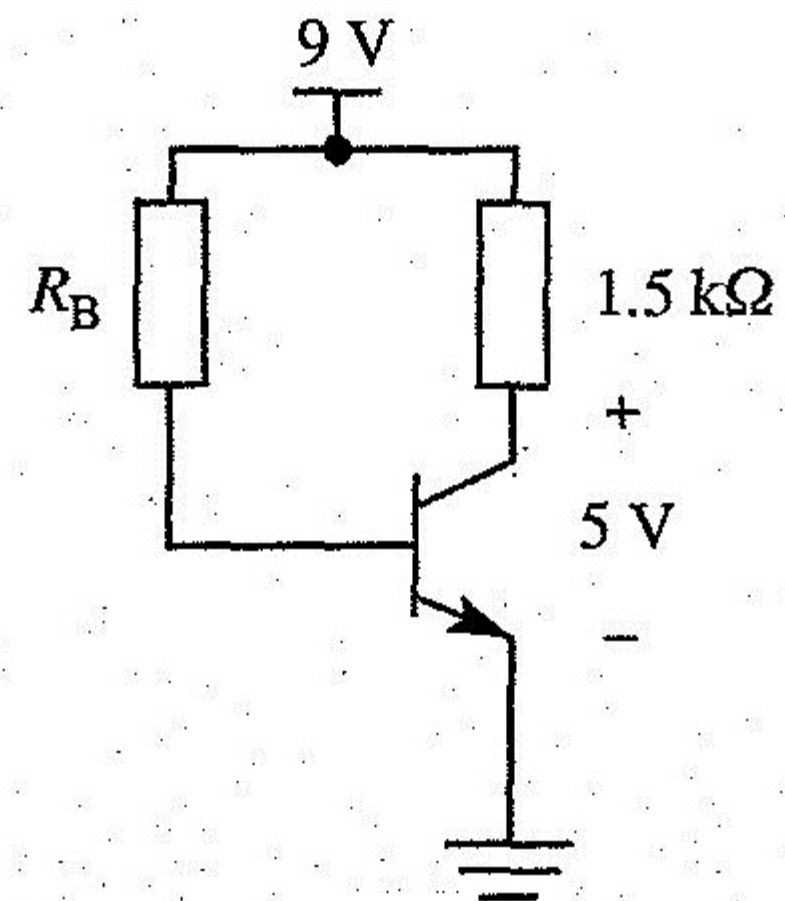

5.2 Repeat Problem 5.1 for $\beta = 350$ and comment on the result.


5.3 Determine I_C and V_{CE} for the circuit shown if $\beta = 120$ and $V_{BE} = 0.7 \text{ V}$.

[2.2 mA, 3.47 V]

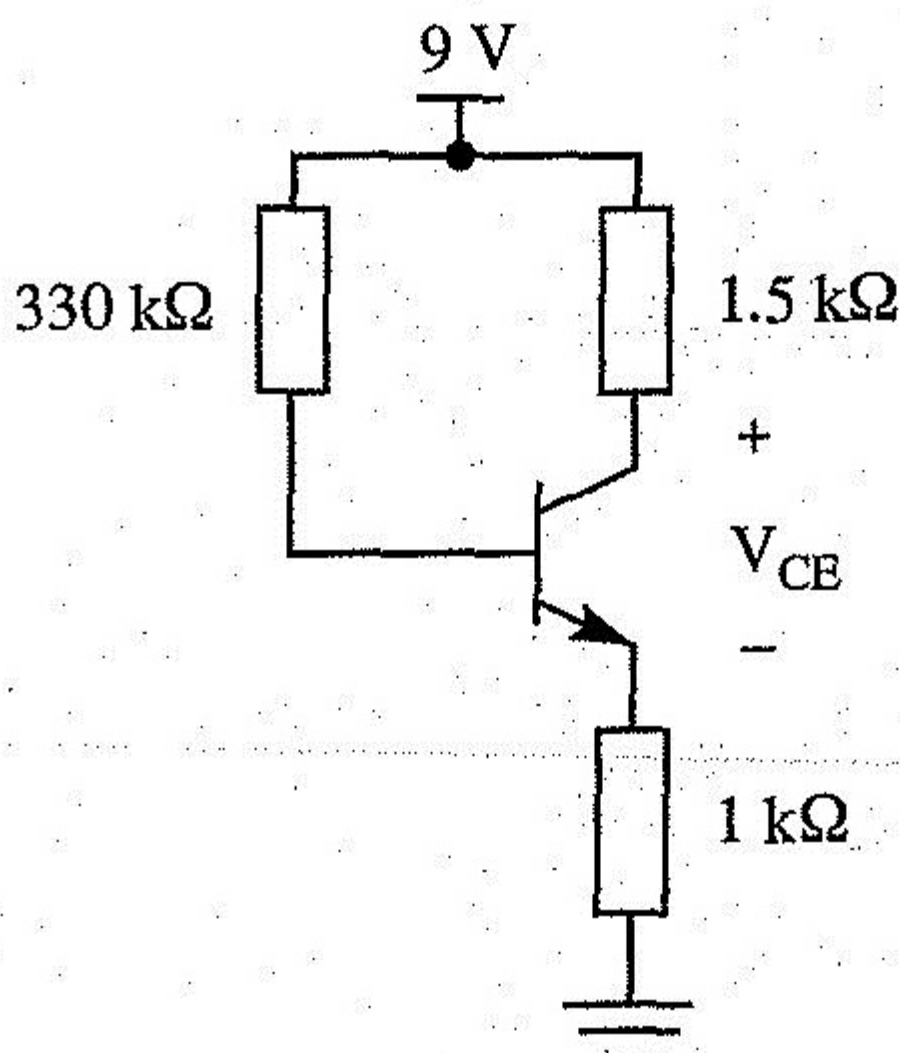


5.5 Determine I_C and V_{CE} for the circuit shown if $\beta = 200$ and $V_{BE} = 0.7 \text{ V}$.

[6.4 mA, 3.4 V]

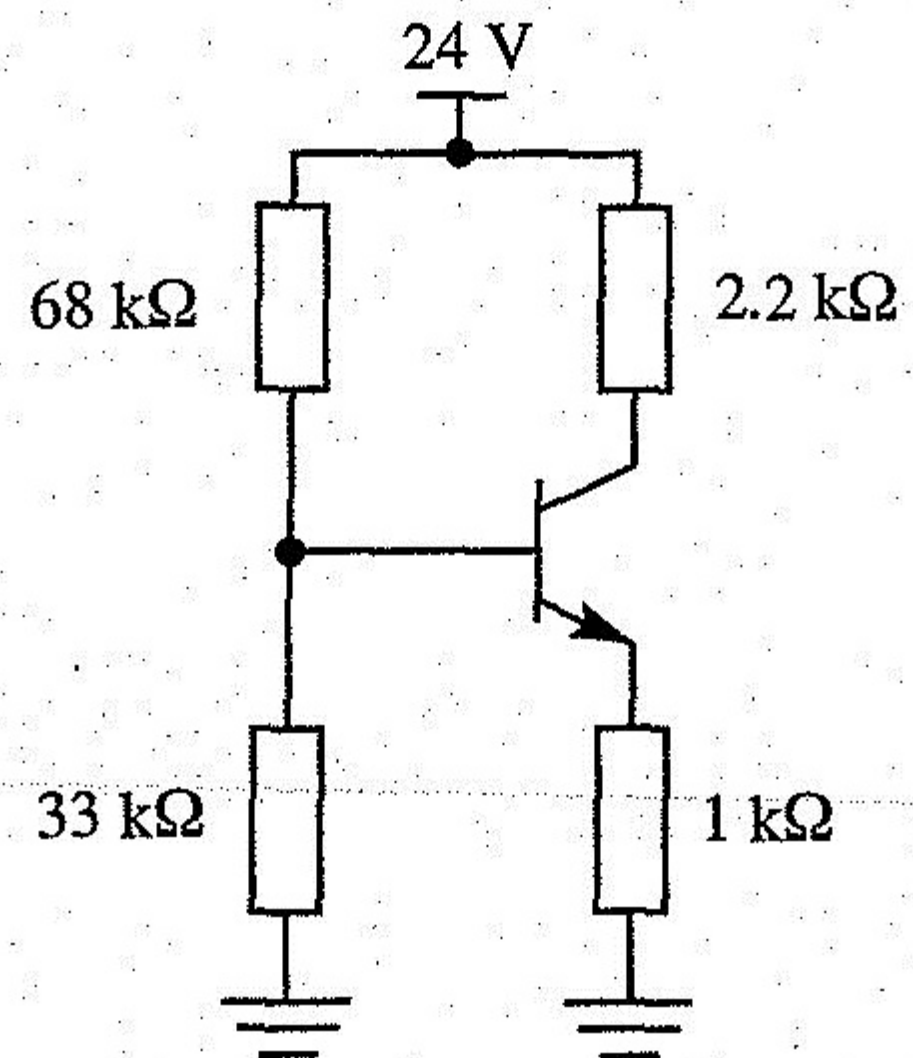


5.6 Determine the value of R_C to ensure that $V_{CE} \geq 3$ V if β varies from 80 to 240. Assume that $V_{BE} = 0.7$ V.

[1.65 k Ω]

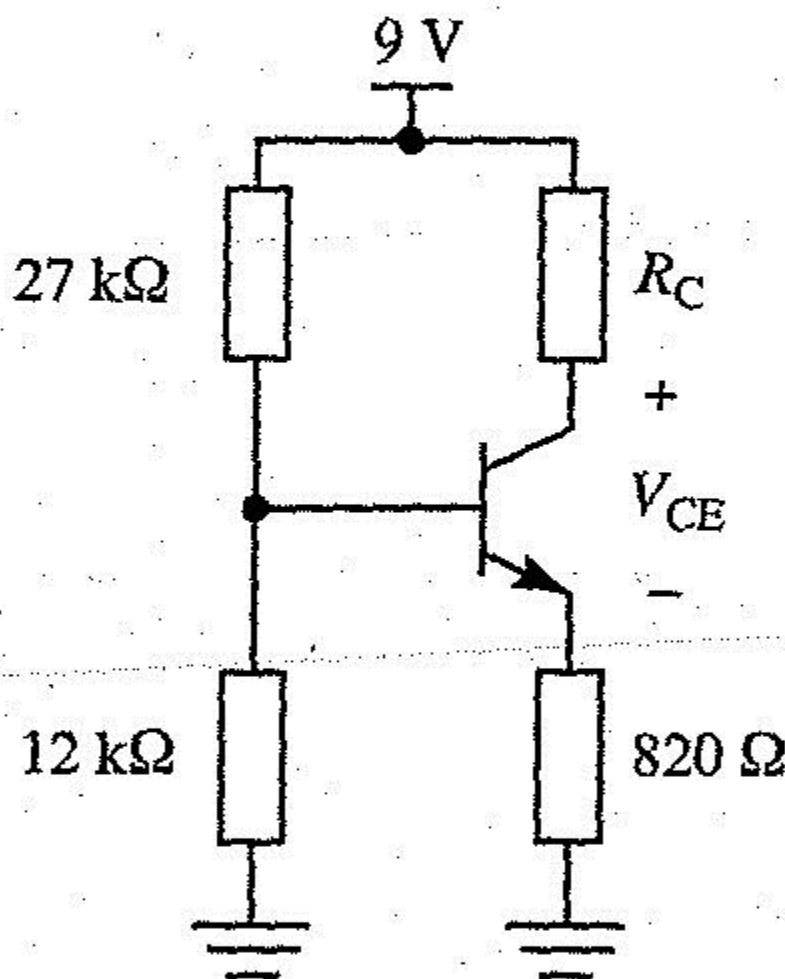


5.9 For the circuit shown $\beta = 120$ and $V_{BE} = 0.7$ V. Verify that the collector current is 1.1 mA and determine the value of R_E which is required to provide a collector current of 2 mA.

[500 Ω]

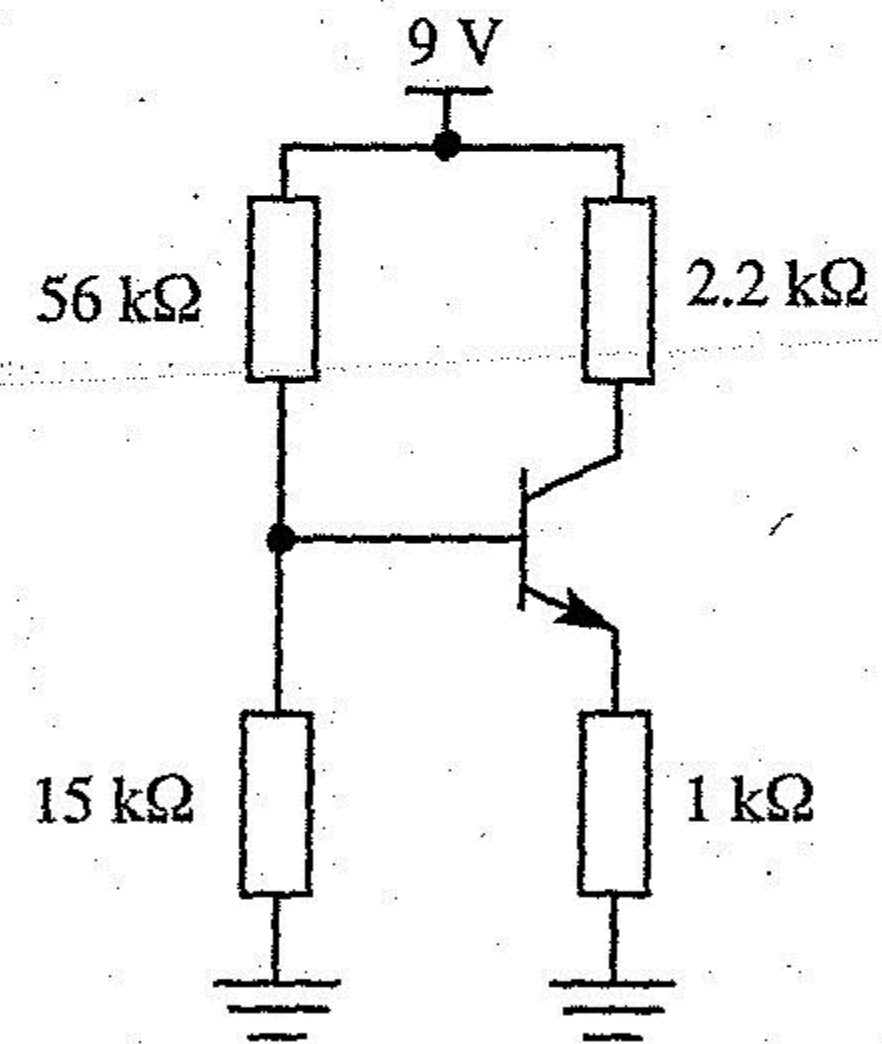

5.7 Determine the change in V_{CE} if β varies from 120 to 420. Assume that $V_{BE} = 0.7$ V.

[4.72 V to 3.76 V]

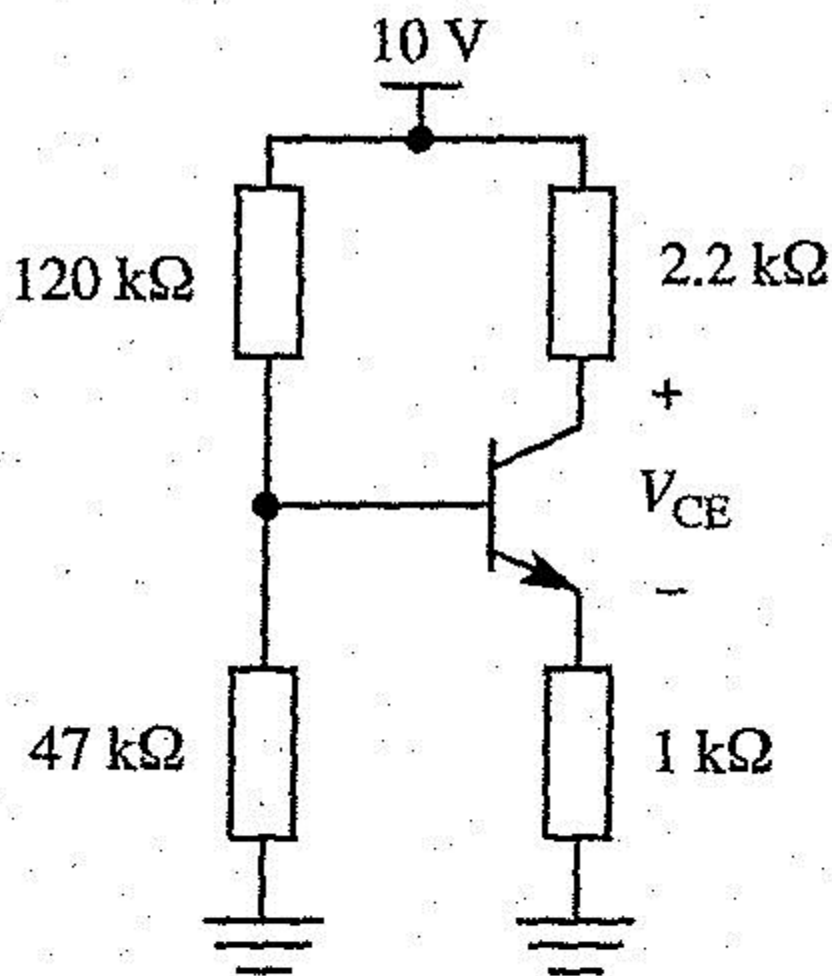


5.10 Design a base potential divider bias circuit to provide a collector current of 3 mA from a supply of 12 V for an npn transistor where the minimum and maximum values of β are specified as 120 and 320 respectively. Determine values for R_1 , R_2 , R_E and R_C .

[30.3 k Ω , 5.7 k Ω , 400 Ω , 1.6 k Ω]


5.8 Select a suitable value for R_E to provide a collector current of 2 mA if $\beta = 150$ and $V_{BE} = 0.7$ V.

[1018 Ω]

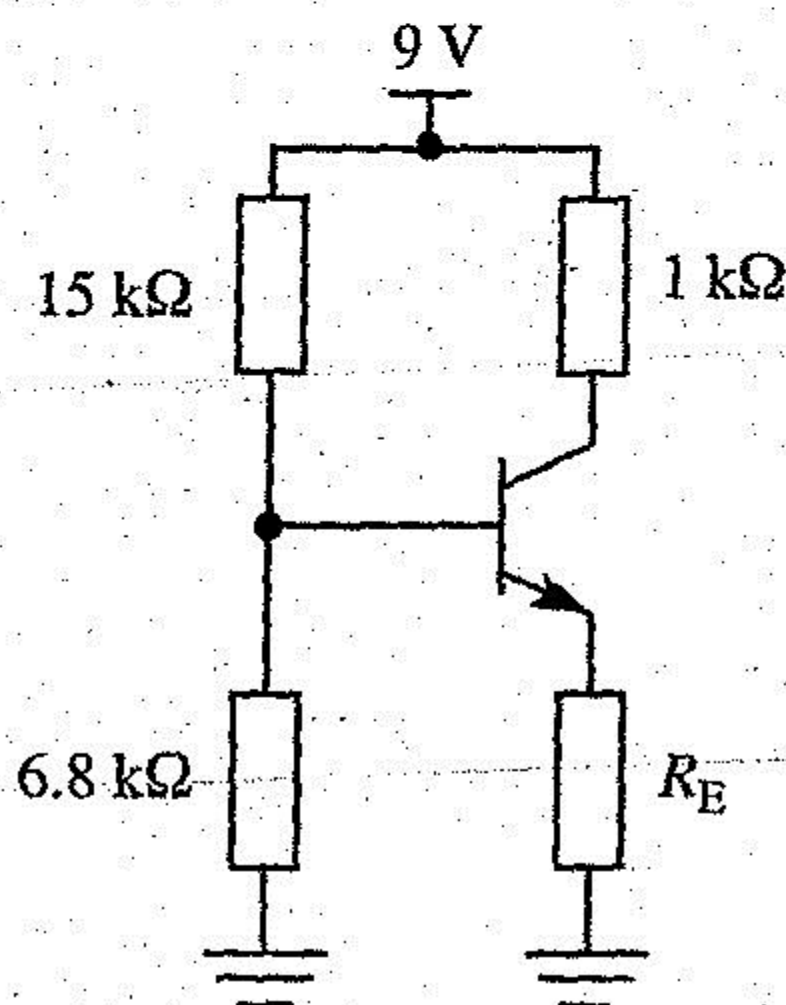


5.11 Determine I_C and V_{CE} if $\beta = 200$ and $V_{BE} = 0.7$ V for the collector-bias circuit shown.

[2.64 mA, 6.4 V]

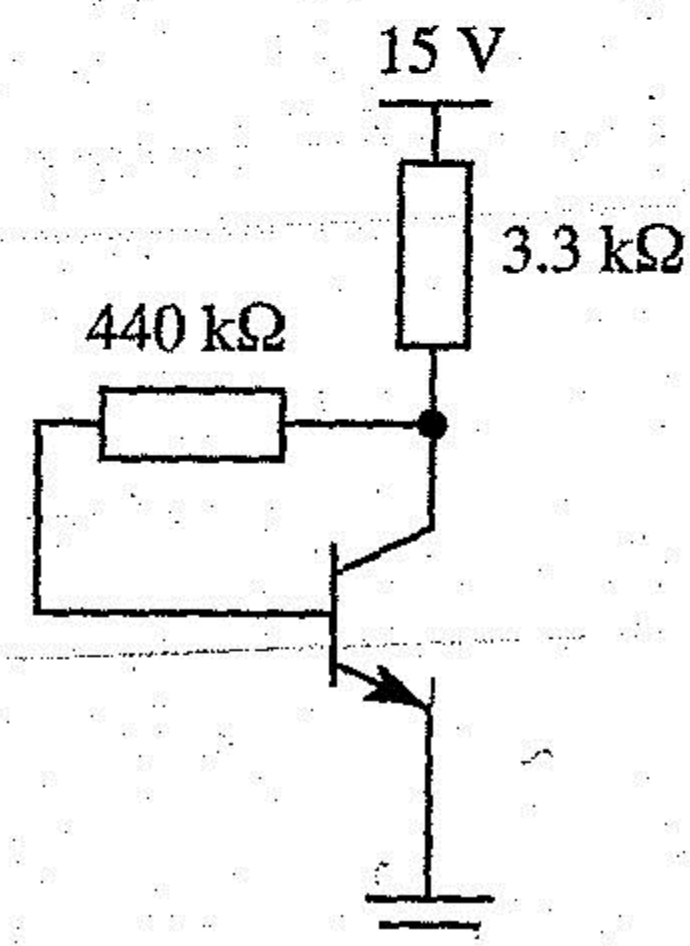


5.12 For the circuit shown determine V_{CE} for $\beta = 120$ and 350 if $V_{BE} = 0.7$ V.

[6.35 V, 3.6 V]

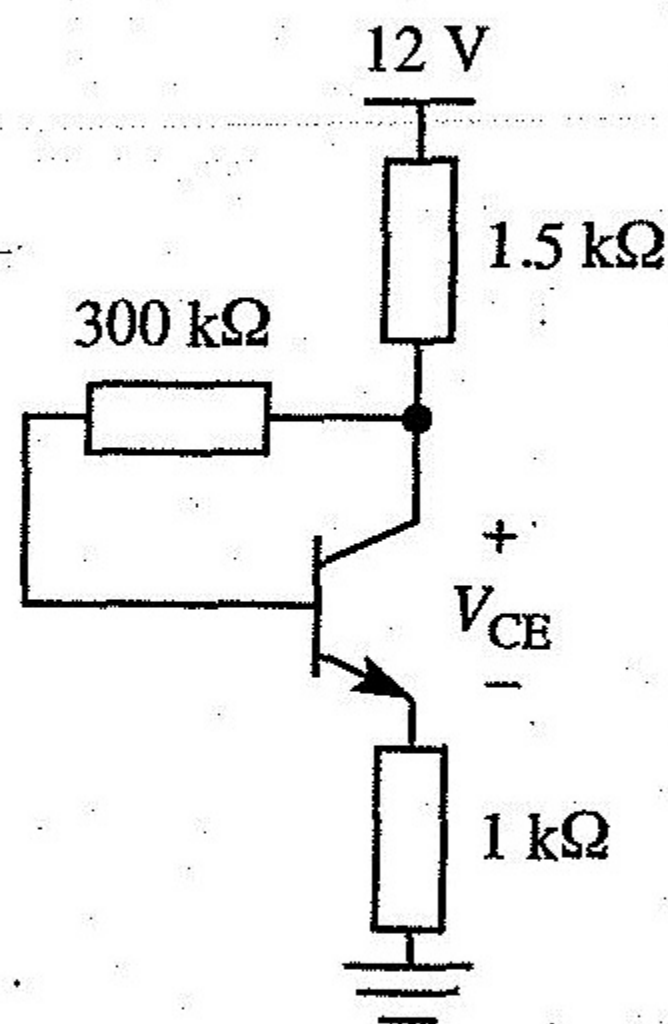


5.15 Determine V_C if $\beta = 150$ and $V_{BE} = 0.65$ V.

[4.4 V]

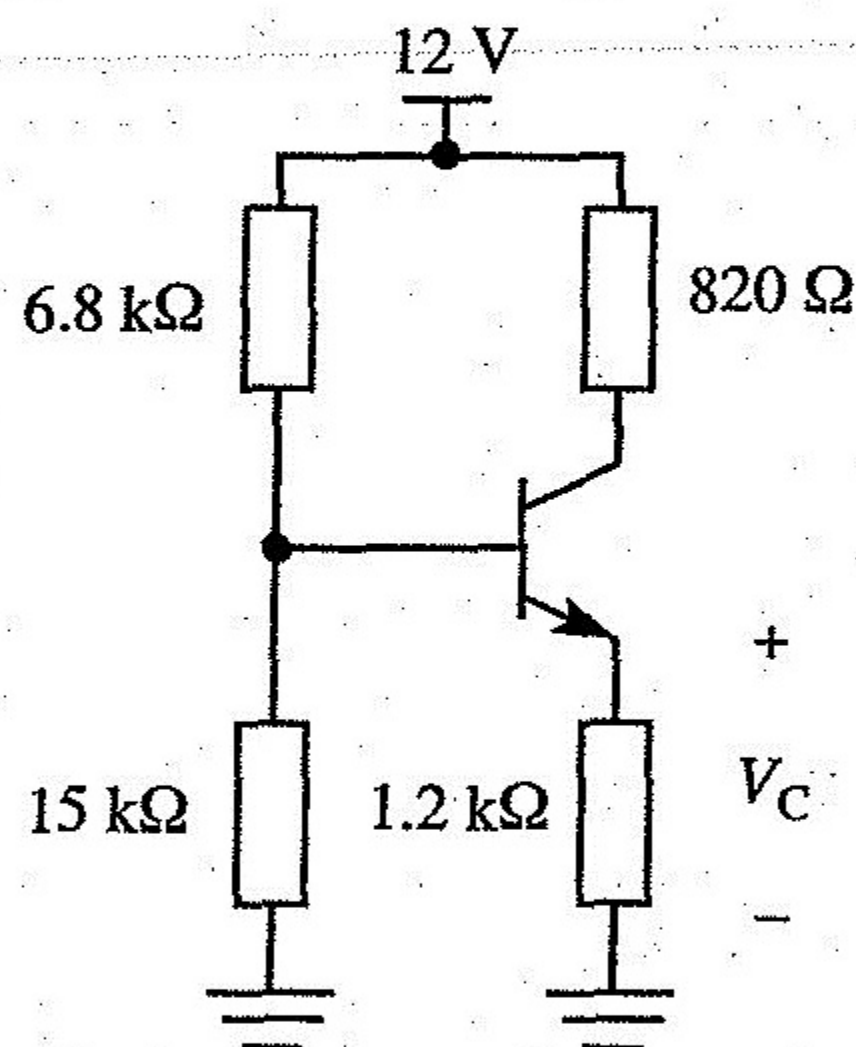


5.13 If $V_{CE} = 5$ V, $\beta = 250$ and $V_{BE} = 0.7$ V, determine R_B .

[537 kΩ]

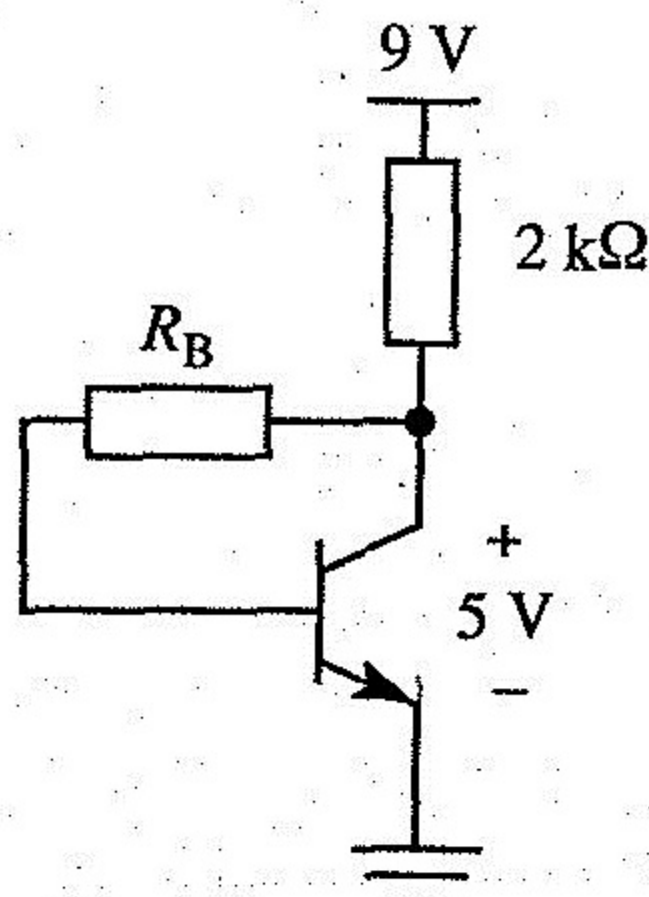


5.16 For the circuit shown $V_C = 4$ V. Determine the value of R_E if $\beta = 200$ and $V_{BE} = 0.7$ V.

[790 Ω]

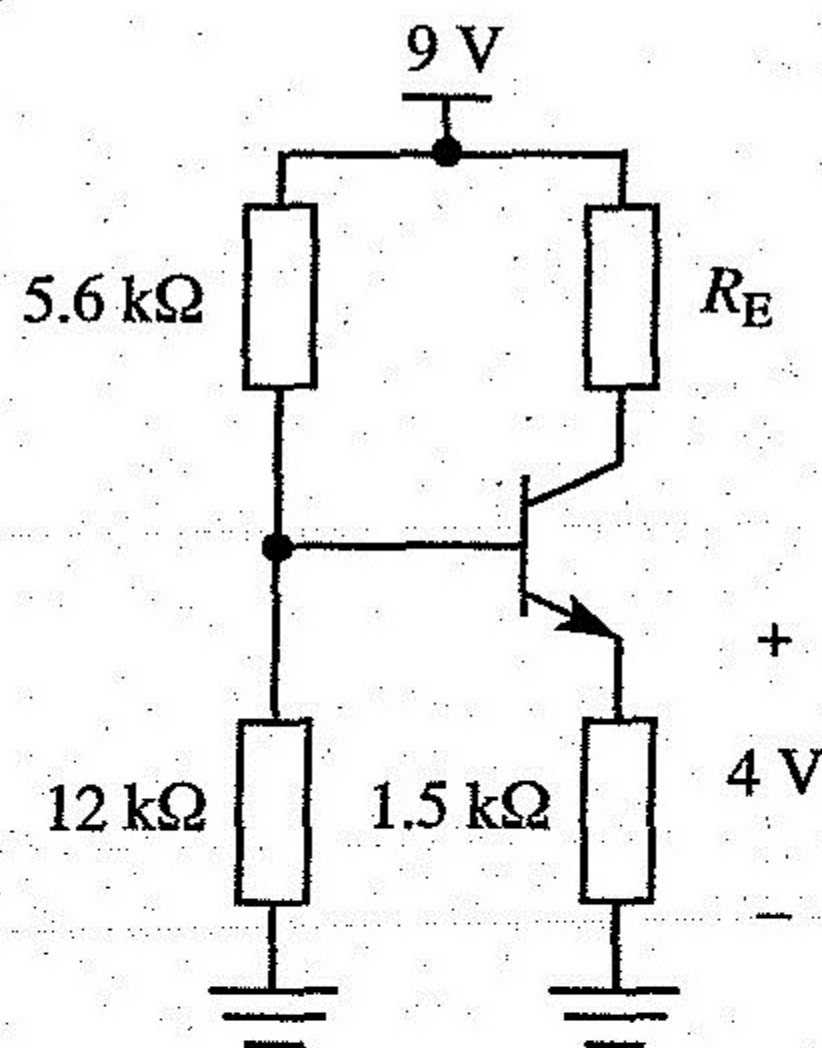

5.14 Determine the collector current for the pnp emitter-biased circuit if $\beta = 120$ and $V_{BE} = 0.7$ V.

[1.94 mA]

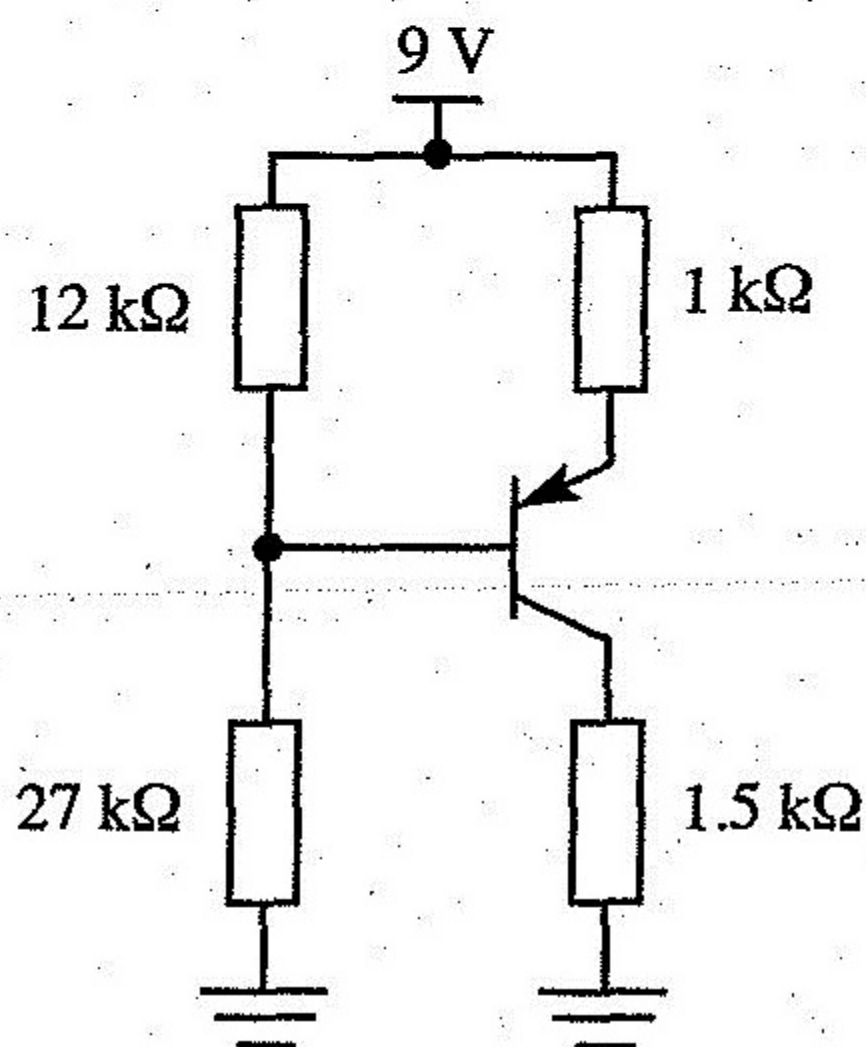

5.17 For Problem 5.10 the nearest preferred values for the resistors are:

$$R_1 = 33 \text{ k}\Omega, R_2 = 5.6 \text{ k}\Omega, R_E = 390 \text{ }\Omega \text{ and } R_C = 1.5 \text{ k}\Omega$$

Use PSpice to observe the value of the collector current for the two extremes of β , that is 120 and 320, with $V_{CC} = 12$ V.

[2.19 mA, 2.33 mA]

5.18 Use PSpice to verify the parameters in Problems 5.3, 5.7, 5.12 and 5.15.

[P5.3 $I_C = 2.18 \text{ mA}$, $V_{CE} = 3.52 \text{ V}$]

[P5.7 $V_{CE} = 4.95 \text{ V}$ and 4.01 V]

[P5.12 $V_{CE} = 6.37 \text{ V}$ and 3.66 V]

[P5.15 $V_C = 4.11 \text{ V}$]
