

1.1 Find  $I_1$  and  $I_2$  in the circuit in Fig. P2.11.


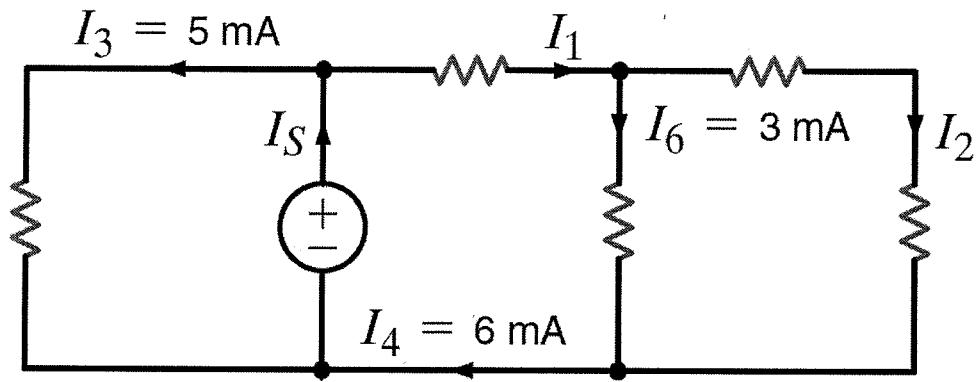


Figure P2.11

SOLUTION:

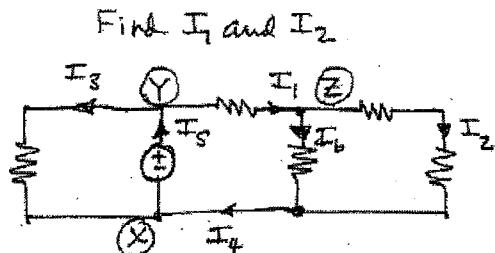

$$I_3 = 5 \text{ mA} \quad I_6 = 3 \text{ mA} \quad I_4 = 6 \text{ mA}$$

KCL @ (X): all currents enter

$$I_3 - I_S + I_4 = 0$$

$$I_S = 5 \times 10^{-3} + 6 \times 10^{-3} \Rightarrow I_S = 11 \text{ mA}$$

KCL @ (Y): all currents enter

$$-I_3 + I_S - I_1 = 0 \Rightarrow I_1 = I_S - I_3 = 11 \times 10^{-3} - 5 \times 10^{-3} \Rightarrow I_1 = 6 \text{ mA}$$

KCL @ (Z): all current enter

$$I_1 - I_6 - I_2 = 0 \Rightarrow I_2 = I_1 - I_6 = 6 \times 10^{-3} - 3 \times 10^{-3} \Rightarrow I_2 = 3 \text{ mA}$$

1.2 Find  $I_o$  and  $I_1$  in the circuit in Fig. P2.12.


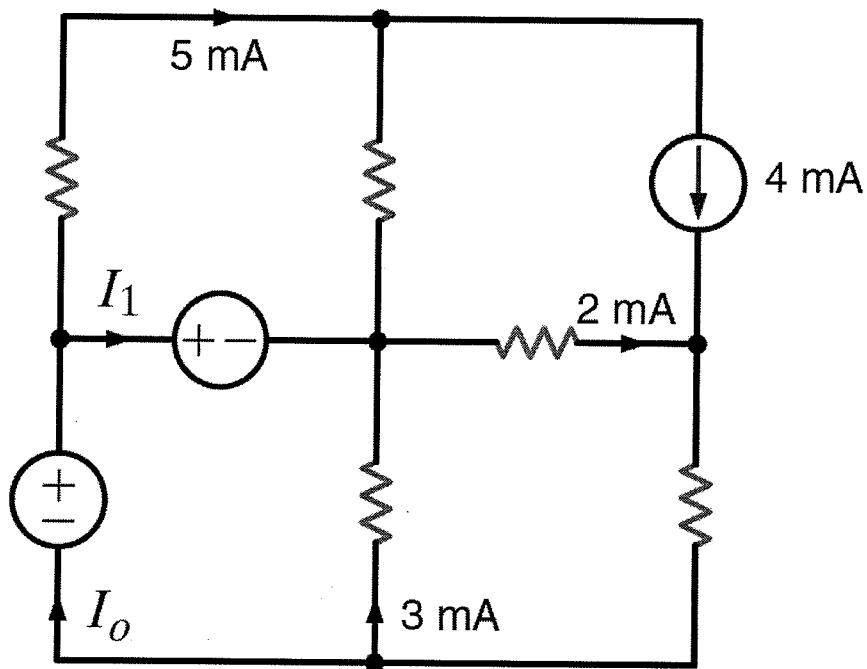


Figure P2.12

SOLUTION:

Find  $I_o$  and  $I_1$

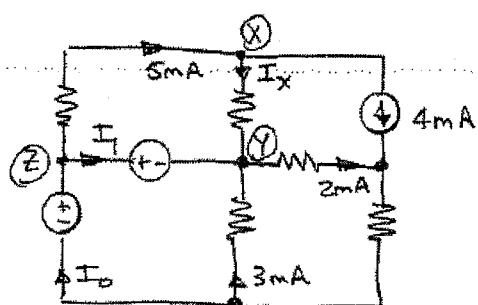

KCL @ (X) : currents enter

$$5 \times 10^{-3} - 4 \times 10^{-3} - I_x = 0 \Rightarrow I_x = 1 \text{ mA}$$

KCL @ (Y) : current enter

$$I_x - 2 \times 10^{-3} + 3 \times 10^{-3} + I_1 = 0 \Rightarrow I_1 = -2 \text{ mA}$$

KCL @ (Z) : current enter

$$-5 \times 10^{-3} - I_1 + I_o = 0 \Rightarrow I_o = 3 \text{ mA}$$

1.3 Find  $I_x$  in the circuit in Fig. P2.15.

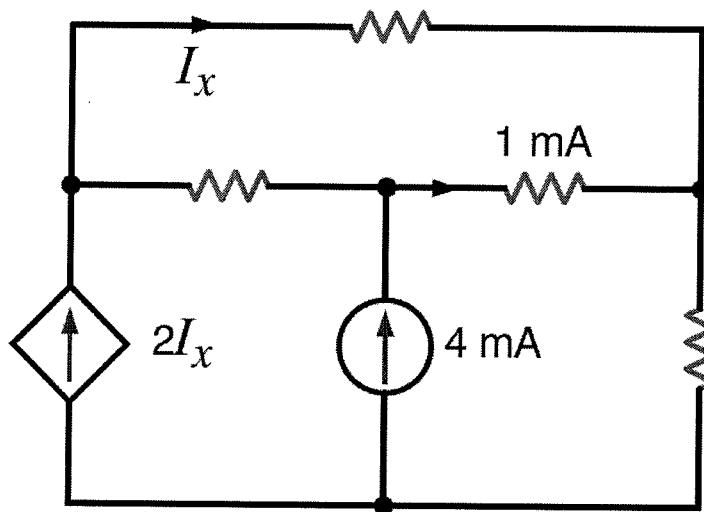


Figure P2.15

SOLUTION:

Find  $I_x$ .

KCL @ ④: currents leaving

$$-4 \times 10^{-3} + 10^{-3} + I_y = 0 \quad I_y = 3 \text{ mA}$$

KCL @ ③: currents entering

$$I_y + 2I_x - I_x = 0 \quad I_x = -3 \text{ mA}$$

1.4 Find  $U_{fb}$  and  $U_{ec}$  in the circuit in Fig. P2.17.

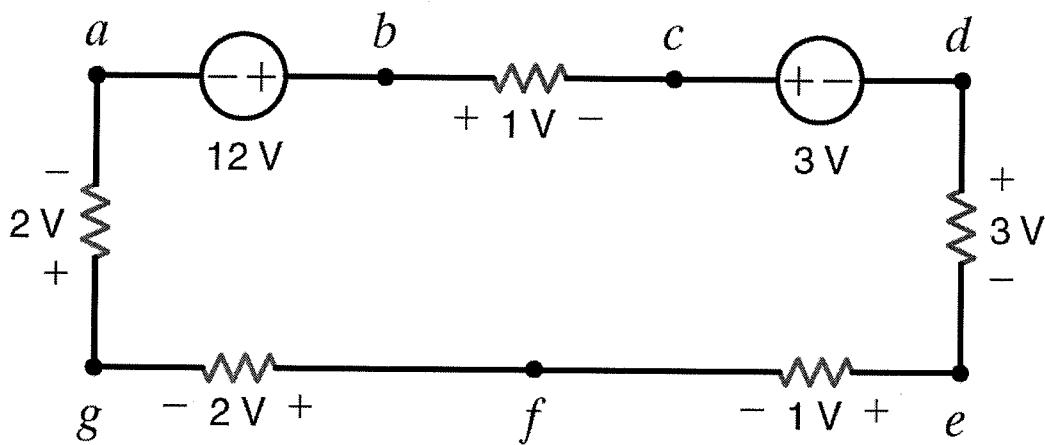


Figure P2.17

SOLUTION:

Find  $U_{fb}$  and  $U_{ec}$

KVL along abfga:

$$-12 + U_{bf} + 2 + 2 = 0$$

$$U_{bf} = 8 \text{ V} \Rightarrow U_{fb} = -8 \text{ V}$$

KVL along cdec:

$$3 + 3 + U_{ec} = 0 \Rightarrow U_{ec} = -6 \text{ V}$$

1.5 Find  $U_o$  in the circuit in Fig. P2.22.


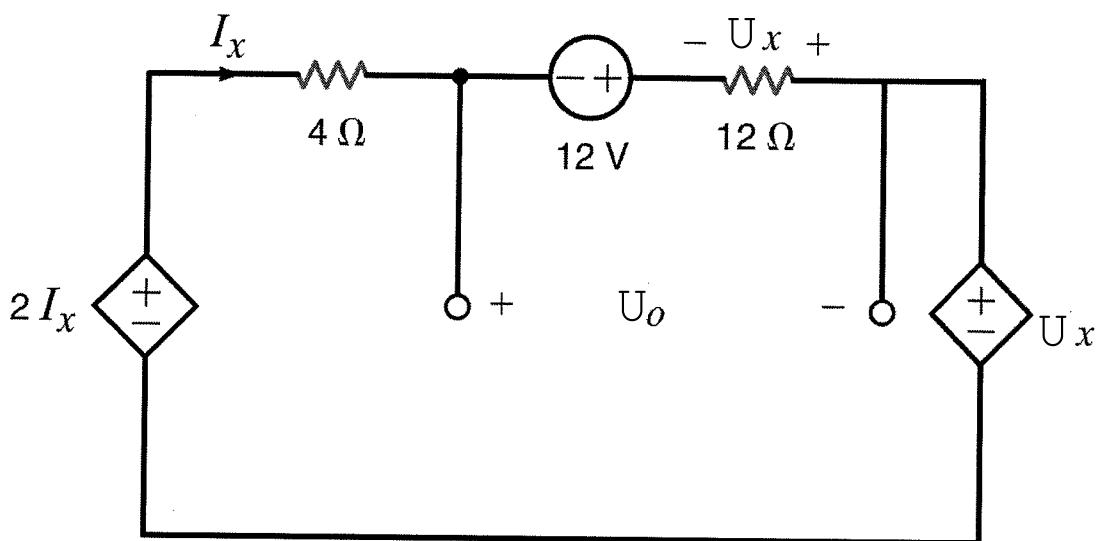


Figure P2.22

SOLUTION:

Find  $U_o$ .

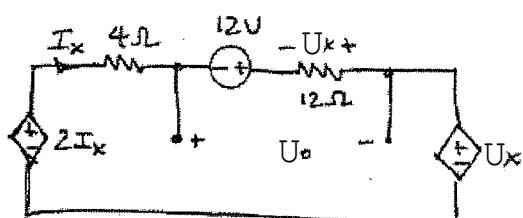

KVL:

$$4I_x - 12 + 12I_x + U_o - 2I_x = 0 \quad (1)$$

$$U_o = -12I_x \quad (2)$$

Substitute (2) into (1):  $4I_x + 12I_x - 12I_x - 2I_x = 12$

$$2I_x = 12 \Rightarrow I_x = 6A$$

$$U_o = -12 + 12I_x = -12 + 12(6) \Rightarrow U_o = 60V$$

1.6 Find  $U_1$  in the network in Fig. P2.26.

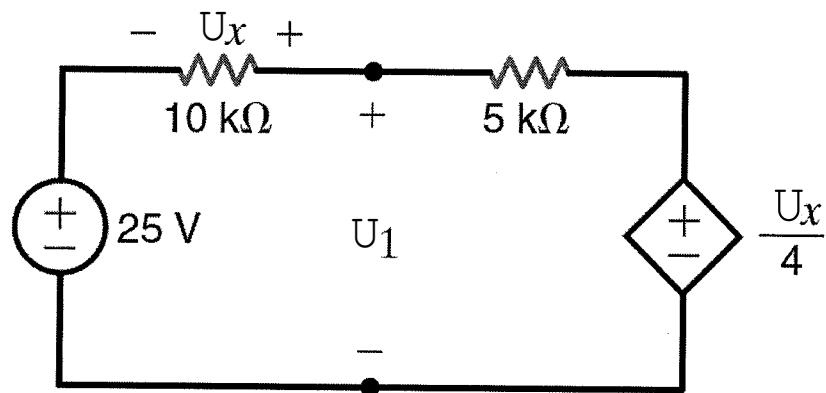


Figure P2.26

SOLUTION:

Find  $U_1$ .

$\text{KVL: } -25 + 10^4 I + 5 \times 10^3 I + \frac{U_x}{4} = 0 \quad (1)$

also:  $U_x = -10^4 I \quad (2)$

Substitute (2) into (1):

$$-25 + I (10^4 + 5 \times 10^3 - 10^4/4) = 0$$

$$I = 2 \text{ mA}$$

$$U_1 = 25 - 10^4 I \Rightarrow U_1 = 5 \text{ V}$$

1.7 If  $U_o = 4 \text{ V}$  in the network in Fig. P2.30, find  $U_s$ .


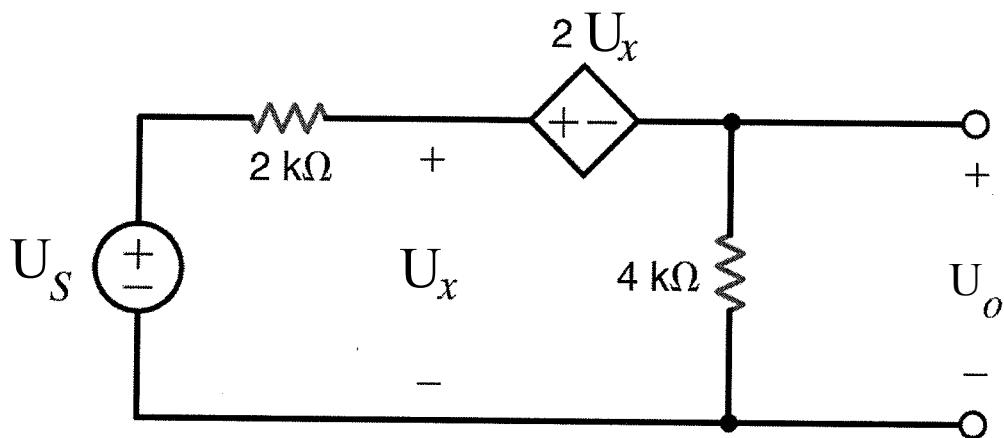


Figure P2.30

SOLUTION:

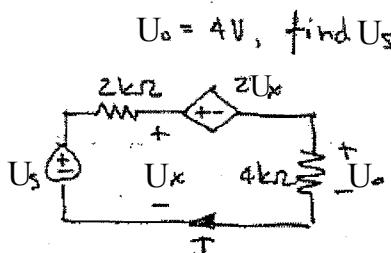

$$\text{KVL: } -U_s + 2 \times 10^3 I + 2U_x + 4 \times 10^3 I = 0 \quad (1)$$

$$\text{also: } -U_x + 2U_x + U_o = 0 \Rightarrow U_x = -4 \text{ V} \quad (2)$$

$$\text{and } U_o = 4 \times 10^3 I \Rightarrow I = 1 \text{ mA} \quad (3)$$

substitute (2) & (3) into (1):  $I(6 \times 10^3) + 2U_x = U_s \Rightarrow \boxed{U_s = -2 \text{ V}}$

1.8 Find  $R_{AB}$  in the circuit in Fig. P2.49.

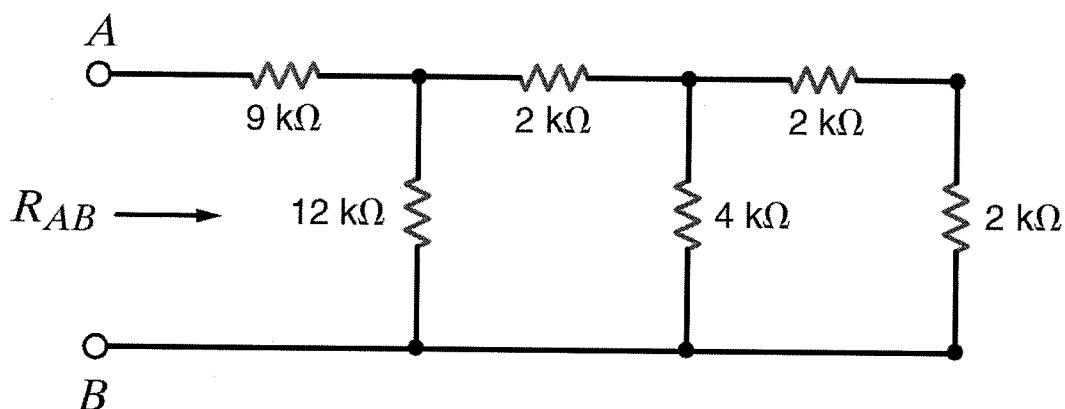


Figure P2.49

SOLUTION:

Find  $R_{AB}$ .

Diagram showing the circuit with node labels and equivalent resistances:

Nodes labeled: A, B,  $R_1$ ,  $R_2$ ,  $R_3$ ,  $R_4$ ,  $R_5$ ,  $R_6$ ,  $R_Y$ ,  $R_X$ ,  $R_W$ .

$R_{AB} \rightarrow$

Equivalent resistances:

$$R_1 = 9\text{ k}\Omega \quad R_2 = 12\text{ k}\Omega \quad R_3 = 2\text{ k}\Omega$$

$$R_4 = 4\text{ k}\Omega \quad R_5 = 2\text{ k}\Omega \quad R_6 = 2\text{ k}\Omega$$

$$R_W = R_5 + R_6 = 4\text{ k}\Omega$$

$$R_X = R_4 // R_W = 2\text{ k}\Omega$$

$$R_Y = R_3 + R_X = 4\text{ k}\Omega$$

$$R_Z = R_2 // R_Y = 3\text{ k}\Omega$$

$$R_{AB} = R_1 + R_Z \Rightarrow R_{AB} = 12\text{ k}\Omega$$

1.9 Find  $I_1$  and  $U_o$  in the circuit in Fig. P2.61.

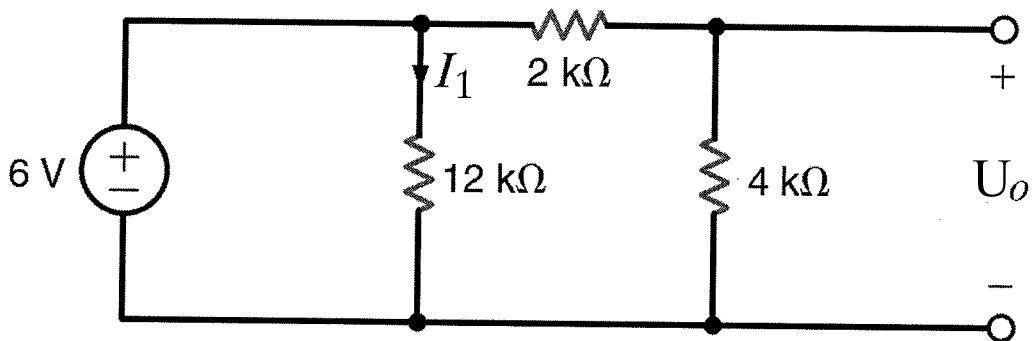


Figure P2.61

SOLUTION:

Find  $I_1$  &  $U_o$

$$\begin{aligned}
 & \text{Circuit diagram: } 6V \text{ source, } R_1 = 12\text{k}\Omega, R_2 = 2\text{k}\Omega, R_3 = 4\text{k}\Omega, I_1, U_o \\
 & I_1 = \frac{6}{R_1} \rightarrow I_1 = 0.5\text{mA} \\
 & U_o = 6 \left[ \frac{R_3}{R_2 + R_3} \right] \Rightarrow U_o = 4V
 \end{aligned}$$

$R_1 = 12\text{k}\Omega$   
 $R_2 = 2\text{k}\Omega$   
 $R_3 = 4\text{k}\Omega$

1.10 Find  $I_1$  and  $U_o$  in the circuit in Fig. P2.62.

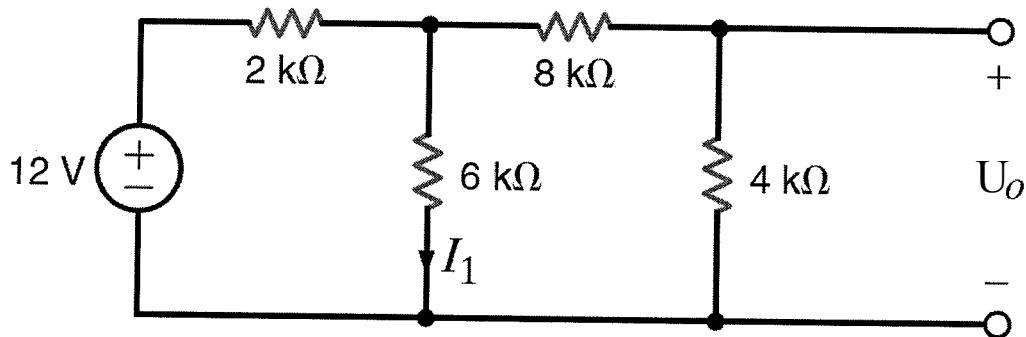


Figure P2.62

SOLUTION:


Find  $I_1$  &  $U_o$ .

$$\begin{aligned}
 &\text{Circuit diagram: } 12V \text{ source} \parallel 2k\Omega \text{ } \parallel 6k\Omega \text{ } \parallel 8k\Omega \text{ } \parallel 4k\Omega \text{ } \parallel \text{ ground} \\
 &\Rightarrow \text{Thevenin equivalent circuit: } 12V \text{ source} \parallel R_A = 6k\Omega // (8k\Omega + 4k\Omega) = 4k\Omega \\
 &\quad \text{Voltage } U_x \text{ across } 8k\Omega \text{ and } 4k\Omega: U_x = 12 \left[ \frac{R_4}{R_A + R_4} \right] = 8V \\
 &\quad \text{Current } I_x \text{ through } 8k\Omega \text{ and } 4k\Omega: I_x = \frac{12}{R_A + R_4} = 2mA \\
 &\quad \text{Current } I_1 \text{ through } 6k\Omega: I_1 = I_x \left[ \frac{R_4 + R_3}{R_2 + R_4 + R_3} \right] = 1.33mA
 \end{aligned}$$

$$\text{By current division: } I_1 = I_x \left[ \frac{R_4 + R_3}{R_2 + R_4 + R_3} \right] \Rightarrow I_1 = 1.33mA$$

$$\text{By voltage division: } U_o = U_x \left[ \frac{R_4}{R_4 + R_3} \right] \Rightarrow U_o = 2.67V$$


1.11 Find  $U_o$  in the network in Fig. P2.111.

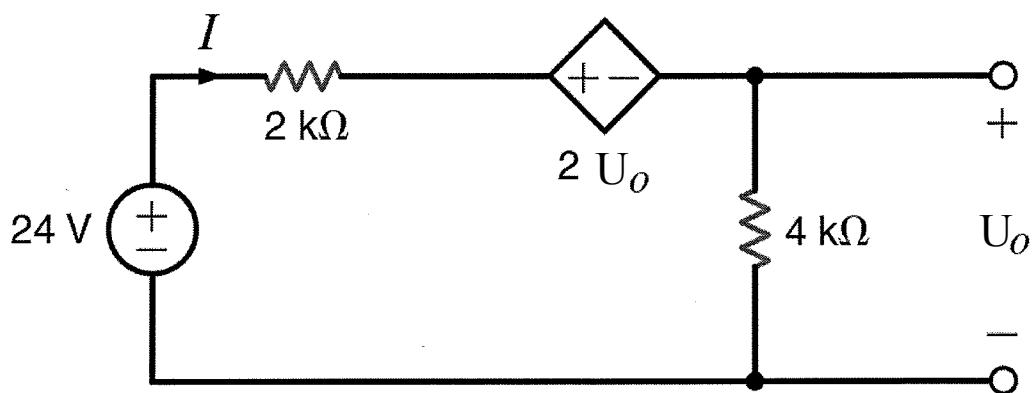

**Figure P2.111**

SOLUTION:

Find  $U_o$ .

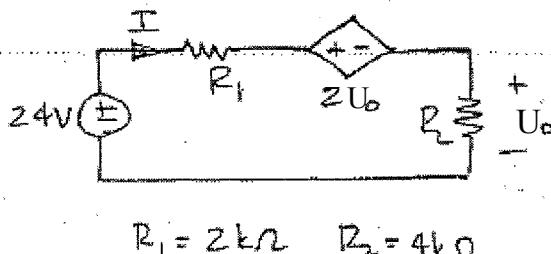

$$24 = R_1 I + 2U_o + R_2 I$$

$$U_o = R_2 I = 4I$$

$$24 = I(14) \Rightarrow I = \frac{12}{7}$$

$$U_o = 6.86 \text{ V}$$

- 1.12** A typical transistor amplifier is shown in Fig. P2.117. Find the amplifier gain  $G$  (i.e., the ratio of the output voltage to the input voltage).


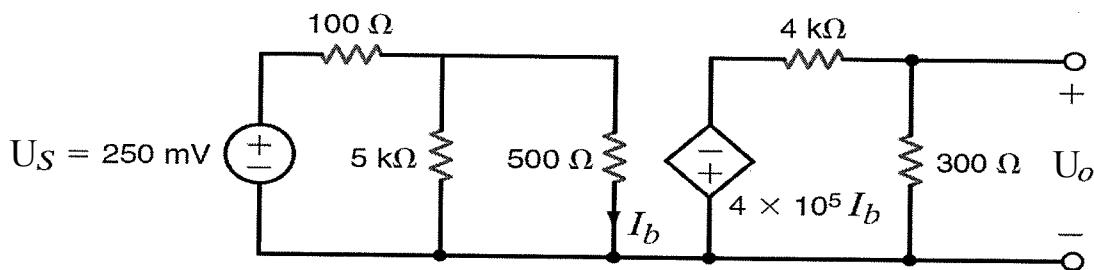


Figure P2.117

SOLUTION:

$$\text{Find } G = U_o / U_s$$

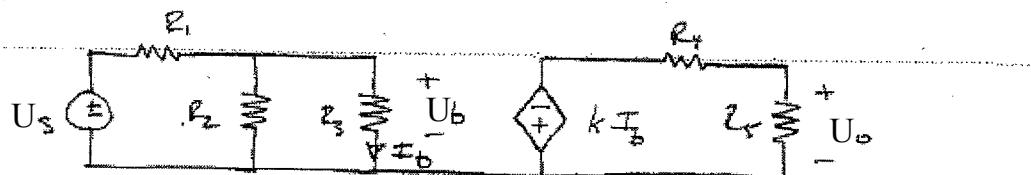

$$U_s = \frac{1}{4} V \quad R_1 = 100 \Omega \quad R_2 = 5 k\Omega \quad R_3 = 500 \Omega$$

$$k = 4 \times 10^5 \quad R_4 = 4 k\Omega \quad R_5 = 300 \Omega$$

$$U_b = U_s \left[ \frac{R_2 / R_3}{R_1 + (R_2 / R_3)} \right] = 0.205 V$$

$$I_b = U_b / R_3 = 410 \mu A$$

$$U_o = -k I_b \left[ \frac{R_5}{R_4 + R_5} \right] \rightarrow U_o = -11.4 V$$

$$G = \frac{U_o}{U_s}$$

$$G = -45.8$$

**1.13** Find  $I_o$  in the circuit in Fig. P3.1 using nodal analysis.


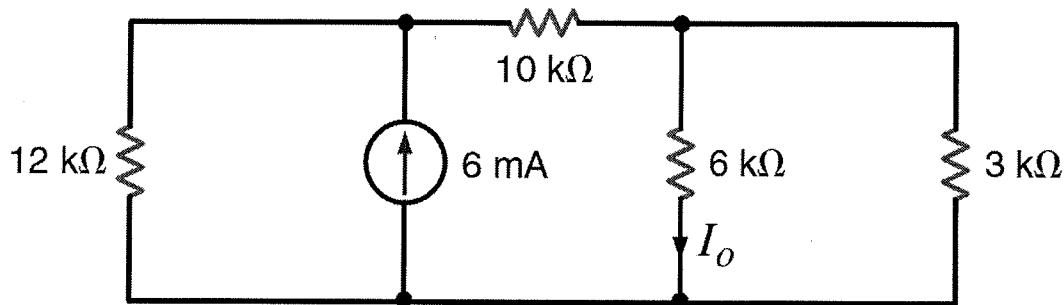


Figure P3.1

SOLUTION:

$I_o$  via nodal.

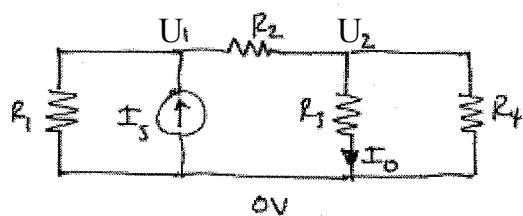

$$@U_1: \frac{U_1}{R_1} - I_s + \frac{U_1 - U_2}{R_2} = 0$$

$$@U_2: \frac{U_2 - U_1}{R_2} + \frac{U_2}{R_3} + \frac{U_2}{R_4} = 0$$


$$R_1 = 12 \text{ k}\Omega \quad R_2 = 10 \text{ k}\Omega \quad R_3 = 6 \text{ k}\Omega$$

$$\therefore I_o = U_2 / R_3$$

$$R_4 = 3 \text{ k}\Omega \quad I_s = 6 \text{ mA}$$

$$I_o = 1 \text{ mA}$$


**1.14** Find  $I_o$  in the circuit in Fig. P3.5 using nodal analysis.

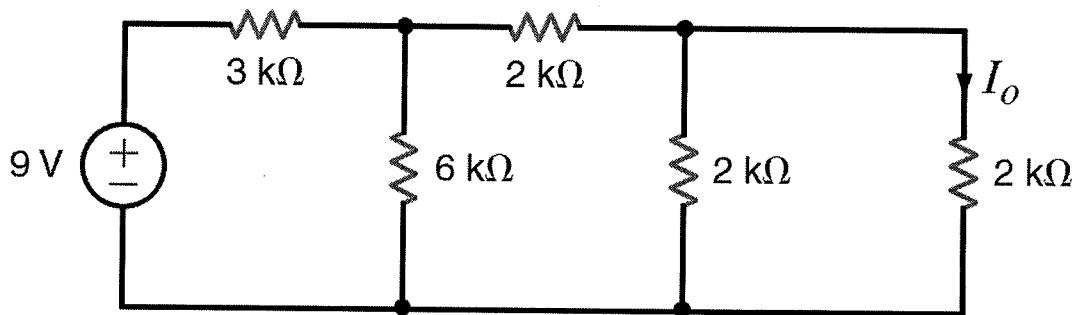

**Figure P3.5**

SOLUTION:

Find  $I_o$  by nodal.

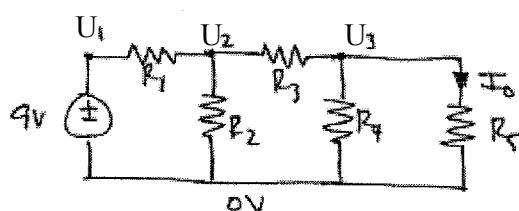

$$\textcircled{1} \quad U_1: \quad U_1 = 9V$$

$$\textcircled{2} \quad U_2: \quad \frac{U_2 - U_1}{R_1} + \frac{U_2}{R_2} + \frac{U_2 - U_3}{R_3} = 0$$


$$\textcircled{3} \quad U_3: \quad \frac{U_3 - U_2}{R_3} + \frac{U_3}{R_4} + \frac{U_3}{R_5} = 0$$

$$R_1 = 3k\Omega \quad R_2 = 6k\Omega \quad R_3 = R_4 = R_5 = 2k\Omega$$

$$\text{and } I_o = U_3 / R_5$$

$$\boxed{I_o = 0.6mA}$$


1.15 Find  $I_o$  in the network in Fig. P3.6 using nodal analysis.

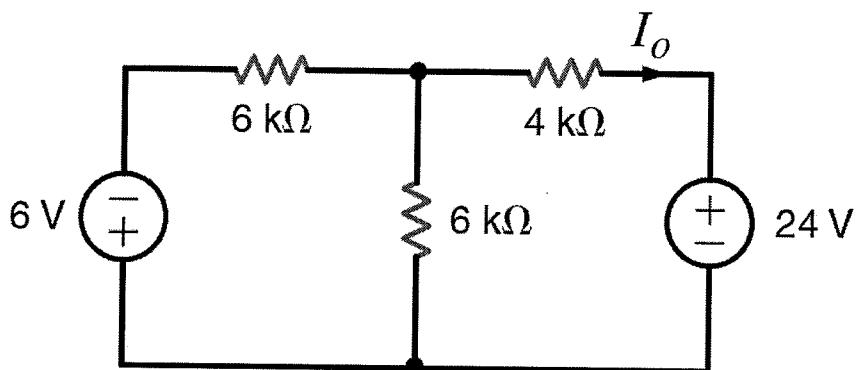

**Figure P3.6**

SOLUTION:

Find  $I_o$  by nodal.

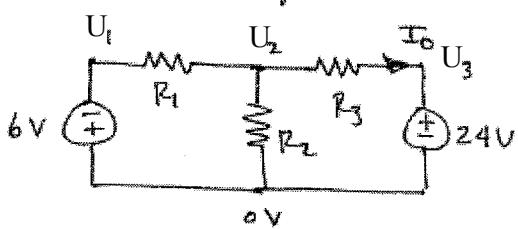

$$\textcircled{1} \quad U_1: \quad U_1 = -6V$$

$$\textcircled{2} \quad U_2: \quad \frac{U_2 - U_1}{R_1} + \frac{U_2 - U_3}{R_2} + \frac{U_2 - U_3}{R_3} = 0$$

$$\textcircled{3} \quad U_3: \quad U_3 = 24V$$

$$R_1 = R_2 = 6 \text{ k}\Omega \quad R_3 = 4 \text{ k}\Omega$$

$$\text{and } I_o = (U_2 - U_3) / R_3$$

$$U_2 = 8.57V$$

$I_o = -3.86 \text{ mA}$

1.16 Find  $U_o$  in the circuit in Fig. P3.8 using nodal analysis.


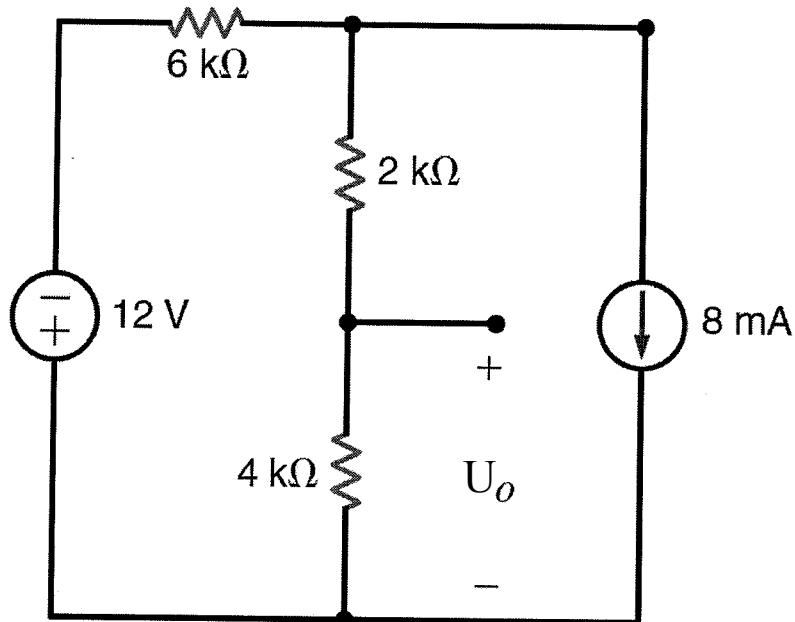


Figure P3.8

SOLUTION:

Find  $U_o$  by nodal.

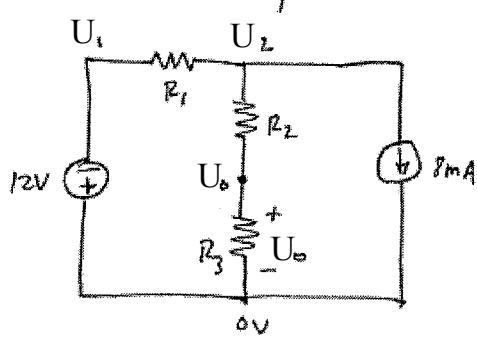

$$U_1 = -12 \text{ V}$$

$$@ U_2 : \frac{U_2 - U_1}{R_1} + \frac{U_2 - U_o}{R_2} + 8 \times 10^{-3} = 0$$

$$@ U_o : \frac{U_2 - U_o}{R_2} = \frac{U_o}{R_3}$$

$$U_o = -20 \text{ V}$$

$$R_1 = 6 \text{ k}\Omega \quad R_2 = 2 \text{ k}\Omega \quad R_3 = 4 \text{ k}\Omega$$

1.17 Use nodal analysis to find  $U_o$  in the circuit in Fig. P3.9.


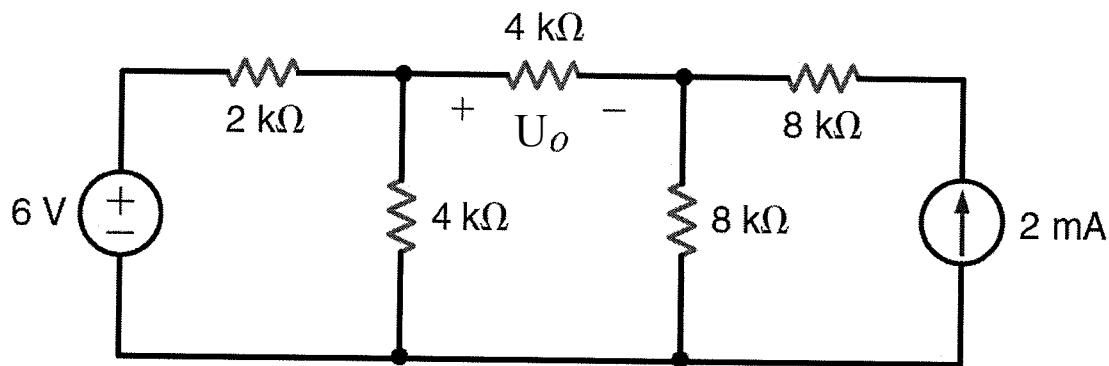


Figure P3.9

SOLUTION:

Find  $U_o$  by nodal.

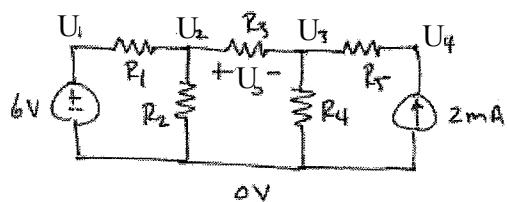

$$U_1 = 6V$$

$$\text{@ } U_2: \frac{U_2 - U_1}{R_1} + \frac{U_2}{R_2} + \frac{U_2 - U_3}{R_3} = 0$$

$$\text{@ } U_3: \frac{U_3 - U_2}{R_2} + \frac{U_3}{R_4} + \frac{U_3 - U_4}{R_5} = 0$$

$$R_1 = 2k\Omega \quad R_2 = R_3 = 4k\Omega$$

$$R_4 = R_5 = 8k\Omega$$

$$\text{@ } U_4: \frac{U_4 - U_3}{R_5} = 2 \times 10^{-3}$$

$$\text{and } U_o = U_2 - U_3$$

$$U_2 = 5.2V, \quad U_3 = 8.8V$$

$$U_o = -3.6V$$

**1.18** Use nodal analysis to find  $U_o$  in the circuit in Fig. P3.13.


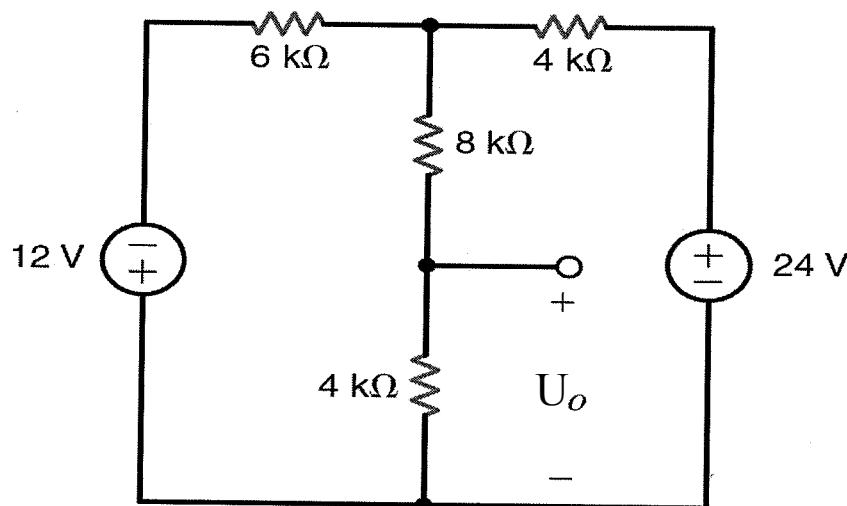


Figure P3.13

SOLUTION:

Find  $U_o$  by nodal.

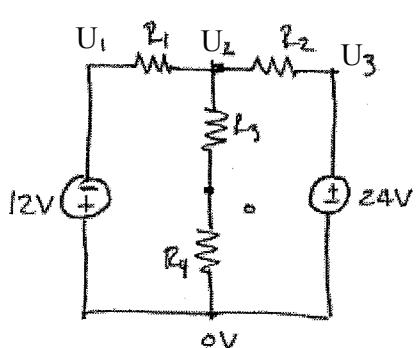

$$U_1 = -12 \text{ V} \quad U_3 = +24 \text{ V}$$

$$\text{@ } U_2: \quad \frac{U_2 - U_1}{R_1} + \frac{U_2 - U_3}{R_2} + \frac{U_2 - U_o}{R_3} = 0$$

$$\text{@ } U_o: \quad \frac{U_o - U_2}{R_3} + \frac{U_o}{R_4} = 0$$

$$U_o = 2.67 \text{ V}$$

$$R_1 = 6 \text{ k}\Omega \quad R_2 = R_4 = 4 \text{ k}\Omega$$

$$R_3 = 8 \text{ k}\Omega$$

1.19 Find  $U_o$  in the network in Fig. P3.32 using nodal analysis.


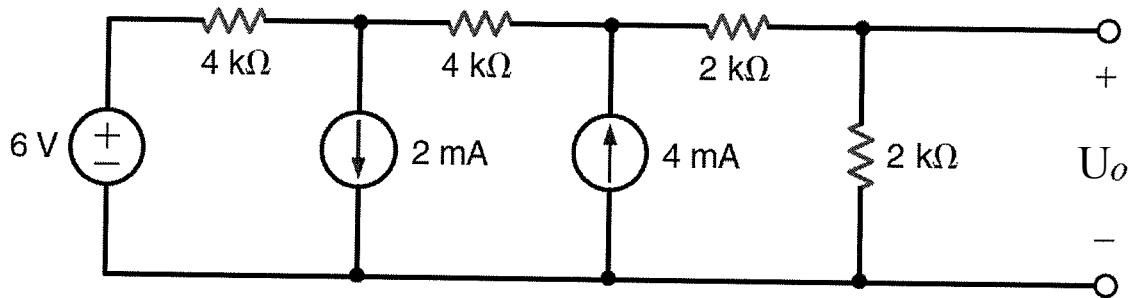


Figure P3.32

SOLUTION:

Find  $U_o$  by nodal.

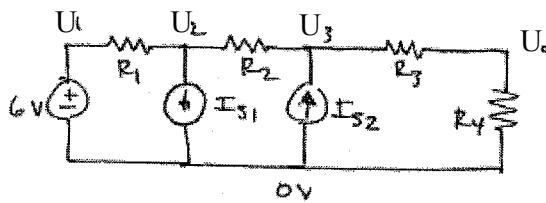

$$U_1 = 6 \text{ V}$$

$$\text{@ } U_2: \frac{U_2 - U_1}{R_1} + \frac{U_2 - U_3}{R_2} + I_{S1} = 0$$

$$\text{@ } U_3: \frac{U_3 - U_2}{R_2} + \frac{U_3 - U_o}{R_3} = I_{S2}$$

$$\text{@ } U_o: \frac{U_o - U_3}{R_3} + \frac{U_o - U_0}{R_4} = 0$$

$$U_o = 5 \text{ V}$$

$$R_1 = R_2 = 4 \text{ k}\Omega \quad R_3 = R_4 = 2 \text{ k}\Omega$$

$$I_{S1} = 2 \text{ mA} \quad I_{S2} = 4 \text{ mA}$$

1.20 Use mesh equations to find  $U_o$  in the circuit in Fig. P3.62.


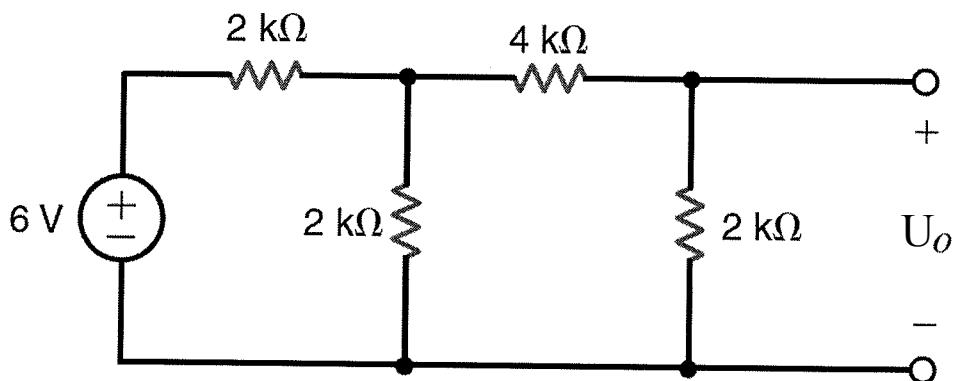


Figure P3.62

SOLUTION:

Use mesh analysis to find  $U_o$ .

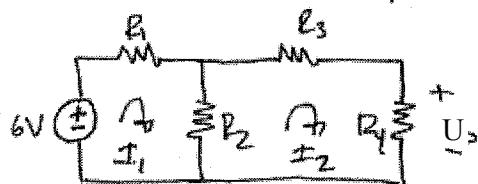

$$R_1 = R_2 = R_4 = 2 \text{ k}\Omega \quad R_3 = 4 \text{ k}\Omega$$

$$0 = I_1 R_1 + (I_1 - I_2) R_2$$

$$0 = -R_2 I_1 + I_2 (R_2 + R_3 + R_4)$$

$$U_o = I_2 R_4$$

$$I_2 = 429 \mu\text{A}$$

$$U_o = 858 \text{ mV}$$

1.21 Use mesh analysis to find  $U_o$  in the circuit in Fig. P3.65.

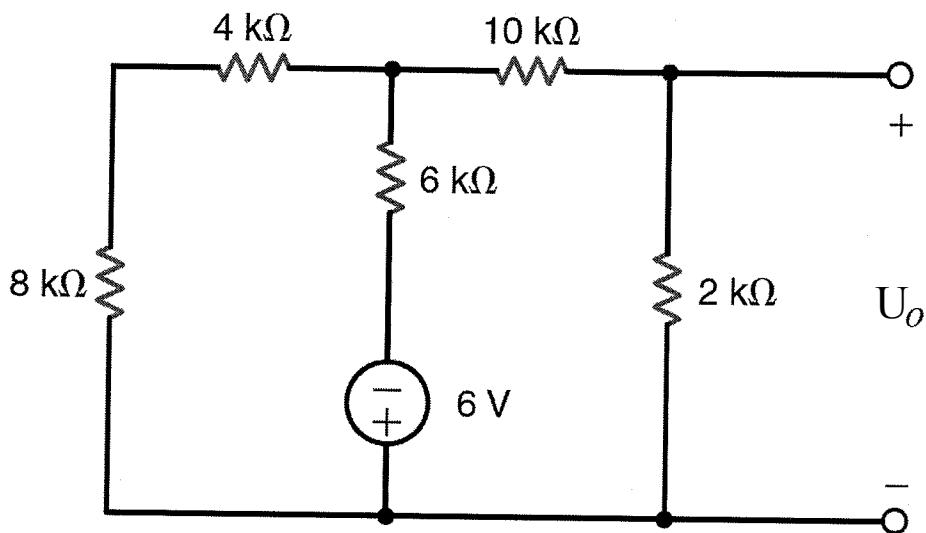


Figure P3.65

SOLUTION:

Find  $U_o$  via mesh

$$R_1 = 4\text{k}\Omega \quad R_2 = 8\text{k}\Omega \quad R_3 = 6\text{k}\Omega$$

$$R_4 = 10\text{k}\Omega \quad R_5 = 2\text{k}\Omega$$

$$U_o = I_2 R_5$$

$$I_1 R_1 + I_1 R_2 + (I_1 - I_2) R_3 = 6$$

$$I_2 R_4 + I_2 R_5 + (I_2 - I_1) R_3 = -6$$

$$I_2 = -250\mu\text{A}$$

$$U_o = -0.5\text{ V}$$

**1.22** Use loop analysis to find  $U_o$  in the circuit in Fig. P3.67.


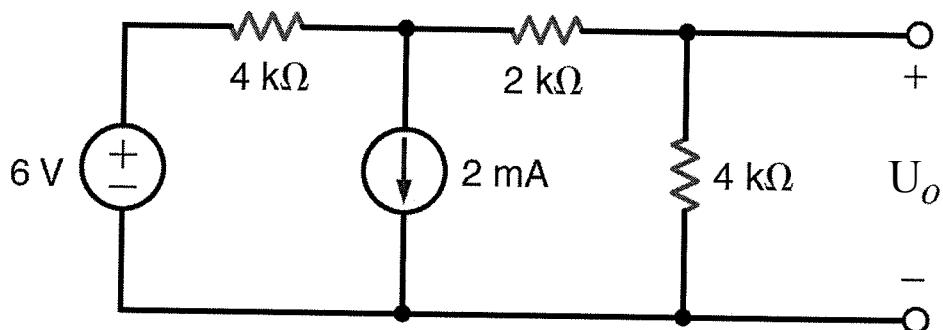


Figure P3.67

SOLUTION:

Find  $U_o$  using loop analysis.

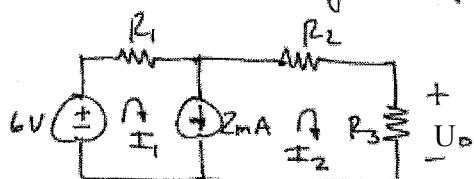

$$R_1 = 4 \text{ k}\Omega \quad R_2 = 2 \text{ k}\Omega \quad R_3 = 4 \text{ k}\Omega$$

$$2 \text{ mA} = I_1 - I_2$$

$$6 = I_1 R_1 + I_2 R_2 + I_2 R_3$$

$$U_o = I_2 R_3$$

$$I_2 = -200 \mu\text{A}$$

$$U_o = -0.8 \text{ V}$$

**1.23** Find  $I_o$  in the network in Fig. P3.69 using mesh analysis.


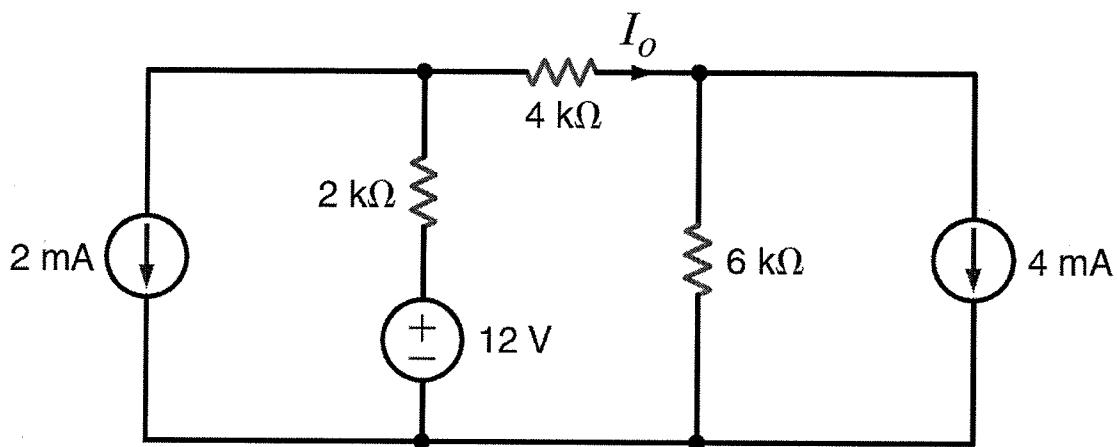


Figure P3.69

SOLUTION:

Use mesh analysis to find  $I_o$ .

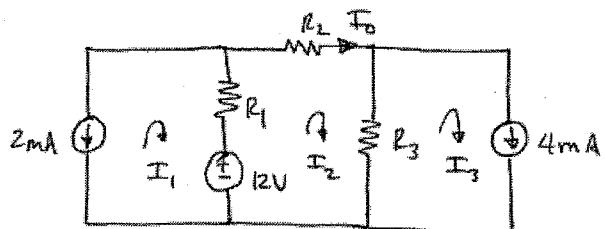

$$R_1 = 2 \text{ k}\Omega \quad R_2 = 4 \text{ k}\Omega \quad R_3 = 6 \text{ k}\Omega$$

$$I_o = I_2$$

$$I_1 = -2 \text{ mA}$$

$$I_3 = 4 \text{ mA}$$

$$12 = (I_2 - I_1)R_1 + I_2R_2 + (I_2 - I_3)R_3 \rightarrow I_2 = 2.67 \text{ mA}$$

$$\boxed{I_o = 2.67 \text{ mA}}$$

1.24 Find  $U_o$  in the circuit in Fig. P3.84 using mesh analysis.


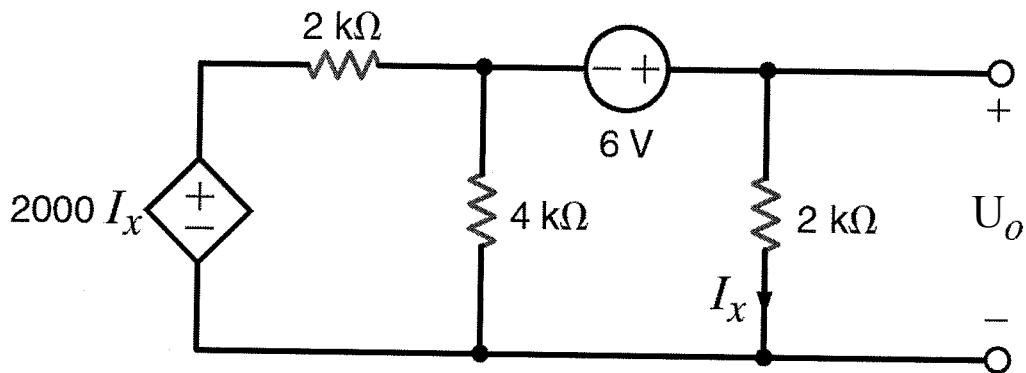


Figure P3.84

SOLUTION:

Find  $U_o$  using mesh analysis.

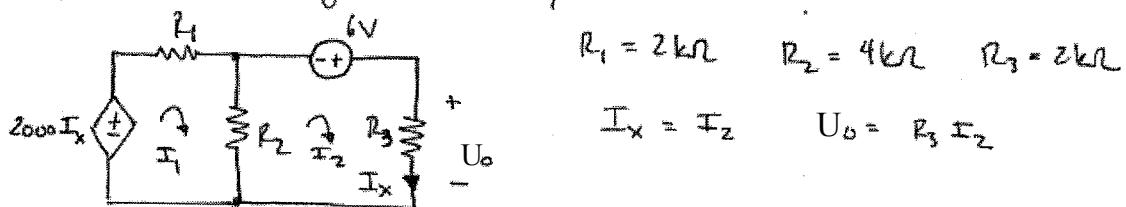

$$2000 I_x = I_1 R_1 + (I_1 - I_2) R_2$$

$$6 = I_2 R_3 + (I_2 - I_1) R_2$$

$$I_2 = 3 \text{ mA}$$

$$U_o = 6 \text{ V}$$

1.25 Find  $U_o$  in the circuit in Fig. 3PFE-1.


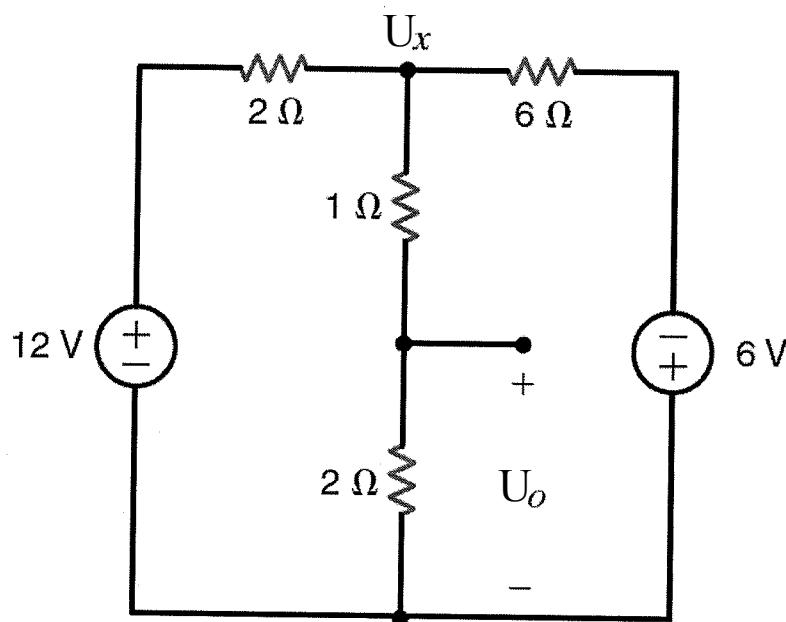


Figure 3PFE-1

---

### SOLUTION

Find  $U_o$ .

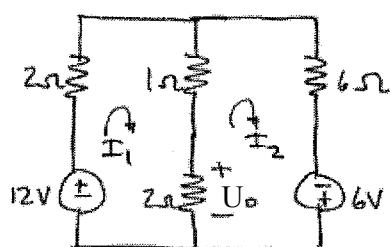

$$12 = 2I_1 + (I_1 - I_2) + 2(I_1 - I_2)$$

$$6 = 2(I_2 - I_1) + (I_2 - I_1) + 6I_2$$

$$U_o = 2(I_1 - I_2)$$

Results:  $I_1 = 3.5 \text{ A}$ ,  $I_2 = 1.83 \text{ A}$

$U_o = 3.33 \text{ V}$

**1.26** Determine the voltage  $U_o$  in the circuit in Fig. 3PFE-4.


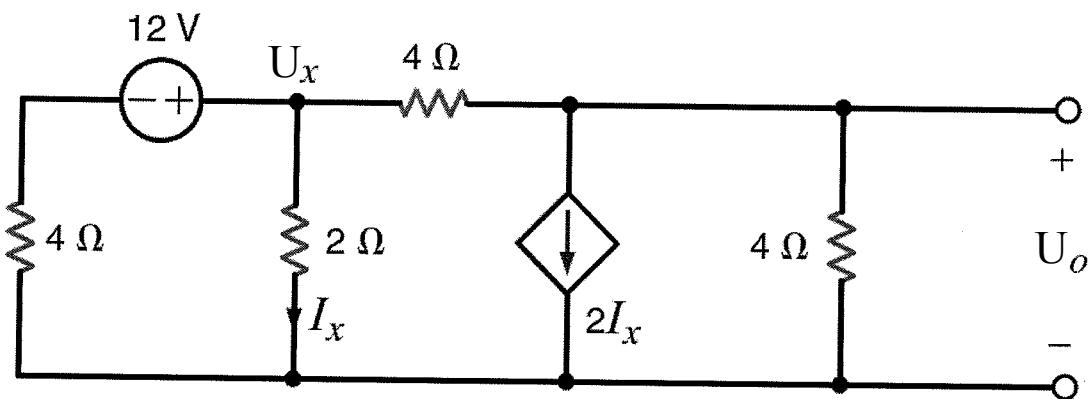


Figure 3PFE-4

SOLUTION

Find  $U_o$

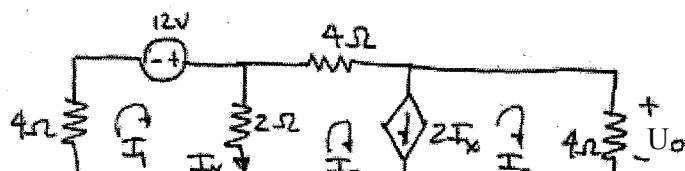

$$12 = 4I_1 + 2(I_1 - I_2)$$

$$I_x = I_1 - I_2$$

$$U_o = 4I_3$$

$$2I_x = I_2 - I_3$$

$$4I_1 + 4I_2 + 4I_3 = 12$$

Result:  $I_3 = -0.818 \text{ A}$

$$U_o = -3.27 \text{ V}$$