

2.1 Determine the gain of the amplifier in Fig. P4.9. What is the value of I_o ?

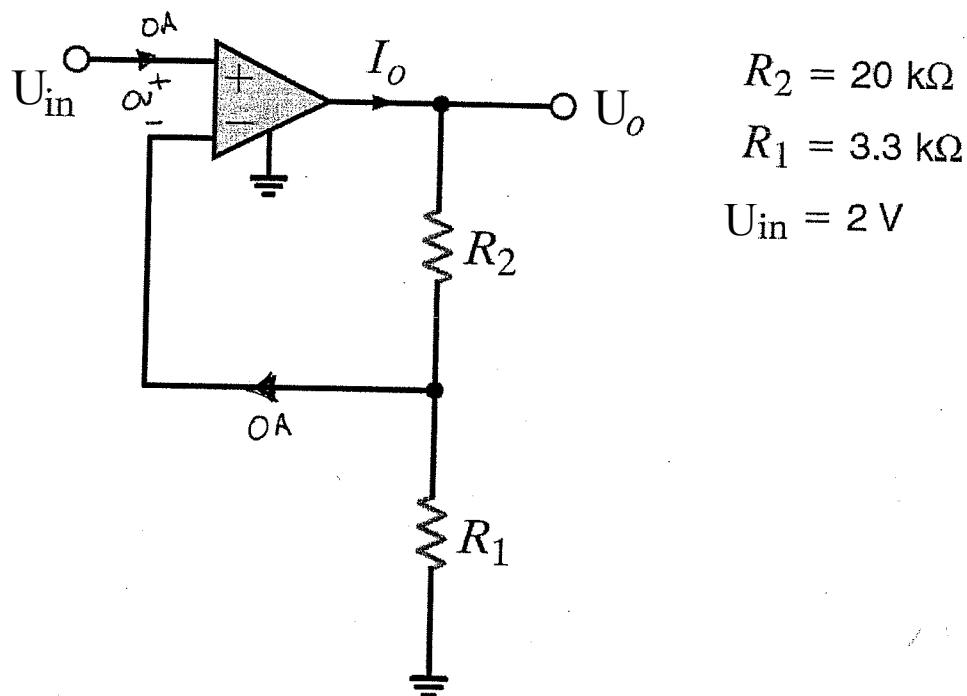


Figure P4.9

SOLUTION:

Basic noninverting configuration

$$\frac{U_o}{U_{in}} = 1 + \frac{R_2}{R_1} \Rightarrow \boxed{\frac{U_o}{U_{in}} = 7.06}$$

If $U_{in} = 2 \text{ V}$, $U_o = 14.12 \text{ V}$

$$I_o = \frac{U_o}{R_1 + R_2} = 606 \mu\text{A} \quad \boxed{I_o = 606 \mu\text{A}}$$

2.2 For the amplifier in Fig. P4.10, find the gain and I_o ?

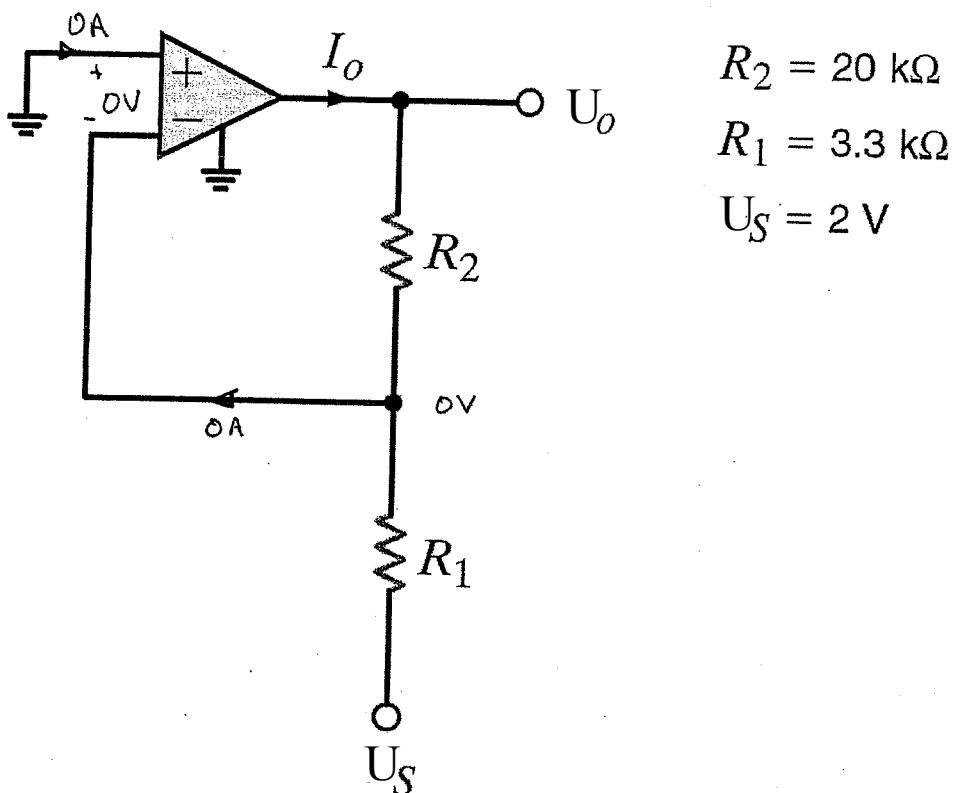


Figure P4.10

SOLUTION:

Basic inverting configuration, $\frac{U_o}{U_S} = -\frac{R_2}{R_1} \Rightarrow -6.06 = \frac{U_o}{U_S}$

$$I_o = \frac{U_o}{R_2} \quad U_o = (-6.06)U_S = -12.12$$

$$I_o = -606 \mu A$$

2.3 Using the ideal op-amp assumptions, determine the values of U_o and I_1 in Fig. P4.11.

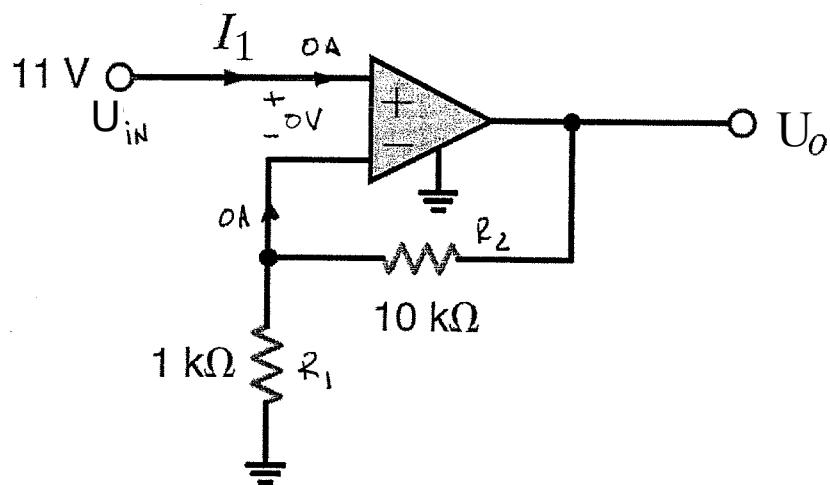


Figure P4.11

SOLUTION:

Basic non-inverting configuration,

$$\frac{U_o}{U_{in}} = 1 + \frac{R_2}{R_1} = 11 \Rightarrow U_o = 11U_{in}$$

$U_o = 121V$

Since $R_{in} = \infty$, $I_{in} = 0$

$I_1 = 0A$

2.4 Using the ideal op-amp assumptions, determine I_1 , I_2 , and I_3 in Fig. P4.12.

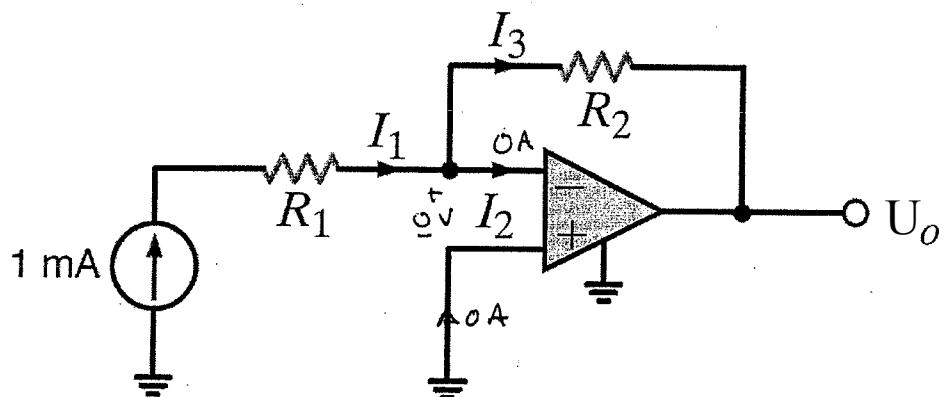


Figure P4.12

SOLUTION:

$$I_1 = 1 \text{ mA} \quad I_2 = 0 \text{ A} \quad (\text{ideal op-amp})$$

By KCL,

$$I_3 = I_1 - I_2$$

$$I_3 = 1 \text{ mA}$$

2.5 For the circuit in Fig. P4.17,

- (a) find U_o in terms of U_1 and U_2 .
- (b) If $U_1 = 2 \text{ V}$ and $U_2 = 6 \text{ V}$, find U_o .
- (c) If the op-amp supplies are $\pm 12 \text{ V}$, and $U_1 = 4 \text{ V}$, what is the allowable range of U_2 ?

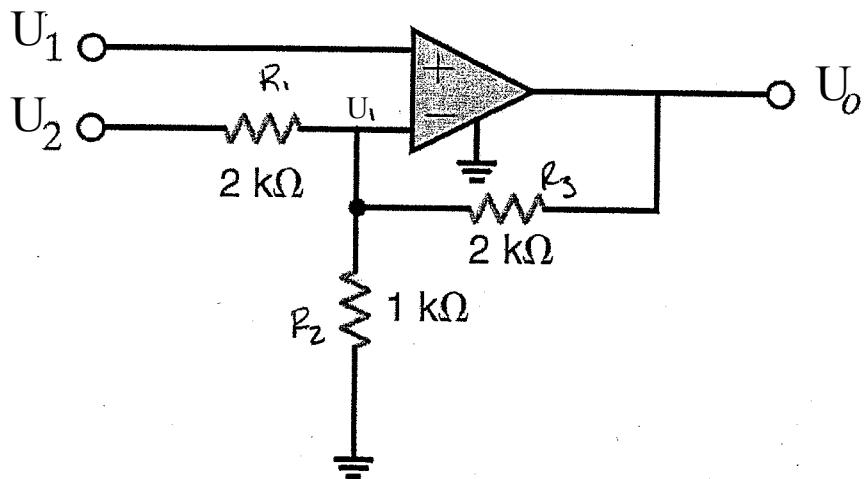


Figure P4.17

SOLUTION:

a) KCL at u_- input: (remember $u_+ = u_- = U_1$)

$$\frac{U_2 - U_1}{R_1} = \frac{U_1}{R_2} + \frac{U_1 - U_o}{R_3} \Rightarrow U_o = U_1 \left(1 + \frac{R_3}{R_1} + \frac{R_3}{R_2} \right) - U_2 \left(\frac{R_3}{R_1} \right)$$

$$U_o = 4U_1 - U_2$$

b) $U_o = 4(2) - 6$ U_o = 2 V

c) $|4(4) - U_2| \leq 12 \text{ V}$ 4 V ≤ U₂ ≤ 28 V

2.6 Find U_o in the circuit in Fig. P4.18 assuming the op-amp is ideal.

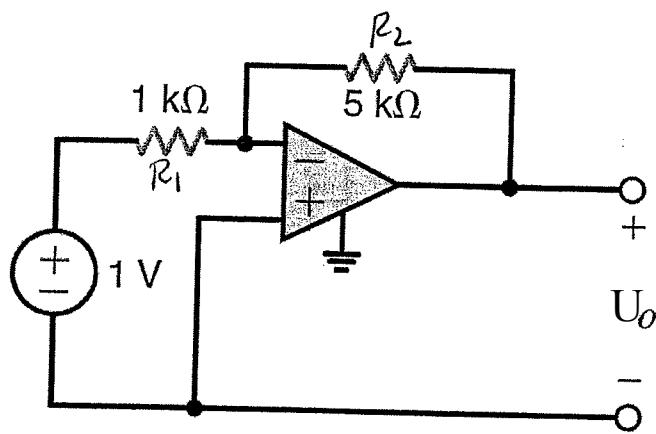


Figure P4.18

SOLUTION:

Basic inverting configuration.

$$U_o = U_s \left[- \frac{R_2}{R_1} \right] \quad U_o = 1 \left(- \frac{5000}{1000} \right) \quad \boxed{U_o = -5V}$$

2.7 The network in Fig. P4.19 is a current-to-voltage converter or transconductance amplifier. Find u_o / i_s for this network.

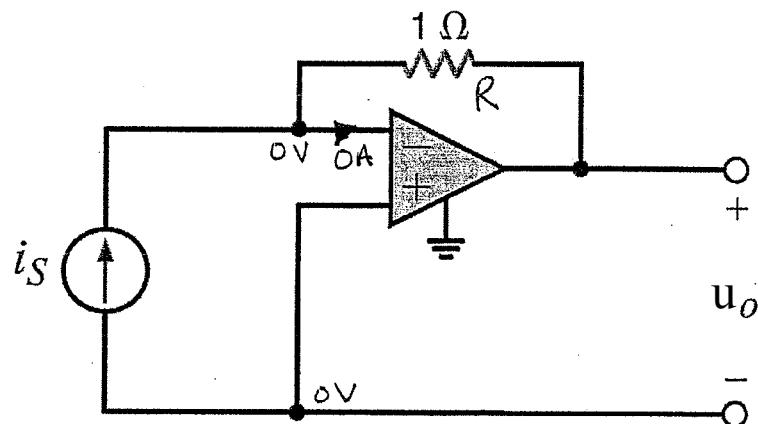


Figure P4.19

SOLUTION:

$$\text{KCL at } u_- \text{ input: } i_s = \frac{0 - u_o}{R}$$

$$\frac{u_o}{i_s} = -R$$

$$\boxed{\frac{u_o}{i_s} = -1}$$

2.8 Calculate the transfer function i_o/u_1 for the network shown in Fig. P4.20.

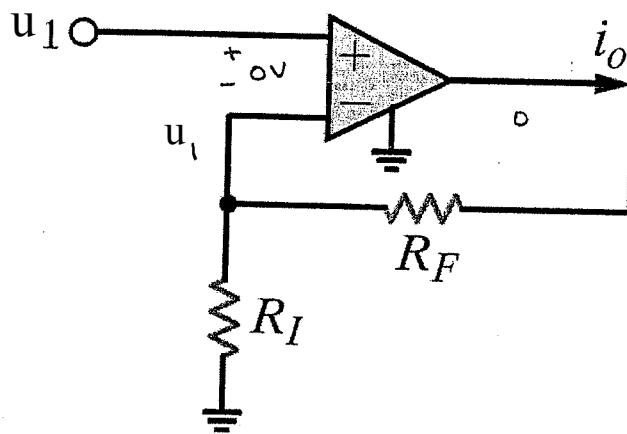


Figure P4.20

SOLUTION:

$$\text{KCL at } u_- \text{ input: } \frac{u_1}{R_I} = \frac{u_o - u_1}{R_F}$$

$$\frac{u_o}{u_1} = 1 + \frac{R_F}{R_I} = \frac{R_I + R_F}{R_I}$$

$$i_o = \frac{u_o}{R_I + R_F} = u_1 / R_I$$

$$\boxed{\frac{i_o}{u_1} = \frac{1}{R_I}}$$

2.9 Determine the relationship between u_1 and i_o in the circuit shown in Fig. P4.21.

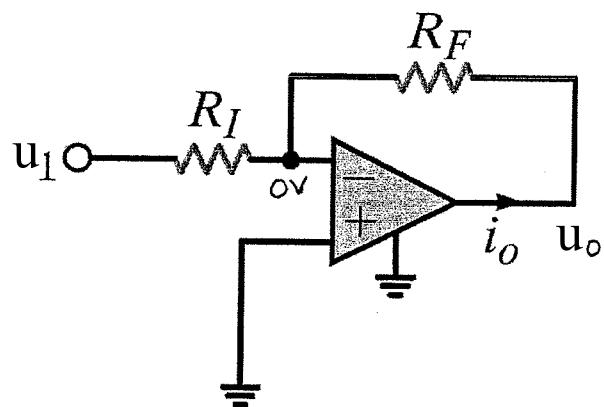


Figure P4.21

SOLUTION:

Basic inverting configuration:

$$\frac{u_o}{u_1} = - \frac{R_F}{R_I} \quad i_o = \frac{u_o}{R_F} = -u_1 / R_I$$

$$\frac{i_o}{u_1} = - \frac{1}{R_I}$$

2.10 Find U_o in the network in Fig. P4.22 and explain what effect R_1 has on the output.

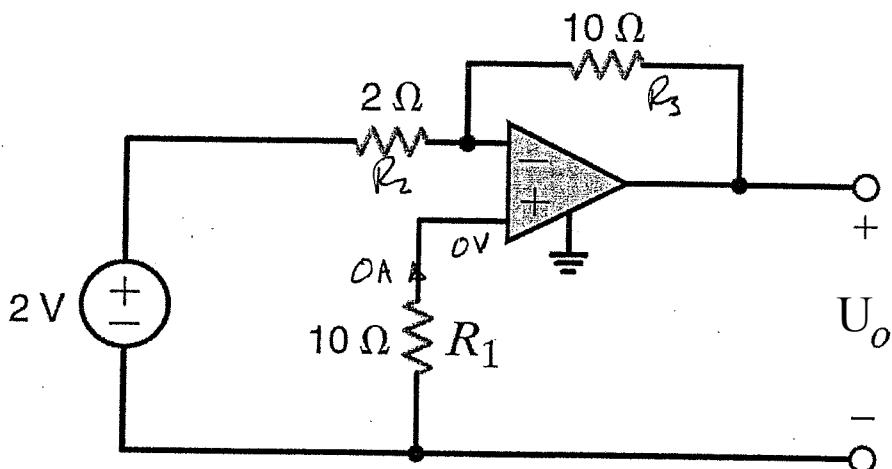


Figure P4.22

SOLUTION:

Since $i_{in} = 0$ for ideal opamp, voltage across $R_1 = 0$ and u_+ input is at 0V as well. Result is a basic inverting configuration.

$$u_o = -2 \left(\frac{R_3}{R_2} \right) \Rightarrow \boxed{U_o = -10V}$$

R_1 has no impact on the circuit at all!

2.11 Determine the expression for u_o in the network in Fig. P4.23.

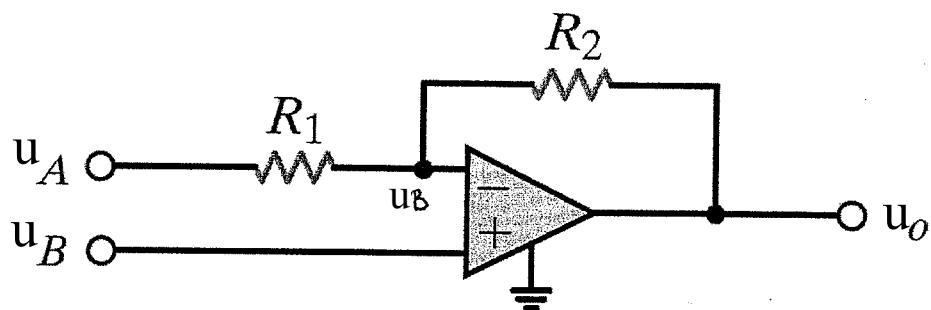


Figure P4.23

SOLUTION:

KCL at u₋ node:

$$\frac{u_A - u_B}{R_1} + \frac{u_o - u_B}{R_2} = 0$$

$$u_o = u_B \left(1 + \frac{R_2}{R_1} \right) - u_A \left(\frac{R_2}{R_1} \right)$$

2.12 Show that the output of the circuit in Fig. P4.24 is

$$U_o = \left[1 + \frac{R_2}{R_1} \right] U_1 - \frac{R_2}{R_1} U_2$$

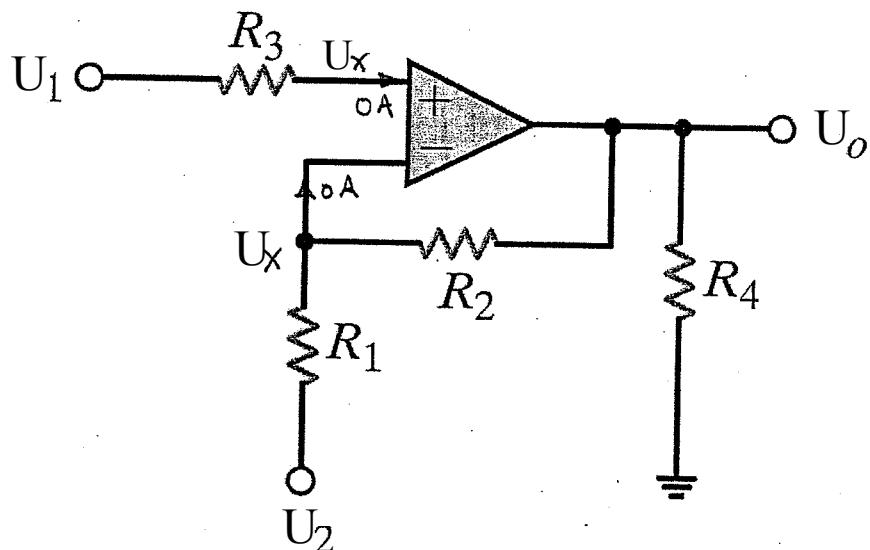


Figure P4.24

SOLUTION:

$$\text{KCL at } u_+ \text{ input: } \Rightarrow \frac{U_1 - U_x}{R_3} = 0 \Rightarrow U_1 = U_x$$

$$\frac{U_2 - U_x}{R_1} + \frac{U_o - U_x}{R_2} = 0 \quad U_o = U_x \left(1 + \frac{R_2}{R_1} \right) - U_2 \left(\frac{R_2}{R_1} \right)$$

$$U_o = \left[1 + \frac{R_2}{R_1} \right] U_1 - \frac{R_2}{R_1} U_2$$

2.13 Find U_o in the network in Fig. P4.25.

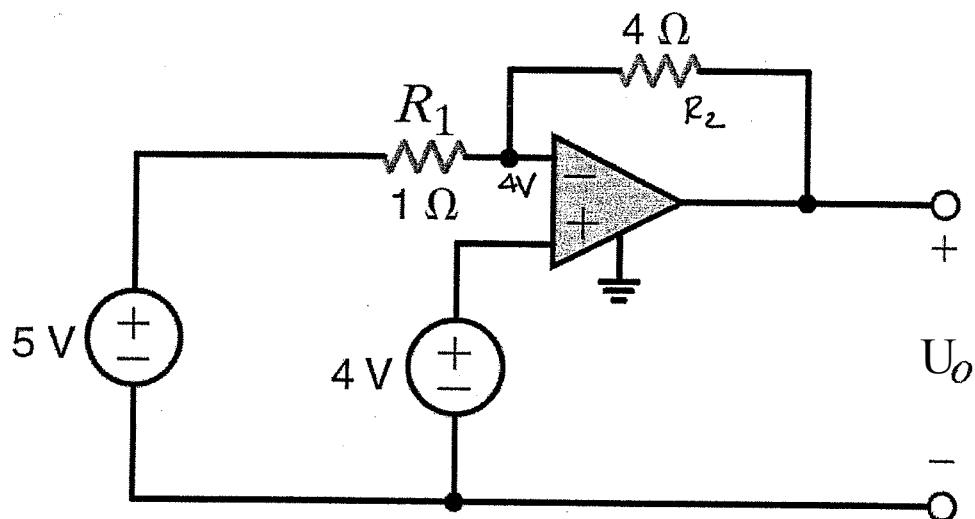


Figure P4.25

SOLUTION:

$$\text{KCL at } u_- \text{ input: } \frac{5 - 4}{R_1} + \frac{U_o - 4}{R_2} = 0$$

$$\boxed{U_o = 0 \text{ V}}$$

2.14 Find the voltage gain of the op-amp circuit shown in Fig. P4.26.

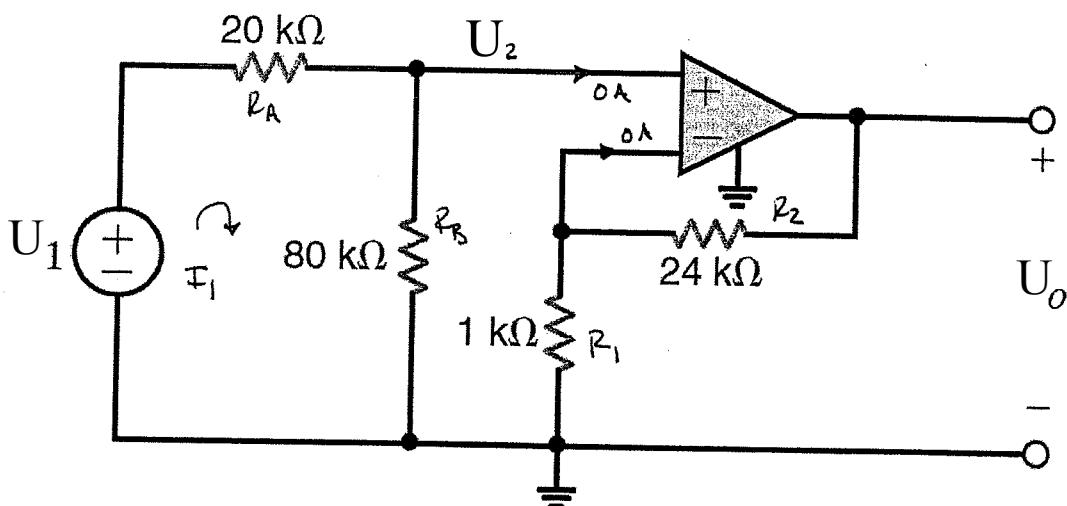


Figure P4.26

SOLUTION:

Two step solution: 1) Find U_2/U_1
2) Find U_o/U_2

1) Loop analysis:

$$U_1 = I_1 R_A + I_1 R_B \quad \text{and} \quad U_2 = I_1 R_B$$

$$I_1 = U_2 / R_B \quad \frac{U_2}{U_1} = \frac{R_B}{R_A + R_B} = 0.8$$

2) Op-amp is in basic non-inverting configuration.

$$\frac{U_o}{U_2} = 1 + \frac{R_2}{R_I} = 25$$

Overall gain is $\frac{U_o}{U_1} = \left(\frac{U_2}{U_1}\right)\left(\frac{U_o}{U_2}\right)$

$$\boxed{\frac{U_o}{U_1} = 20}$$

2.15 For the circuit in Fig. 4.27 find the value of R_1 that produces a voltage gain of 10.

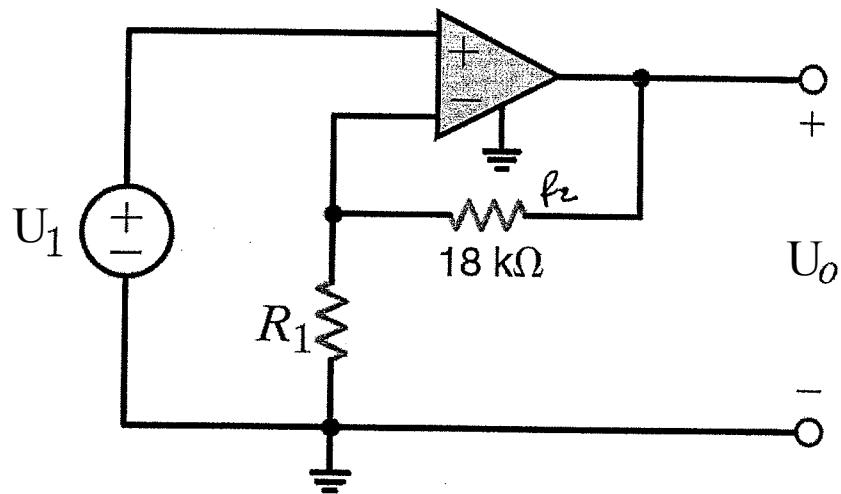


Figure P4.27

SOLUTION:

Basic non-inverting configuration:

$$\frac{U_o}{U_1} = 1 + \frac{R_2}{R_1} = 1 + \frac{18 \times 10^3}{R_1} = 10$$

$R_1 = 2 \text{ k}\Omega$

2.16 Determine the relationship between U_o and U_{in} in the circuit in Fig. P4.28.

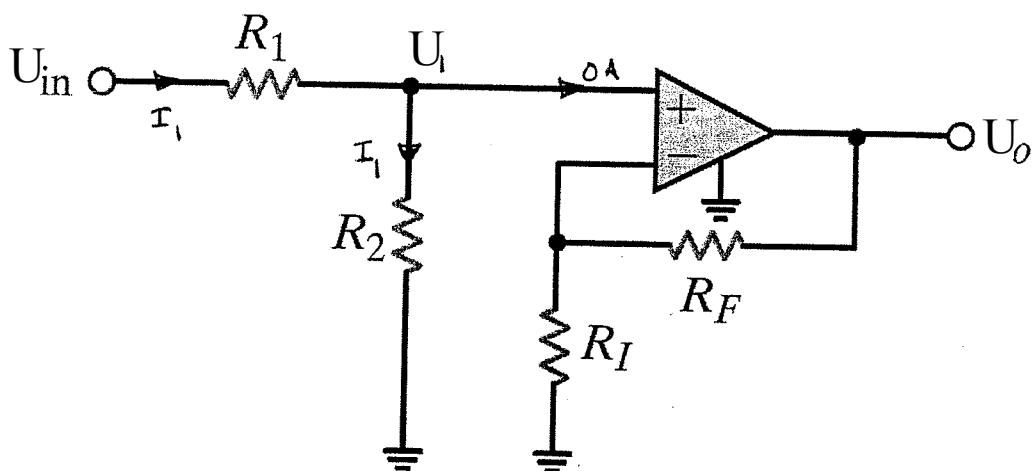


Figure P4.28

SOLUTION: Two step solution: 1) find U_1/U_{in}
2) find U_o/U_1

$$1) \quad U_{in} = I_1 R_1 + I_2 R_2 \quad U_1 = I_2 R_2 \quad \Rightarrow \quad \frac{U_1}{U_{in}} = \frac{R_2}{R_1 + R_2}$$

2) Opamp is in basic non-inverting configuration

$$\frac{U_o}{U_1} = 1 + \frac{R_F}{R_I}$$

Overall gain

$$\frac{U_o}{U_{in}} = \left(\frac{U_o}{U_1} \right) \left(\frac{U_1}{U_{in}} \right)$$


$$\boxed{\frac{U_o}{U_{in}} = \left(\frac{R_2}{R_1 + R_2} \right) \left(\frac{R_F + R_I}{R_I} \right)}$$

2.17 Design an op-amp-based circuit to produce the function

$$U_o = 5U_1 - 7U_2$$

SOLUTION:

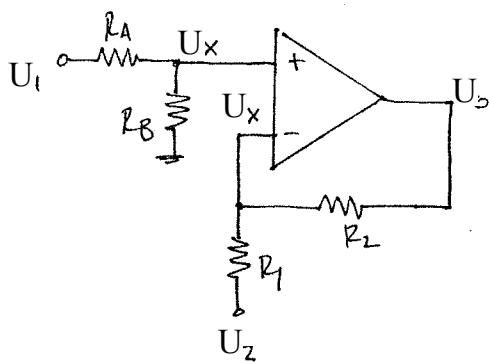Use both + & - inputs to get + & - gains.



KCL at u_+ input,

$$\frac{U_1 - U_x}{R_A} = \frac{U_x}{R_B} \Rightarrow \frac{U_x}{U_1} = \frac{R_B}{R_A + R_B}$$

KCL at u_- input

$$\frac{U_o - U_x}{R_2} = \frac{U_x - U_2}{R_1}$$

$$U_o = U_x \left(1 + \frac{R_2}{R_1} \right) - \frac{R_2}{R_1} U_2$$

$$U_o = U_1 \left(\frac{R_B}{R_A + R_B} \right) \left(1 + \frac{R_2}{R_1} \right) - \frac{R_2}{R_1} U_2$$

$$\frac{R_2}{R_1} = 7$$

$$\left(\frac{R_B}{R_A + R_B} \right) 8 = 5$$

$$\boxed{\text{Choose } R_1 = 1k\Omega \Rightarrow R_2 = 7k\Omega}$$

$$\boxed{\text{Choose } R_B = 5k\Omega \Rightarrow R_A = 3k\Omega}$$