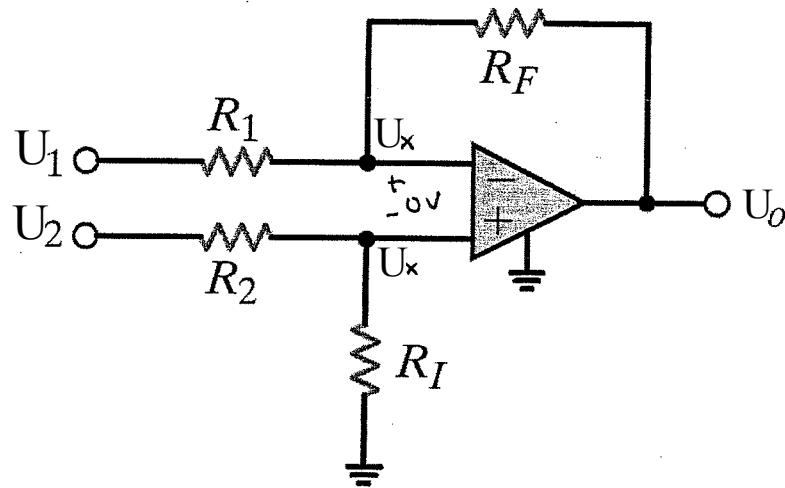


3.1 In the network in the figure derive the expression for  $U_o$  in terms of the inputs  $U_1$  and  $U_2$ .




SOLUTION:

$$\text{KCL at } U_+ \text{ input: } \frac{U_2 - U_x}{R_2} = \frac{U_x}{R_I} \Rightarrow U_x = U_2 \left( \frac{R_I}{R_I + R_2} \right)$$

$$\text{KCL at } U_- \text{ input: } \frac{U_1 - U_x}{R_1} = \frac{U_x - U_o}{R_F} \Rightarrow U_o = U_x \left( 1 + \frac{R_F}{R_1} \right) - \frac{R_F}{R_1} U_1$$

$$U_o = U_2 \left( \frac{R_I}{R_I + R_2} \right) \left( \frac{R_1 + R_F}{R_1} \right) - \frac{R_F}{R_1} U_1$$

3.2 Find  $U_o$  in the circuit

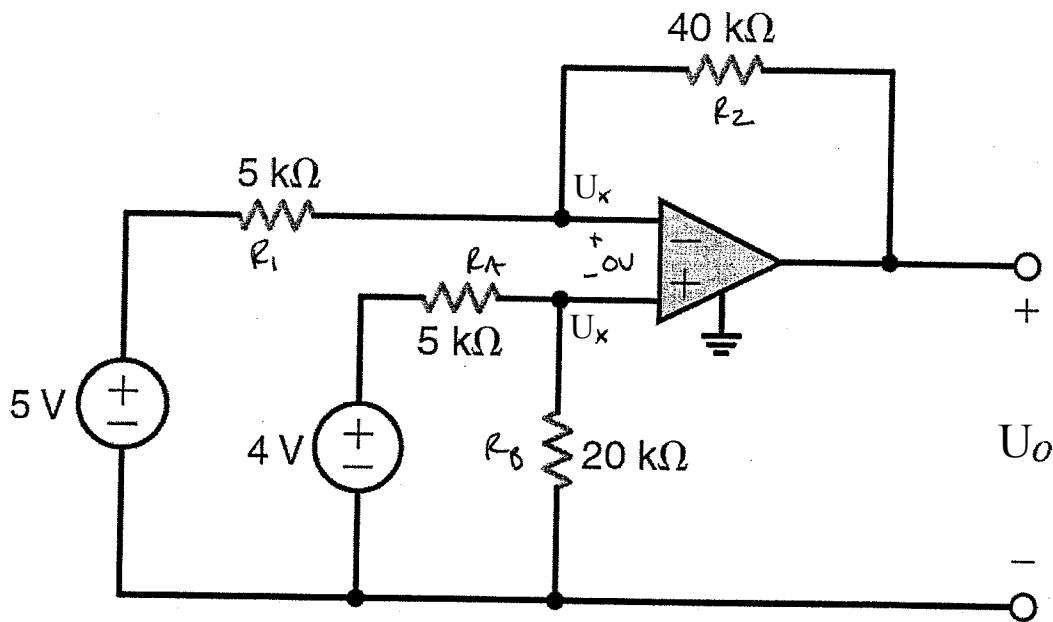

SOLUTION:

$$\text{KCL at } U_- \text{ input: } \frac{5 - U_x}{R_1} = \frac{U_x - U_o}{R_2} \Rightarrow U_x = 5 \left( \frac{R_2}{R_1 + R_2} \right) + U_o \left( \frac{R_1}{R_1 + R_2} \right)$$


$$\text{KCL @ } U_+ \text{ input: } \frac{4 - U_x}{R_A} = \frac{U_x}{R_B} \Rightarrow U_x = \frac{4 R_B}{R_A + R_B}$$

$$5 \left( \frac{R_2}{R_1 + R_2} \right) + U_o \left( \frac{R_1}{R_1 + R_2} \right) = \frac{4 R_B}{R_A + R_B}$$

$$U_o = \left( \frac{4 R_B}{R_A + R_B} - \frac{5 R_2}{R_1 + R_2} \right) \frac{R_1 + R_2}{R_1}$$

$$U_o = -11.2 \text{ V}$$

3.3 Find  $U_o$  in the circuit

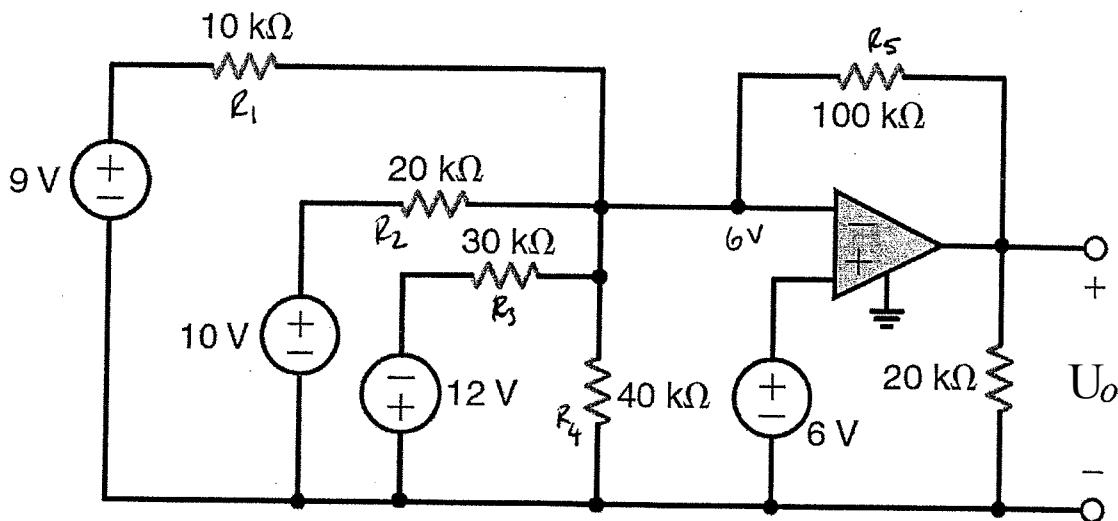


SOLUTION:

$$\text{KCL at } U_- \text{ input: } \frac{9-6}{R_1} + \frac{10-6}{R_2} + \frac{-12-6}{R_3} = \frac{6}{R_4} + \frac{6-U_o}{R_5}$$

$$\frac{3}{10^4} + \frac{4}{2 \times 10^4} - \frac{18}{3 \times 10^4} = \frac{6}{4 \times 10^4} + \frac{6}{10^5} - \frac{U_o}{10^5}$$

$$U_o = 31V$$

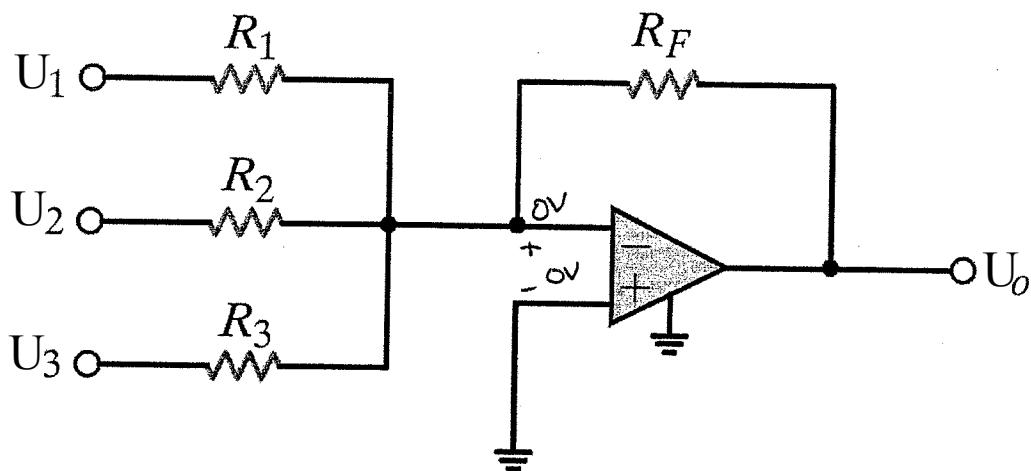**3.4** Determine the expression for the output voltage,  $U_o$ , of the inverting summer circuit




**SOLUTION:**

$$\text{KCL at } U_- \text{ input: } \frac{U_1 - 0}{R_1} + \frac{U_2 - 0}{R_2} + \frac{U_3 - 0}{R_3} = \frac{0 - U_o}{R_F}$$

$$U_o = -\frac{R_F}{R_1}U_1 - \frac{R_F}{R_2}U_2 - \frac{R_F}{R_3}U_3$$

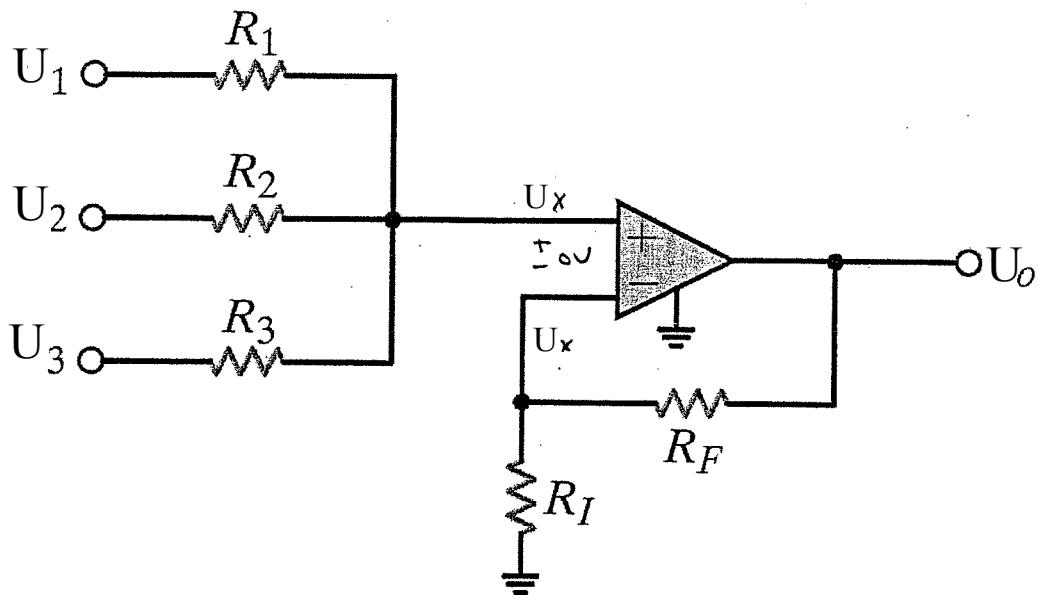**3.5** Determine the output voltage,  $U_o$ , of the noninverting averaging circuit




---

SOLUTION:


$$\text{KCL at } U_+ \text{ input: } \frac{U_1 - U_x}{R_1} + \frac{U_2 - U_x}{R_2} + \frac{U_3 - U_x}{R_3} = 0$$

$$\text{KCL at } U_- \text{ input: } \frac{U_o - U_x}{R_F} = \frac{U_x}{R_I} \quad U_x = U_o \left( \frac{R_I}{R_F + R_I} \right)$$

Eliminate  $U_x$ ,

$$U_o = \left( \frac{R_I + R_F}{R_I} \right) \left[ \frac{R_2 R_3 U_1 + R_1 R_3 U_2 + R_1 R_2 U_3}{R_1 R_2 + R_2 R_3 + R_1 R_3} \right]$$

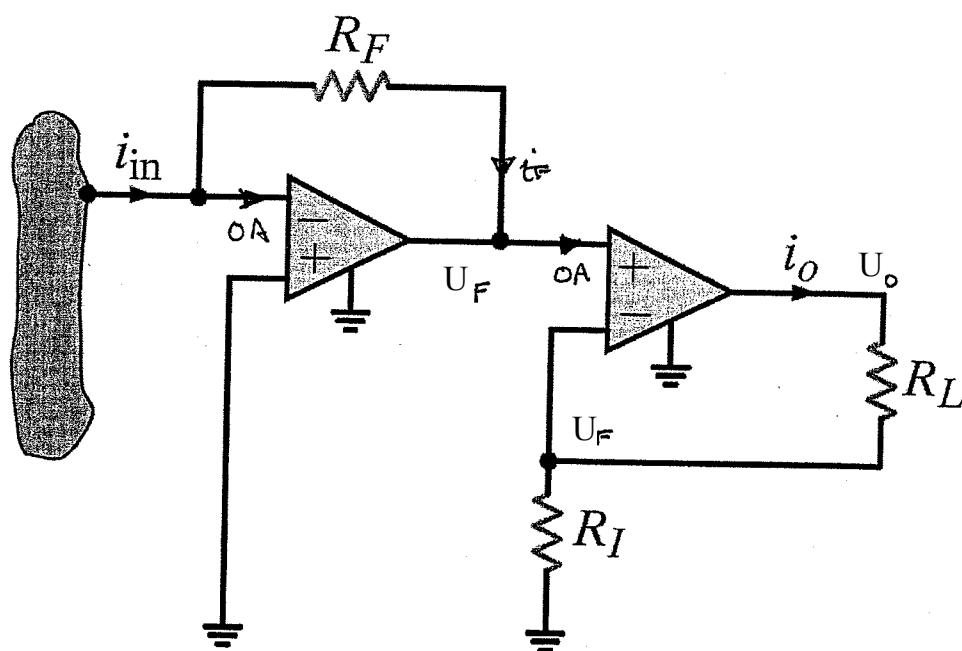3.6 Find the input/output relationship for the current amplifier



SOLUTION: KCL at  $U_-$  input of 1<sup>st</sup> op amp.


$$i_{in} = \frac{0 - U_F}{R_F} \quad U_F = -R_F i_{in}$$

2<sup>nd</sup> op-amp in classic inverting configuration

$$U_o = U_F \left( 1 + \frac{R_L}{R_I} \right) \quad i_o = \frac{U_o - U_-}{R_L} = \frac{U_F}{R_I}$$

$$\frac{i_o}{i_{in}} = \left( \frac{U_F}{i_{in}} \right) \left( \frac{i_o}{U_F} \right) \quad \frac{i_o}{i_{in}} = -\frac{R_F}{R_I}$$

3.7 Find  $U_o$  in the circuit

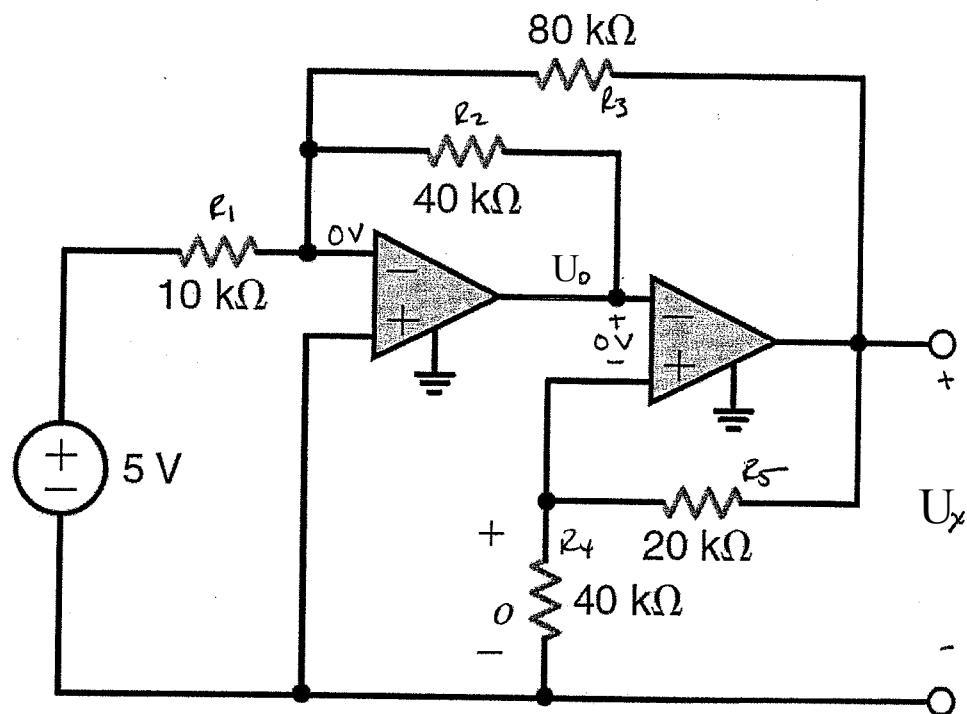

SOLUTION:

$$\text{KCL at } U_- \text{ of 1st op amp: } \frac{5}{R_1} + \frac{U_o}{R_2} + \frac{U_x}{R_3} = 0 \Rightarrow U_x = -\frac{R_3}{R_1}(s) - \frac{R_3}{R_2}U_o$$

$$\text{KCL at } U_+ \text{ of 2nd op amp: } \frac{U_o}{R_4} + \frac{U_o - U_x}{R_5} = 0 \Rightarrow U_x = U_o \left(1 + \frac{R_5}{R_4}\right)$$


Put in numbers,

$$U_x = -40 - 2U_o \quad \& \quad U_x = 1.5U_o$$

Eliminate  $U_x$ ,

$$U_o = -11.43 \text{ V}$$

**3.8** Find  $U_o$  in the circuit

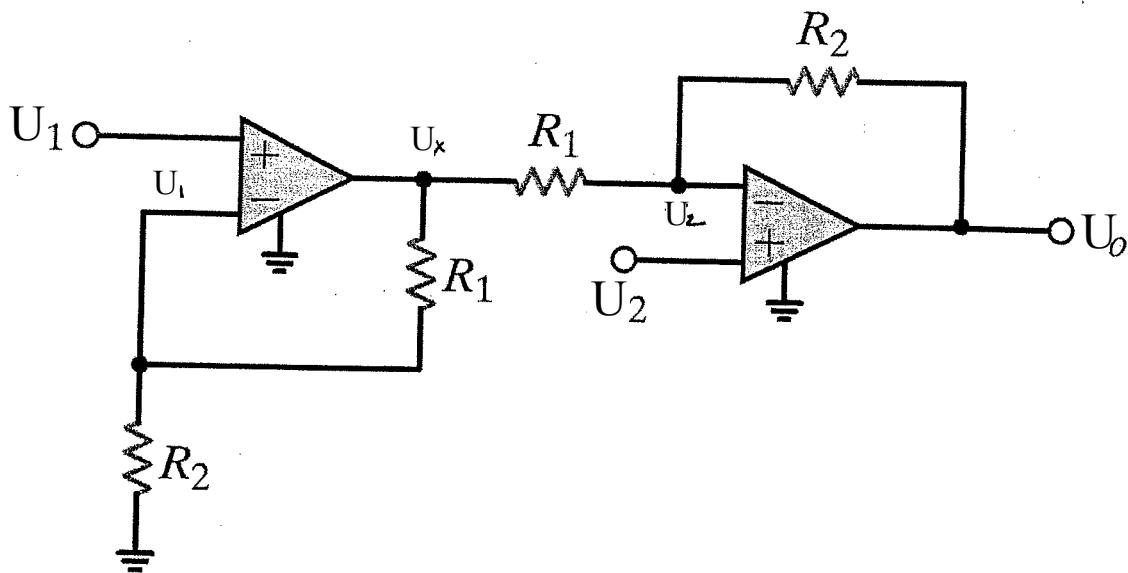

**SOLUTION:**

1<sup>st</sup> Op amp in basic non-inverting configuration:


$$\frac{U_x}{U_1} = 1 + \frac{R_1}{R_2} \Rightarrow U_x = U_1 \left( 1 + \frac{R_1}{R_2} \right)$$

KCL at  $U_-$  of 2<sup>nd</sup> op amp:  $\frac{U_x - U_2}{R_1} + \frac{U_o - U_2}{R_2} = 0$

$$U_x = U_2 \left( 1 + \frac{R_2}{R_1} \right) - \frac{R_2}{R_1} U_o$$

$$U_o = \left( 1 + \frac{R_2}{R_1} \right) (U_2 - U_1)$$

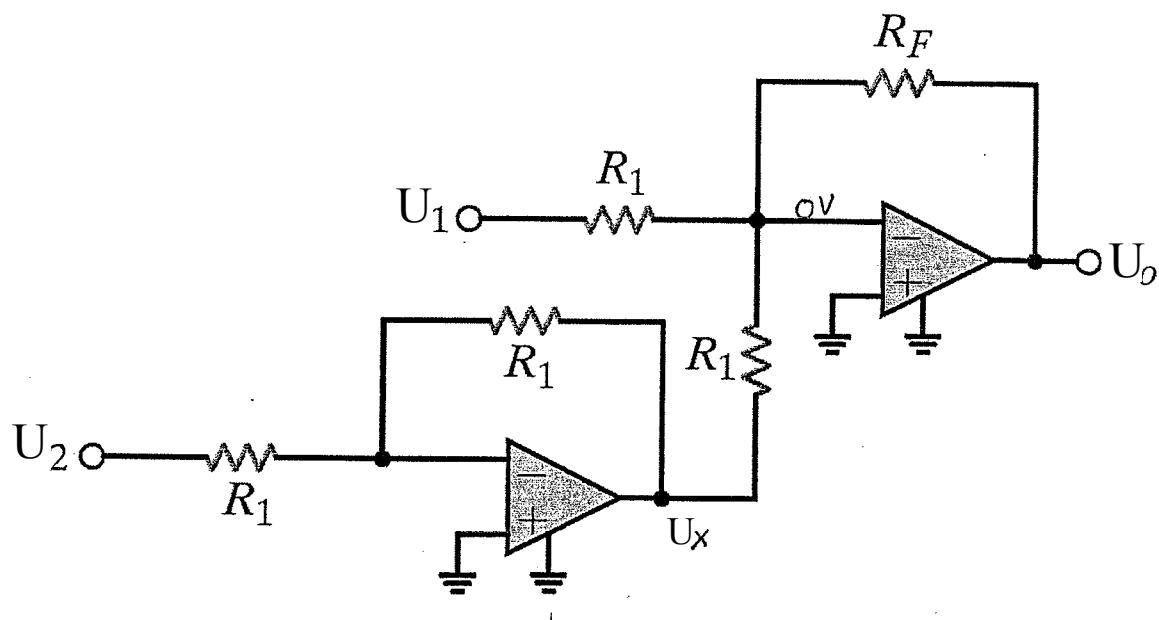3.9 Find the expression for  $U_o$  in the differential amplifier circuit




---

SOLUTION:


Op-amp in classic inverting configuration:

$$U_x = -\frac{R_1}{R_1} U_2 \quad U_x = -U_2$$

KCL at  $U_-$  of 2<sup>nd</sup> opamp:  $\frac{U_1}{R_1} + \frac{U_x}{R_1} + \frac{U_o}{R_F} = 0$

$$U_o = \frac{R_F}{R_1} [U_2 - U_1]$$

3.10 Find  $U_o$  in the circuit

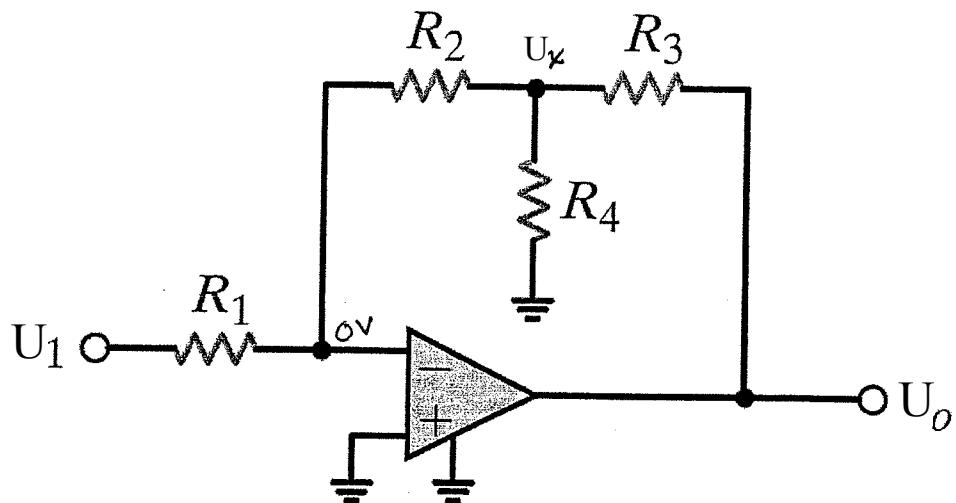


SOLUTION:

$$\text{KCL at } U_- \text{ input: } \frac{U_1}{R_1} + \frac{U_x}{R_2} = 0 \quad U_x = -\frac{R_2}{R_1} U_1$$

$$\text{KCL at } U_x \text{ node: } \frac{U_x}{R_2} + \frac{U_x}{R_4} + \frac{U_x - U_o}{R_3} = 0 \quad U_o = U_x \left( \frac{R_3}{R_2} + \frac{R_3}{R_4} + 1 \right)$$

$$U_o = U_1 \left[ 1 + \frac{R_3}{R_2} + \frac{R_3}{R_4} \right] \left( -\frac{R_2}{R_1} \right)$$

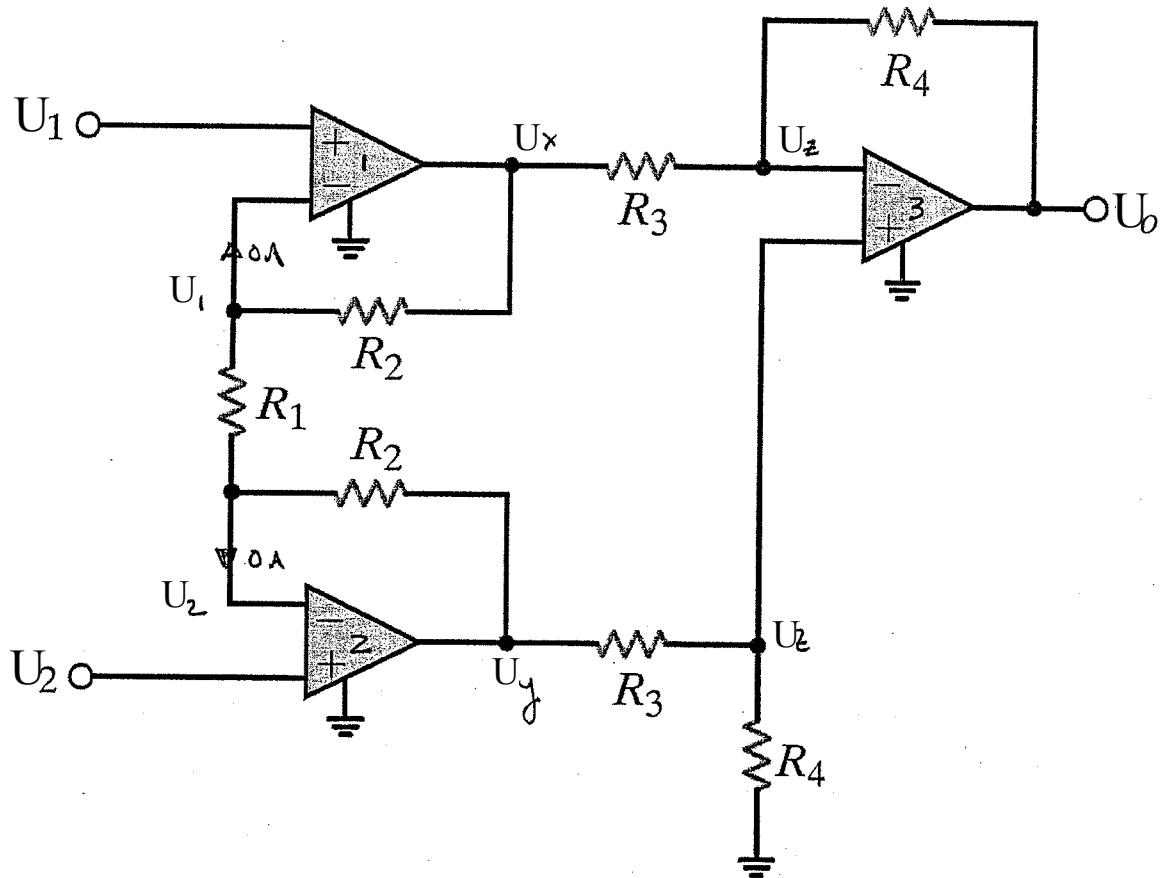3.11 Find the output voltage,  $U_o$ , in the circuit



SOLUTION:

$$\text{KCL at } U_{-} \text{ of opamp 1: } \frac{U_x - U_1}{R_2} = \frac{U_1 - U_2}{R_1} \Rightarrow U_x = U_1 \left( 1 + \frac{R_2}{R_1} \right) - \frac{R_2}{R_1} U_2$$

$$\text{KCL at } U_{-} \text{ of opamp 2: } \frac{U_y - U_2}{R_2} = \frac{U_2 - U_1}{R_1} \Rightarrow U_y = U_2 \left( 1 + \frac{R_2}{R_1} \right) - \frac{R_2}{R_1} U_1$$

$$\text{KCL at } U_{+} \text{ of opamp 3: } \frac{U_y - U_z}{R_3} = \frac{U_z}{R_4} \Rightarrow U_z = U_y \left( \frac{R_4}{R_3 + R_4} \right)$$

$$\text{KCL at } U_{-} \text{ of opamp 3: } \frac{U_x - U_z}{R_3} + \frac{U_o - U_z}{R_4} = 0 \Rightarrow U_o = U_z \left( 1 + \frac{R_4}{R_3} \right) \cdot U_x \frac{R_4}{R_3}$$


$$U_o = \frac{R_4}{R_3} \left( 1 + 2 \frac{R_2}{R_1} \right) (U_2 - U_1)$$

**3.12** Given a box of  $10\text{-k}\Omega$  resistors and an op-amp, design a circuit that will have an output voltage of


$$U_o = -2U_1 - 4U_2$$

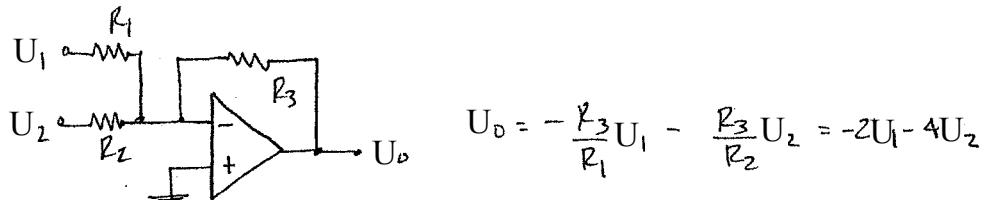**SOLUTION:**

Since signs on gains associated with  $U_1$  &  $U_2$  are both negative, a simple summer will suffice.



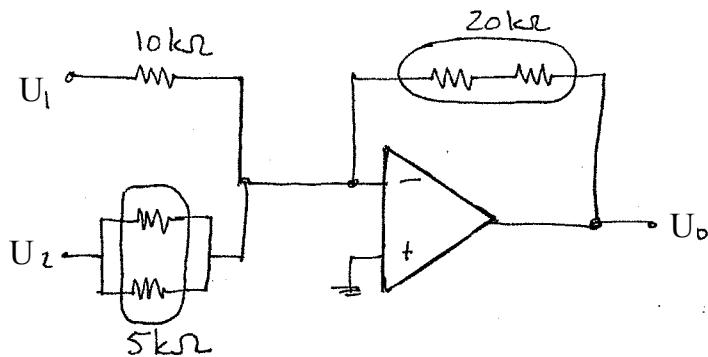
The following circuit with all resistors =  $10\text{k}\Omega$  works.



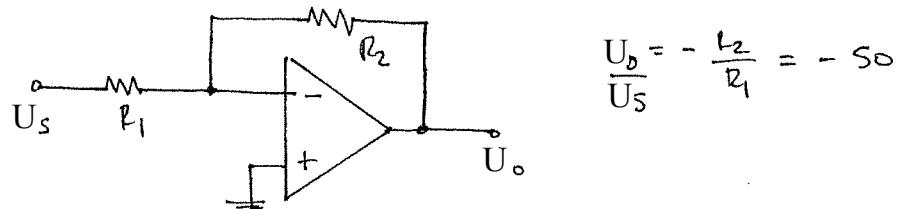3.13 Design an op-amp circuit that has a gain of  $-50$  using resistors no smaller than  $1 \text{ k}\Omega$ .

SOLUTION:

Since gain is negative, use inverting configuration:




$$\text{Choose } R_1 = 2 \text{ k}\Omega \Rightarrow R_2 = 100 \text{ k}\Omega$$

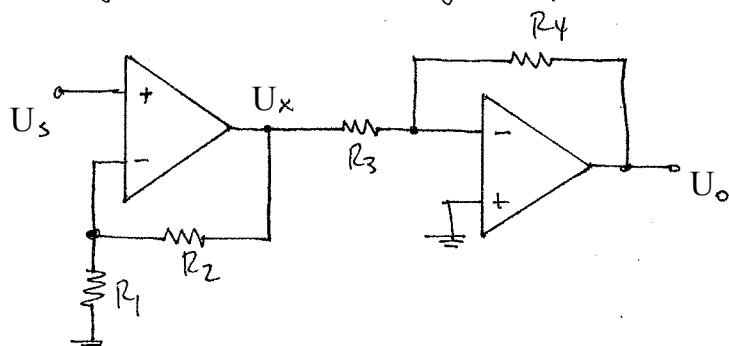**3.14** Design a two-stage op-amp network that has a gain of  $-50,000$  while drawing no current into its input terminal. Use no resistors smaller than  $1 \text{ k}\Omega$ .

SOLUTION:

for no input current, a non-inverting configuration is needed  
for negative, one inverting stage is needed.



$$\frac{U_x}{U_s} = 1 + \frac{R_2}{R_1} \quad \frac{U_o}{U_x} = -\frac{R_4}{R_3} \quad \frac{U_o}{U_s} = -\frac{R_4}{R_3} \left(1 + \frac{R_2}{R_1}\right)$$

Choose  $\frac{U_x}{U_s} = 250$  and  $\frac{U_o}{U_x} = -200$   $R_1 = R_3 = 2 \text{ k}\Omega$

$R_2 = 498 \text{ k}\Omega$


$R_4 = 400 \text{ k}\Omega$

**3.15** Design an op-amp circuit that has the following input/output relationship:

$$U_o = -5U_1 + 0.5U_2$$

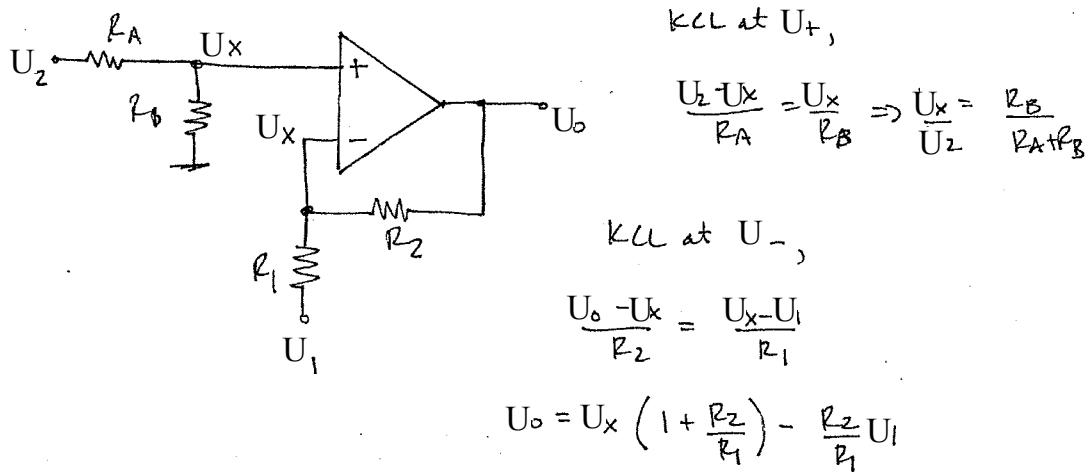**SOLUTION:**

A single op-amp will do if we use both + & - inputs.



$$U_o = \left( 1 + \frac{R_2}{R_1} \right) \left( \frac{R_B}{R_A + R_B} \right) U_2 - \frac{R_2}{R_1} U_1$$

$$\text{So, } \frac{R_2}{R_1} = 5$$

$$\text{Now, } \frac{R_B}{R_A + R_B} = \frac{1}{2}$$

Choose  $R_1 = 1\text{k}\Omega \Rightarrow R_2 = 5\text{k}\Omega$


Choose  $R_B = 1\text{k}\Omega \Rightarrow R_A = 11\text{k}\Omega$

**3.16** Design an op-amp-based circuit to produce the function

$$U_o = 5U_1 - 4U_2$$

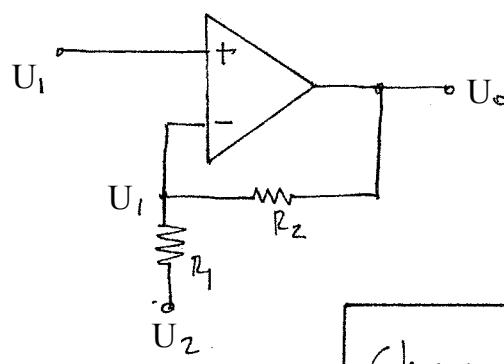**SOLUTION:**

To get + & - gains, we can use both + & - inputs




KCL @ U- input,

$$\frac{U_o - U}{R_2} = \frac{U_1 - U_2}{R_1}$$

$$U_o = U_1 \left( 1 + \frac{R_2}{R_1} \right) - \frac{R_2}{R_1} U_2$$

Choose  $R_1 = 5k\Omega \Rightarrow R_2 = 20k\Omega$

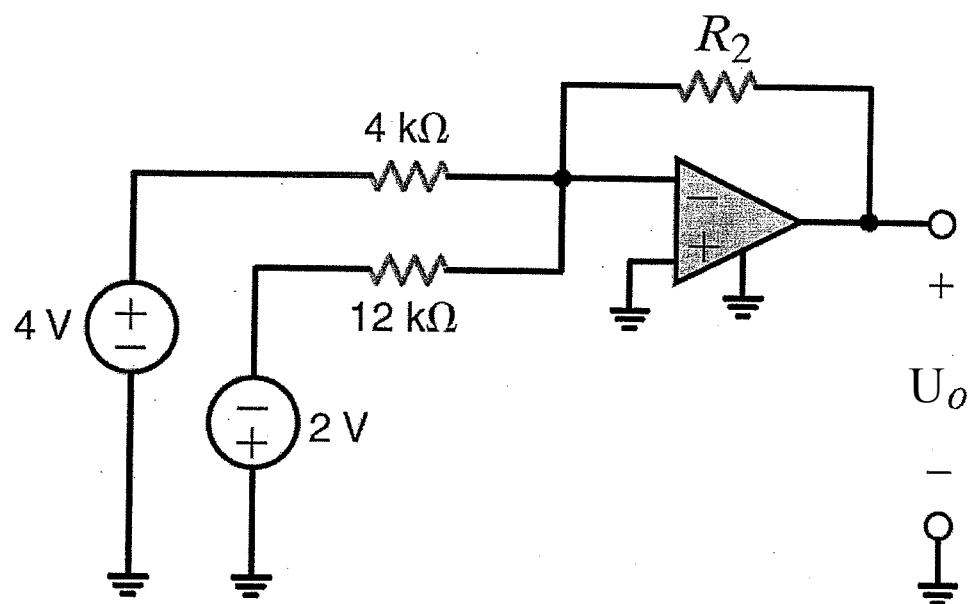- 3.17 Given the summing amplifier shown in the figure select the values of  $R_2$  that will produce an output voltage of  $-3 \text{ V}$ .




SOLUTION: For summing amp:

$$U_o = - \left( \frac{R_2}{4000} \right) 4 - \left( \frac{R_2}{12000} \right) (2) = -3$$

$R_2 = 2.57 \text{ k}\Omega$

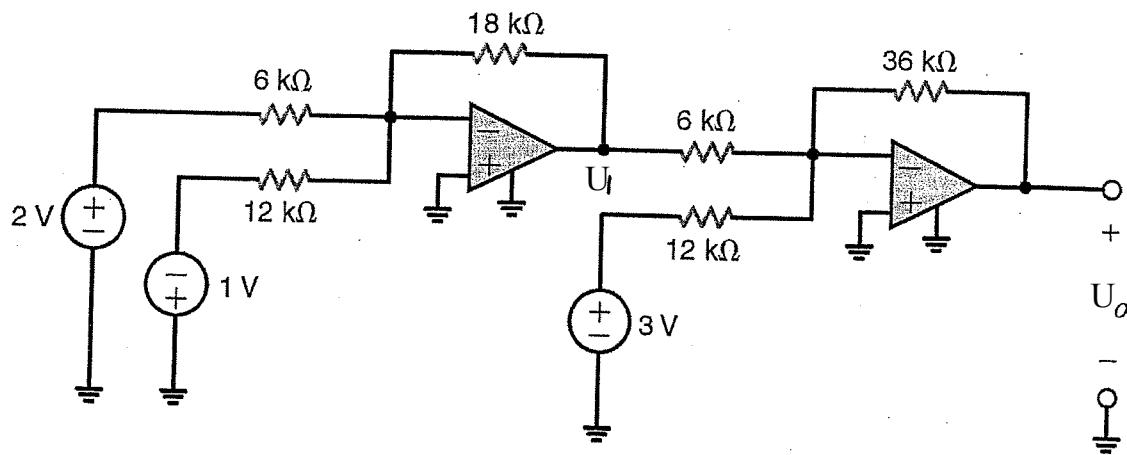**3.18** Determine the output voltage  $U_o$  of the summing op-amp circuit



**SOLUTION:**

$$U_1 = -2 \left( \frac{18 \times 10^3}{6 \times 10^3} \right) + 1 \left( \frac{18 \times 10^3}{12 \times 10^3} \right) = -4.5 \text{ V}$$

$$U_o = -U_1 \left( \frac{36 \times 10^3}{6 \times 10^3} \right) - 3 \left( \frac{36 \times 10^3}{12 \times 10^3} \right) \Rightarrow \boxed{U_o = 18 \text{ V}}$$