

Koaksialen kabel je tokovna zanka enosmernega toka $I = 500 \text{ A}$. Tok žile polmera $r_0 = 6 \text{ mm}$ se v celoti vrača po plašču polmerov $r_n = 1 \text{ cm}$ in $r_z = 1.1 \text{ cm}$. Žila in plašč sta iz bakra. Določite magnetni pretok v žili in v dielektriku kabla na dolžini $l = 2 \text{ km}$!

Rešitev:

$$B_1 = \mu_0 \frac{J}{2} r = \mu_0 \frac{I}{2\pi r_0^2} r$$

$$\Phi_1 = \int_{A_1} \vec{B}_1 d\vec{A}_1 = \int_0^{r_0} \mu_0 \frac{I}{2\pi r_0^2} r \cdot l dr = \mu_0 \frac{I}{4\pi} \cdot l$$


$$\Phi_1 = 4\pi \cdot 10^{-7} \frac{500}{4\pi} 2 \cdot 10^{-3} = 0.1 \text{ Wb}$$

$$B_2 = \mu_0 \frac{I}{2\pi r}$$

$$\Phi_2 = \int_{A_2} \vec{B}_2 \cdot d\vec{A}_2 = \int_{r_0}^{r_z} \mu_0 \frac{I}{2\pi r} \cdot l dr = \mu_0 \frac{I}{4\pi} \cdot l \ln \frac{r_z}{r_0}$$

$$\Phi_2 = 4\pi \cdot 10^{-7} \frac{500}{2\pi} 2 \cdot 10^3 \ln \frac{10}{6} = 0.102 \text{ Wb}$$

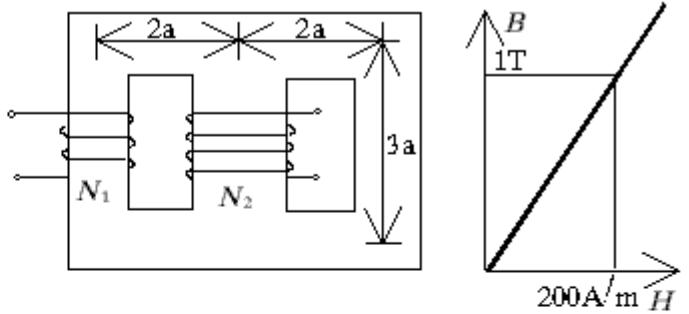Dano je magnetno jedro z linearno magnetilno krivuljo, $N_1 = 250$, $N_2 = 300$, $a = 10 \text{ cm}$, $A = 10 \text{ cm}^2$. Izračunajte medsebojno induktivnost navitij!



Rešitev:

$$L_{12} = N_1 \frac{\Phi_{21}}{I_2} = N_1 \frac{\Phi_2 / 2}{I_2} = N_1 \frac{\Phi_2}{2I_2}$$

$$I_2 N_2 = R_m \Phi_2$$


$$L_{12} = \frac{N_1 N_2}{2 R_m}$$

$$R_m = \frac{1}{\mu} \cdot \frac{3a}{A} + \frac{1}{2} \cdot \frac{1}{\mu} \cdot \frac{7a}{A} = \frac{13a}{2\mu A}$$

$$L_{12} = \mu N_1 N_2 \frac{A}{13a}$$

$$L_{12} = \frac{1}{200} \cdot 250 \cdot 300 \frac{10 \cdot 10^{-4}}{13 \cdot 0.1} = 0.288 \text{ H}$$

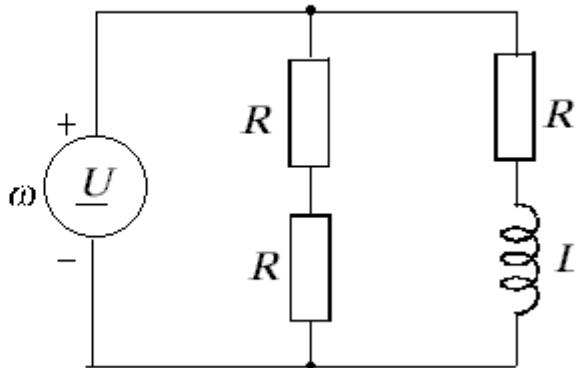V narisani vezavi je kazalec efektivne vrednosti napetosti izvora $\underline{U} = 20V$ in upornost uporov $R = 10\Omega$. Skozi obe vzporedni veji tečeta toka enakih efektivnih vrednosti. Določite kompleksor moči in navidezno moč vezave! Zapišite trenutne vrednosti tokov v vezju!



Rešitev:

$$X_L = \sqrt{Z^2 - R^2} = \sqrt{20^2 - 10^2} = 10\sqrt{3} = 17.3\Omega$$

$$\underline{I}_1 = \frac{\underline{U}}{2R} = \frac{20}{20} = 1A$$

$$\underline{I}_2 = \frac{\underline{U}}{R + jX} = \frac{20}{10(1 + j\sqrt{3})} = \frac{2}{1 + j\sqrt{3}} = \frac{1}{2}(1 - j\sqrt{3})$$

$$\underline{I} = \frac{1}{2}(3 - j\sqrt{3})$$


$$\underline{S} = \underline{U} \underline{I}^* = 20 \frac{1}{2}(3 + j\sqrt{3}) = (30 + j17.3) \text{ VA}$$

$$S = UI = 10\sqrt{12} = 34.64 \text{ VA}$$


$$i_1(t) = \sqrt{2} \cos \omega t \text{ A}$$

$$i_2(t) = \sqrt{2} \cos(\omega t - \pi/3) \text{ A}$$
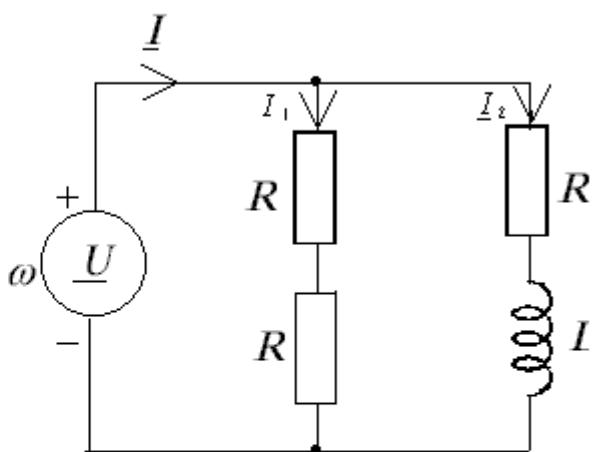
$$i(t) = 2.45 \cos(\omega t - \pi/6) \text{ A}$$



Določite vhodno impedanco danega vezja!

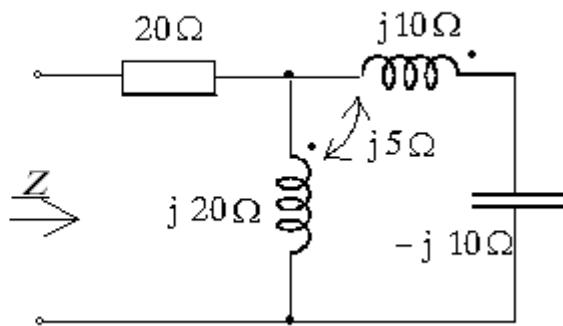

Rešitev:

$$\underline{U} = (20 + j20)\underline{I}_1 - (j20 + j5)\underline{I}_2$$

$$0 = -(j20 + j5)\underline{I}_1 + (j20 + j10 + 2 \cdot j5 - j15) - \underline{I}_2$$

$$\underline{U} = (20 + j20)\underline{I}_1 - j25\underline{I}_2$$


$$0 = -j25\underline{I}_1 + j25\underline{I}_2$$

$\underline{I}_2 = \underline{I}_1$: po veji $j20\Omega$ ni toka in


$$\underline{Z} = (20 + j10 - j15) = (20 - j5)\Omega$$

$$\underline{U} = (20 + j20)\underline{I}_1 - j25\underline{I}_1 = (20 - j5)\underline{I}_1$$
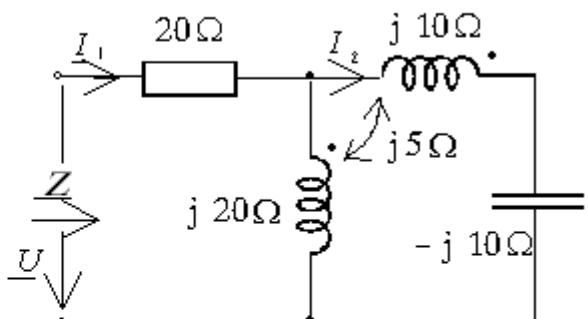
$$\underline{Z} = \frac{\underline{U}}{\underline{I}_1} = (20 - j5)\Omega$$




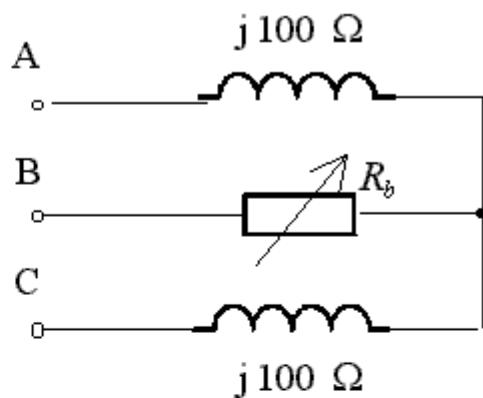Pri kateri upornosti R_b bo delovna moč na bremenu največja in kolikšna je ta moč? $U_m = 400 \text{ V}$. (Napotek: med priključnima sponkama upora uporabite Théveninov teorem.)





Rešitev:

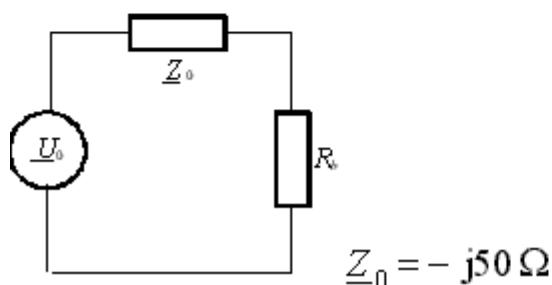Vezje spremenimo v Theveninov generator $\underline{U}_0, \underline{Z}_0$



$$\underline{Z}_0 = -j50 \Omega$$

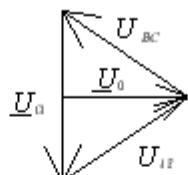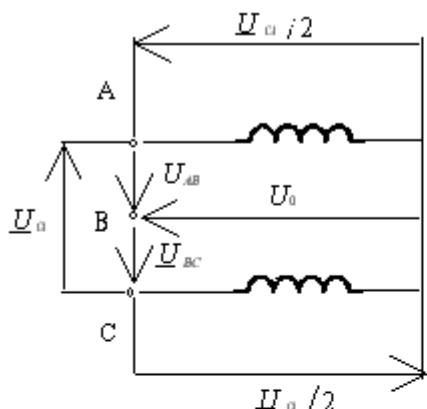

$$\underline{U}_0 = \frac{\underline{U}_{CA}}{2} + \underline{U}_{AB} = \frac{\sqrt{3}}{2} 400 \text{ V}$$

Maksimalna moč na bremenu je pri $R_b = |\underline{Z}_0| = 50 \Omega$ in je

$$P_{\max} = \frac{U_0^2}{2(R_b + |\underline{Z}_0|)}$$

$$Z_0 = R_0 + jX_0. \text{ V našem primeru } R_0 = 0$$

$$P_{\max} = \frac{3 \cdot 400^2}{4} \cdot \frac{1}{2 \cdot 50} = 1200 \text{ W}$$