

Premi vodnik, ki vodi tok  $i$ , se lomi pod kotom  $\alpha$ . Kolikšna je sila  $d\vec{F}/dl$  na vodnik v točki T, ki je za  $x$  oddaljena od točke preloma?

**Rešitev:**

$$d\vec{F} = i d\vec{l} \times \vec{B}$$


$$\vec{B} = \vec{e}_y \frac{\mu_0 i}{4\pi} (\cos \alpha'_1 - \cos \alpha'_2)$$

$$\alpha'_1 = 0, \quad \cos \alpha'_1 = 1$$

$$\alpha'_2 = \pi - \alpha, \quad \cos \alpha'_2 = -\cos \alpha$$

$$r = x \sin \alpha'_2 = x \sin \alpha$$
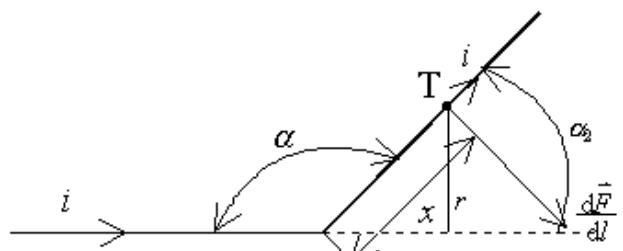
$$\frac{dF}{dl} = \mu_0 \frac{i^2}{4\pi x} \left( \frac{1}{\sin \alpha} + \tan \alpha \right)$$



Okrog premega linijskega vodnika s tokom  $i = 10 \text{ A}$  je koncentrično postavljena feromagnetna cev polmerov  $r_n = 1 \text{ cm}$  in  $r_z = 2 \text{ cm}$  v dolžini 10 m. Kolikšen je magnetni pretok v steni feromagnetne cevi, ki ima magnetilno karakteristiko  $B=100 \mu_0 H$ ?

**Rešitev:**

$$\Phi = \int_A \vec{B} \cdot d\vec{A}$$

$$\vec{B} = \vec{e}_\varphi 100 \mu_0 \frac{i}{2\pi}$$

$$d\vec{A} = \vec{e}_\varphi l dr$$

$$\Phi = \int_{r_n}^{r_z} 100 \mu_0 \frac{i}{2\pi} l \frac{dr}{r} = 100 \mu_0 \frac{i}{2\pi} l \ln \frac{r_z}{r_n}$$

$$\Phi = 100 \cdot 4\pi \cdot 10^{-7} \frac{10}{2\pi} 10 \ln \frac{2}{1} = 1.39 \text{ mWb}$$

Okrog jedra z magnetnim fluksom  $\Phi(t) = 6t + 0.1 \text{ Wb}$  je obroč upornosti  $120 \Omega$ . Kolikšno napetost kažeta voltmetra po sliki?

**Rešitev:**

V zanki se inducira napetost

$$u_i = -\frac{d\Phi}{dt} = -\frac{d}{dt}(6t + 0.1) = -6 \text{ V}$$


in v obroču teče tok

$$i = \frac{u_i}{R} = \frac{6}{120} = 50 \text{ mA.}$$

Voltmeter kaže padec napetosti na uporu, ki je vzporeden voltmetu



$$V_1 : U_{V1} = -iR_1 = -0.05 \cdot 120 \cdot \frac{3}{4} = -4.5 \text{ V.}$$
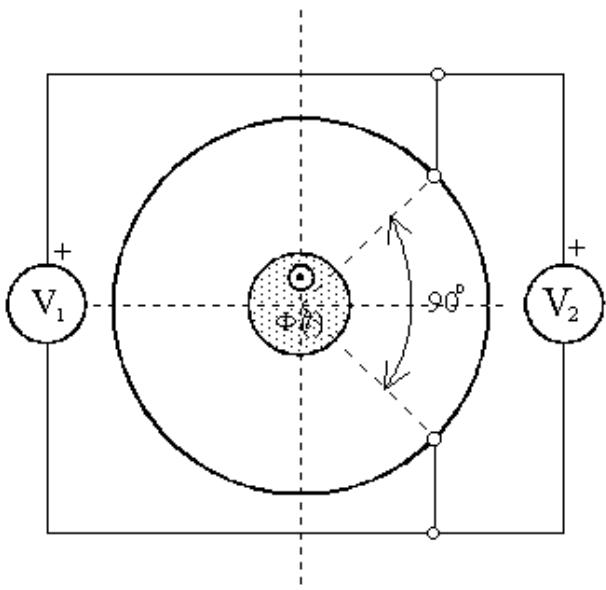
$$V_2 : U_{V2} = iR_2 = 0.05 \cdot 120 \cdot \frac{1}{4} = 1.5 \text{ V.}$$



V vezju spremenjamo  $R$  od nič do  $\infty$ . ( $0 \leq R < \infty$ ). Narišite diagram spremembe napetosti na induktivni upornosti  $jX_L$ !

**Rešitev:**

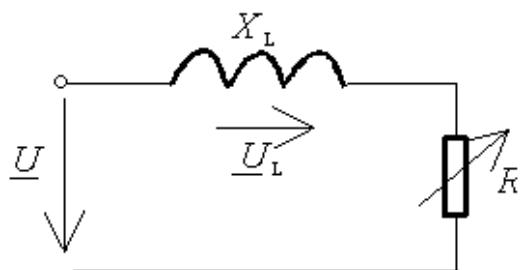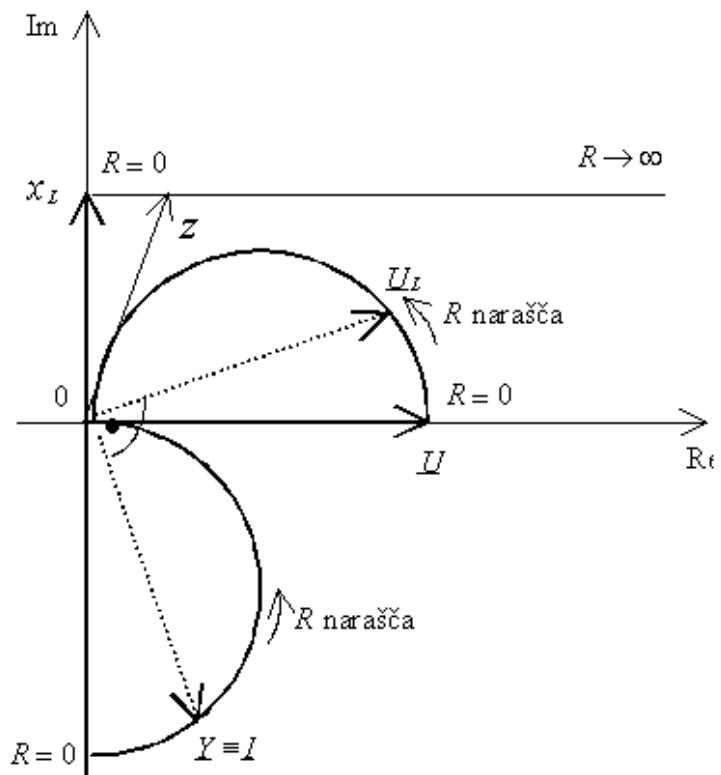

V trenutku  $t = 0$  izklopimo stikalo. Kolikšna je napetost na uporu  $R_2$  v času  $t_1 = 10^{-6}\text{s}$  ( $L = 100\text{ mH}$ ,  $R_1 = 6\Omega$ ,  $R_2 = 9\text{ k}\Omega$ )?

**Rešitev:**

$$U_{R_2} = i \cdot R_2$$

$$i = I_0 e^{-\frac{t}{\tau}}$$

$$I_0 = \frac{U}{R_1} = \frac{12}{6} = 2\text{A}$$

$$\tau = \frac{L}{R_1 + R_2} = 11.1\text{ }\mu\text{s}$$

$$i = 2 \cdot e^{-\frac{1}{11.1}} = 1.83\text{A}$$

$$U_{R_2} = 1.83 \cdot 9 \cdot 10^3 = 16.45\text{ kV.}$$

