

Izračunajte magnetno napetost

$$\Theta = \int_A^B \vec{H} \cdot d\vec{l} \text{ vzdolž krivulje } \mathcal{L} \text{ med točko A in}$$


točko B v okolici treh vodnikov po sliki ($i = 50 \text{ A}$, $a = 0.2 \text{ m}$)!

Rešitev:

$$\Theta_{AB} = \int_A^B \vec{H} \cdot d\vec{l} = \sum_k \frac{i_k}{2\pi} \cdot \varphi_k$$

$$\Theta_{AB} = \frac{2i}{2\pi} \cdot \frac{\pi}{2} - \frac{3i}{2\pi} \cdot \frac{\pi}{4} - \frac{2i}{2\pi} \cdot \arctg \frac{2a}{a}$$
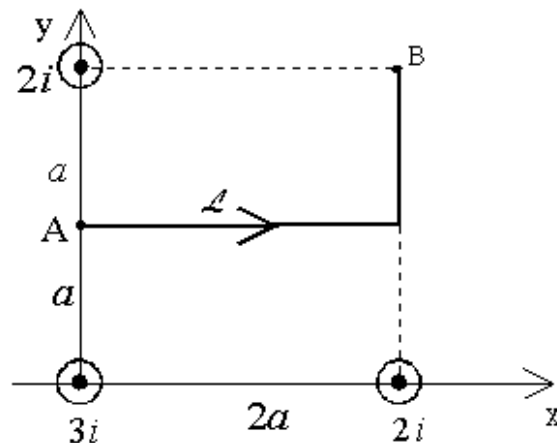
$$\Theta_{AB} = -0.23i = -11.4 \text{ A}$$



Po dvovodu omrežne napetosti 230 V/50 Hz teče tok efektivne vrednosti 25 A. Kolikšna efektivna napetost se inducira v vzporednem telefonskem vodu v dolžini 100 m po sliki ($a = 0.4$ m, $b = 0.2$ m, $c = 0.2$ m)?

Rešitev:

$$U_i = - \frac{d\Phi}{dt} = -M \frac{di}{dt}$$


$$\Phi = \mu_0 \frac{i}{2\pi} l \cdot \left(-\ln \frac{\sqrt{a^2 + (b+c)^2}}{\sqrt{a^2 + b^2}} + \ln \frac{b+c}{b} \right) = M \cdot i$$

$$M = 4 \pi 10^{-7} \cdot \frac{100}{2\pi} \ln \frac{0.4 \sqrt{0.4^2 + 0.2^2}}{0.2 \sqrt{0.4^2 + 0.4^2}} = 9.16 \mu\text{H}$$

$$i = 25\sqrt{2} \cos 314t$$

$$\frac{di}{dt} = -25\sqrt{2} \cdot 314 \sin 314t$$
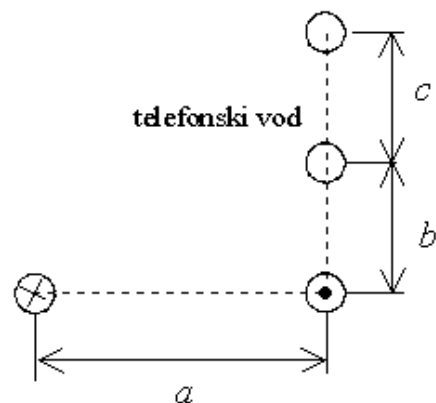
$$U = \omega IM = 314 \cdot 25 \cdot 9.16 \cdot 10^{-6} = 71.9 \text{ mV}$$



Ravnina $x = 0$ je meja dveh linearnih magnetnih snovi. V prostoru $x < 0$ je $\mu = 100\mu_0$ in vektor gostote magnetnega pretoka $\vec{B} = \vec{e}_x 5 + \vec{e}_y 2 + \vec{e}_z 3$ mT. V prostoru $x > 0$ je $\mu = 20\mu_0$. Na meji ni tokovne obloge. Kolikšen je vektor \vec{B} v prostoru $x > 0$?

Rešitev:

$$B_{1n} = B_{2n}, B_n = B_x$$

$$H_{1t} = H_{2t}, B_{2t} = \frac{\mu_2}{\mu_1} B_{1t}, B_{2y} = \frac{20\mu_0}{100\mu_0} \cdot 2 = 0.4 \text{ mT}, B_{2z} = \frac{20\mu_0}{100\mu_0} \cdot 3 = 0.6 \text{ mT}$$

$$\vec{B}_{(x>0)} = \vec{e}_x 5 + \vec{e}_y 0.4 + \vec{e}_z 0.6 \text{ mT}$$

Kolikšna je impedanca \underline{Z} med sponkama a in b ($k = 0.5$)?



Rešitev:

$$X_M = k \sqrt{X_{L1} \cdot X_{L2}} = 0.5 \sqrt{10 \cdot 40} = 10 \Omega$$

$$\underline{U} = \underline{I}_1 (10 + j10) + \underline{I}_1 \cdot j10$$

$$0 = \underline{I}_1 j10 + \underline{I}_2 j40 \rightarrow \underline{I}_2 = -\frac{\underline{I}_1}{4}$$
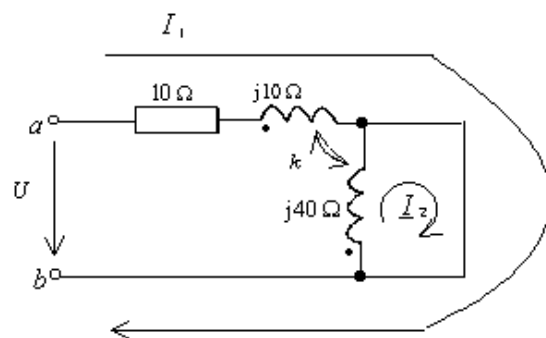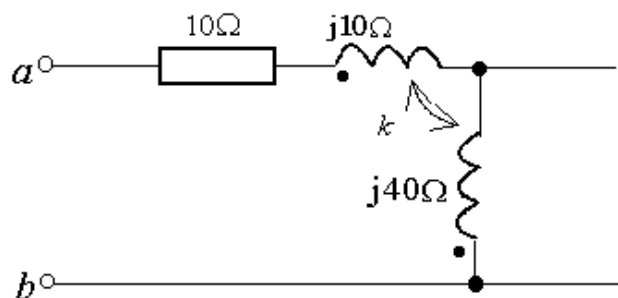
$$\underline{Z} = \frac{\underline{U}}{\underline{I}_1} = 10 + j7.5 \Omega$$



Trifazno breme je priključeno na simetrično trifazno omrežje 3x400/230 V s pozitivnim faznim zaporedjem napetosti. Kolikšna je delovna moč, ki se troši na bremenu?

Rešitev:

$$P = U_A'^2 / R_A$$

$$\underline{U}'_A = \underline{U}_A - \underline{U}_0, \quad \underline{U}_0 = \underline{I}_0 \cdot \underline{Z}_0$$

$$\underline{I}_0 = \frac{\underline{U}_A}{\underline{Z}_A} + \frac{\underline{U}_B}{\underline{Z}_B} + \frac{\underline{U}_C}{\underline{Z}_C} = 2.3 + j2.3 \text{ A}$$

$$\underline{Z}_0 = \frac{1}{1/\underline{Z}_A + 1/\underline{Z}_B + 1/\underline{Z}_C} = 20 + j40$$

$$\underline{U}_0 = -46 + j138 \text{ V}$$

$$\underline{U}'_A = 276 - j138 \text{ V}$$

$$P = 952.2 \text{ W}$$

